

TI Designs: TIDA-01466

适用于超声波模拟前端的低电压低噪声电源参考设计



说明

该参考设计是一款经过优化的电源，用于为超声波成像系统的八个 16 通道 AFE IC 供电。该电源设计通过使用单芯片直流/直流转换器 + LDO 组合稳压器以及将每个 LDO 输入设置为恰好高于压降来减少部件数，同时最大限度地提高效率。超低噪声 LDO 有助于实现更高的模数转换分辨率，从而实现更高的图像质量。该设计允许频率与系统时钟同步，从而允许设计人员应用滤波技术以消除接地回路上的电源开关噪声或使用扩频时钟以降低 EMI。该设计实现了电子保险丝 IC，从而提供简单灵活的过流保护。

资源

TIDA-01466	设计文件夹
TPS54122-Q1	产品文件夹
TPS54824	产品文件夹
TPS7A84	产品文件夹
TPS7A8300	产品文件夹
LM3881	产品文件夹
CDCLVC1106	产品文件夹
TPS25926	产品文件夹
TLV704	产品文件夹




咨询我们的 E2E 专家


特性

- 适用于 12V 输入超声波系统前端
- 具有输入电流限制为 4.2A 的电子保险丝
- 能够为八个 AFE 供电，通道多达 128 个（可扩展通道数），支持 36W 功率输出
- 组合直流/直流转换器 + LDO IC 可通过将 LDO 输入设置为恰好高于压降电压来最大限度地提高 LDO 效率
- 使用高 PSRR 和超低噪声 ($4.4\mu\text{V}_{\text{RMS}}$) LDO 来实现可能的最高模数转换分辨率
- 在同一块 T/R 板上为所有 AFE 提供共用的同步电源，从而减小布板空间，同时有助于降低噪声和消除 EMI

应用

- 医用超声波扫描仪
- 声纳成像设备
- 无损评价设备

 

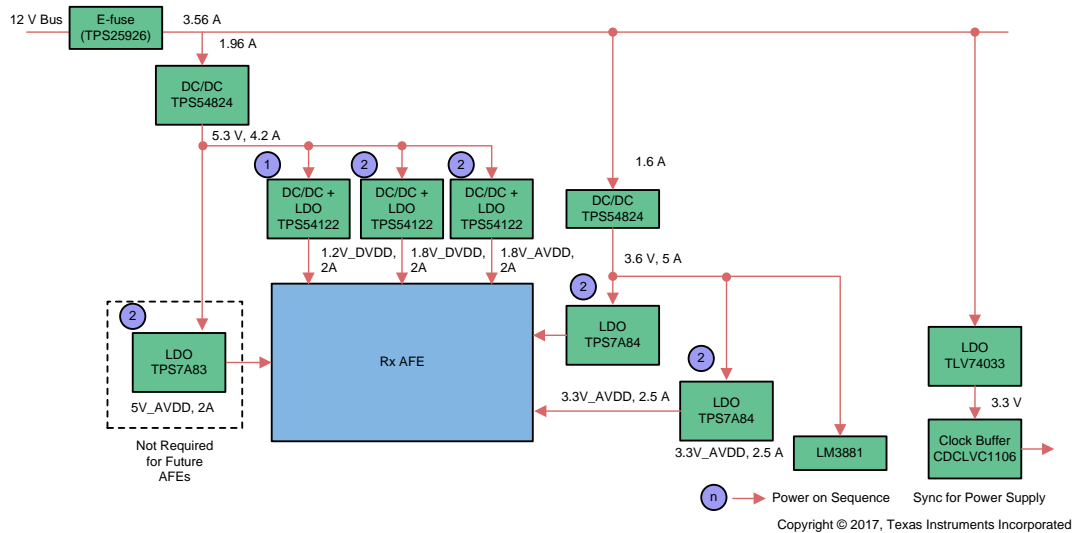

该 TI 参考设计末尾的重要声明表述了授权使用、知识产权问题和其他重要的免责声明和信息。

1 System Description

Ultrasound imaging systems use high-frequency sound waves (several MHz or more) to image internal structures by the differing reflection signals produced when a beam of sound waves is projected into the body and bounces back at the interfaces between those structures. Ultrasound diagnosis differs from radiological diagnosis in that there is no ionizing radiation involved. The use of ultrasound to create images is based on the reflection and transmission of a wave at a boundary. When an ultrasound wave travels inside an object that is made up of different materials (such as the human body), each time it encounters a boundary (for example, between bone and muscle, or muscle and fat), part of the wave is reflected and part of it is transmitted. The reflected rays are detected and used to construct an image of the object.

图 1 显示了超声波成像系统的块图。超声波成像系统具有发射器部分和线性或脉冲发射器部分，该部分为超声波换能器生成激励脉冲，其频率通常为 1 到 15 MHz，幅度为 ± 2.5 到 ± 100 V。在发射 (Tx) 侧，Tx 波束成形器确定延迟模式和脉冲串，以设置所需的发射焦点。超声波换能器是压电换能器，它们在施加电脉冲时会发生机械变形，从而产生超声波波形。该过程也是可逆的，并且可以将超声波转换为电能。接收换能器接收到的反射信号由接收器模拟前端 (AFE) 进行调理。AFE 通常与电压控制放大器 (VCA)、低噪声放大器 (LNA)、PGA 和模拟-to-数字转换器 (ADC) 集成。AFE 产生数字输出，该输出由接收波束成形器 FPGA 接收，然后由 DSP 进行处理、图像形成和显示。在接收 (Rx) 侧，有一个 T/R 开关，通常为二极管桥，该开关阻止高压 Tx 脉冲。该开关后面是一个 LNA 和一个或多个可变增益放大器 (VGAs)，它们实现时间增益补偿 (TGC)。时间增益控制——为来自体内更深处的信号（因此到达较晚）提供增加的增益——由操作员控制并用于保持图像均匀性。

As continuous wave (CW) Doppler has the largest dynamic range of all signals in an ultrasound system—during CW, a sine wave is transmitted continuously with half of the transducer array while the other half is receiving. There is a strong tendency for the Tx signal to leak into the Rx side; there are also strong reflections coming from stationary body parts that are close to the surface. This tends to interfere with examination of, for example, blood flow in a vein deep in the body along with very weak Doppler signals. At its current state, CW Doppler signals cannot be processed through the main imaging (B-mode) and pulsed wave (PW) Doppler (F-mode) path in a digital beamforming system; for this reason, images can be formed as a sequence of analog levels that are delayed with analog delay lines, summed, and converted to digital after summation, indicated as CW Doppler processing. The Rx AFE also integrates CW mixer and a low-noise summer to form a CWD beamformer. LNA output is passed through the CW mixer to demodulate the Doppler frequencies and produce I and Q signals. These I and Q signals from all the channels in the same AFE are summed at a low-noise summer. Sixteen selectable phase delays can be applied to each analog input signal. The most common use of ultrasound, creating images, has industrial and medical applications. Ultrasound systems has different forms or variants available in the market including cart based, portable, or handheld.

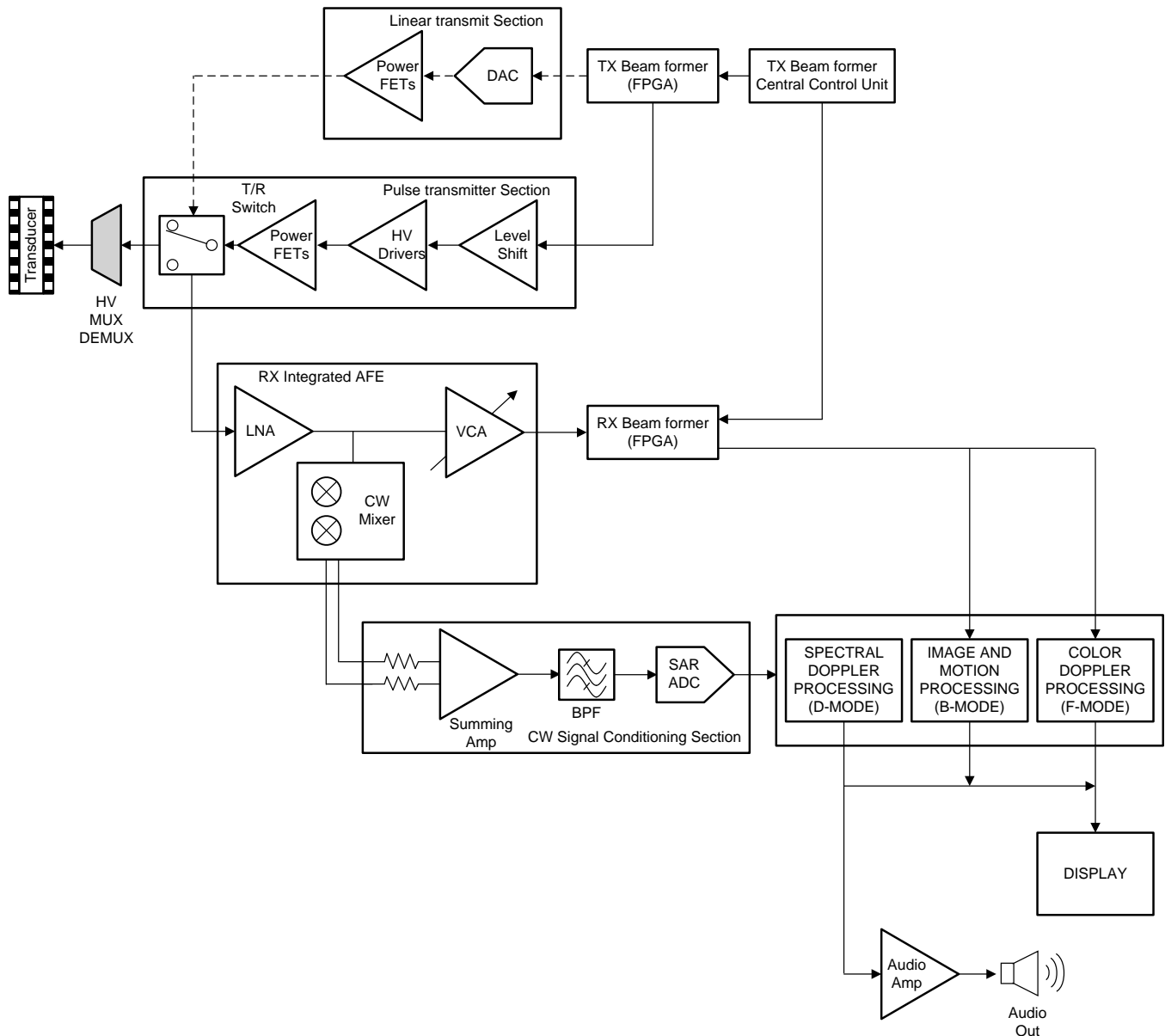


图 1. Ultrasound Imaging System Block Diagram

This reference design is a power supply optimized specifically for providing power to eight 16-channel receive AFE ICs for ultrasound imaging systems. This design uses single-chip DC-DC converter + LDO combo regulators to obtain maximum efficiency by setting the low dropout (LDO) input just above the dropout voltage while taking full advantage of the LDO PSRR and reducing part count. In addition, ultra-low-noise LDOs helps to attain highest resolution possible from A/D conversion, leading to higher image quality. This reference design is capable of switching frequency synchronization with the master and system clock frequency to aid system designers apply simple filtering techniques to remove power supply switching noise on ground loops or use spread-spectrum clocking to reduce EMI. Additionally, the design implements an eFuse IC, providing a simple and flexible means of overcurrent protection.

1.1 Key System Specifications

表 1. Key System Specifications

PARAMETER	SPECIFICATIONS
Input voltage (V)	12 V
OUTPUT VOLTAGES (V)	
Vout_1, Iout_1	5 V, 2 A
Vout_2, Iout_2	3.3 V, 2.5 A
Vout_3, Iout_3	3.3 V, 2.5 A
Vout_4, Iout_4	1.8 V, 2 A
Vout_5, Iout_5	1.8 V, 2 A
Vout_6, Iout_6	1.2 V, 2 A
LOAD REGULATION	
Vout_1 (5 V)	0.04%
Vout_2 (3.3V_1)	0.091%
Vout_3 (3.3V_2)	0.06%
Vout_4 (1.8V_1)	0.78%
Vout_5 (1.8V_2)	0.723%
Vout_6 (1.2V)	0.90%
OUTPUT VOLTAGE NOISE (dBm)	
Vout_5V	Max -60.04 dBm at 524 kHz
Vout_3V3	Max -73.23 dBm at 524 kHz
Vout_1V8	Max -50.23 dBm at 480 kHz
Vout_1V2	Max -60.47 dBm at 476.2 kHz
Rated output power (W)	36.1 W
Efficiency	91.20%
Protections	The overall power exceeds 50-W eFuse cuts off, this sets a limit of 4.2 A

2 System Overview

2.1 Block Diagram

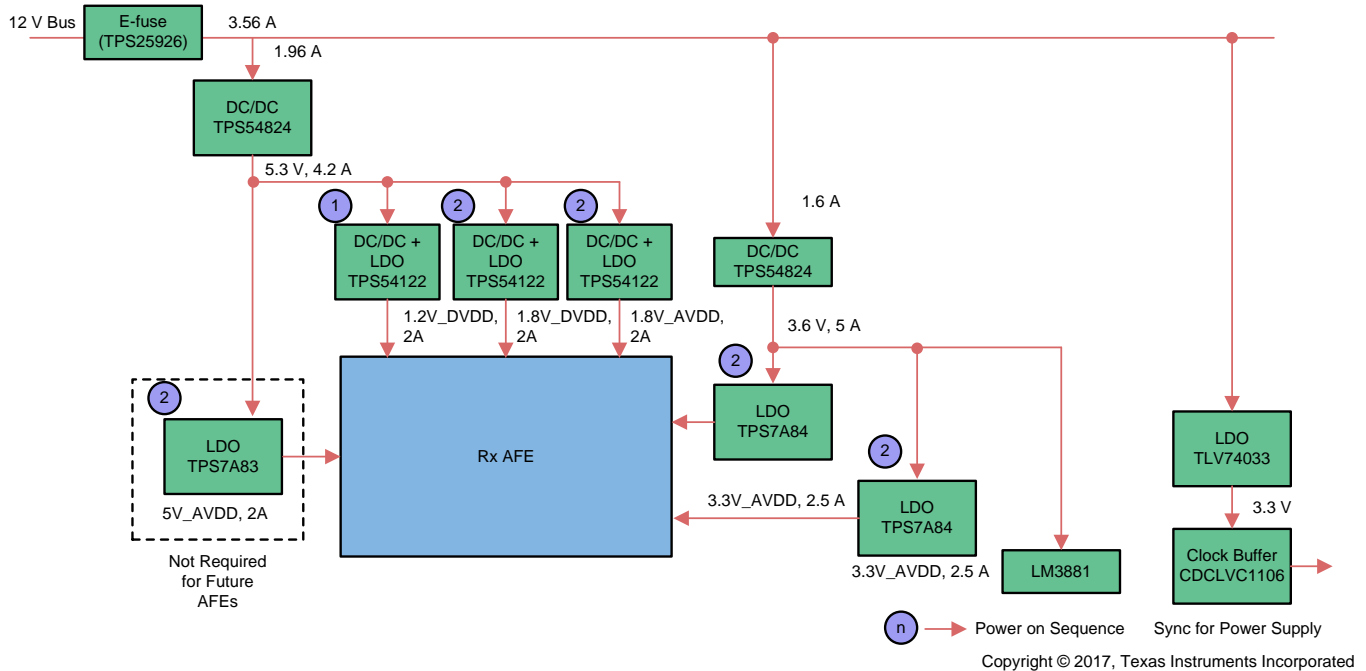


图 2. TIDA-01466 Block Diagram

2.2 Highlighted Products

2.2.1 TPS54122

The TPS54122 device combines the efficiency of a step-down switching (DC-DC) converter with a high power-supply rejection (PSR), low-noise, LDO to provide an ultra-low-noise power supply that delivers QuietSupply™ rails to noise-sensitive applications. The TPS54122 device is ideally suited for systems with 5-V power buses and can support 3-A continuous output current on both the DC-DC or LDO output. The LDO output voltage can be set from 0.8 to 3.6 V and the DC-DC can be adjusted from 0.83 to 5.0 V using external resistors. The TPS54122 device can be used in a wide range of low-noise applications because the DC-DC converter and LDO are completely configurable. In addition, the TPS54122 device includes features such as soft-start, switching frequency synchronization, and a power-good signal. The TPS54122 device can also be configured as a dual-supply rail device, supplying a total of 3 A. The TPS54122 device is available in a space-saving, 3.50-mm×5.50-mm VQFN package, and is specified to operate over a –40°C to 125°C ambient temperature range.

2.2.2 TPS54824

The TPS54824 is a full featured 17-V, 8-A synchronous step-down converter in a 3.5-mm×3.5-mm HotRod™ QFN package. The device is optimized for small solution size through high efficiency and integrating the high-side and low-side MOSFETs. Further space savings are achieved through peak current mode control, which reduces component count, and by selecting a high switching frequency, which reduces the inductor footprint. The peak current mode control simplifies the loop compensation and provides fast transient response. Cycle-by-cycle peak current limiting on the high-side and low-side sourcing current limit protects the device in overload situations. Hiccup limits MOSFET power dissipation if

a short circuit or overloading fault persists. A power good supervisor circuit monitors the regulator output. The PGOOD pin is an open drain output and goes high impedance when the output voltage is in regulation. An internal deglitch time prevents the PGOOD pin from pulling low unless a fault has occurred. A dedicated EN pin can be used to control the regulator on/off and adjust the input undervoltage lockout. The output voltage startup ramp is controlled by the SS/TRK pin, which allows operation as either a standalone power supply or in tracking situations.

2.2.3 TPS7A84

The TPS7A84 is a low-noise ($4.4 \mu\text{V}_{\text{RMS}}$) LDO capable of sourcing 3 A with only 180 mV of maximum dropout. The device output voltage is pin-programmable from 0.8 to 3.95 V and adjustable from 0.8 to 5.0 V using an external resistor divider. The combination of low noise ($4.4 \mu\text{V}_{\text{RMS}}$), high PSRR, and high-output current capability makes the TPS7A84 ideal to power noise-sensitive components such as those found in high-speed communications, video, medical, or test and measurement applications. The high performance of the TPS7A84 limits power-supply-generated phase noise and clock jitter, making this device ideal for powering high-performance serializer and deserializer (SerDes), ADCs, digital-to-analog converters (DACs), and RF components. Specifically, RF amplifiers benefit from the high-performance and 5.0-V output capability of the device. For digital loads [such as application-specific integrated circuits (ASICs), field-programmable gate arrays (FPGAs), and digital signal processors (DSPs)] requiring low-input, low-output (LILO) voltage operation, the exceptional accuracy (0.75% over load and temperature), remote sensing, excellent transient performance, and soft-start capabilities of the TPS7A84 ensure optimal system performance. The versatility of the TPS7A84 makes the device a component of choice for many demanding applications.

2.2.4 TPS7A83

The TPS7A83A device is a low-noise ($4.4 \mu\text{V}_{\text{RMS}}$) LDO capable of sourcing 2 A with only 200 mV of maximum dropout. The device output voltage is pin-programmable from 0.8 to 3.95 V and adjustable from 0.8 to 5.2 V using an external resistor divider. The combination of low noise ($4.4 \mu\text{V}_{\text{RMS}}$), high PSRR, and high-output current capability makes the TPS7A83A ideal to power noise-sensitive components such as those found in high-speed communications, video, medical, or test and measurement applications. The high performance of the TPS7A83A limits power-supply-generated phase noise and clock jitter, making this device ideal for powering high-performance SerDes, ADCs, DACs, and RF components. Specifically, RF amplifiers benefit from the high-performance and 5.2-V output capability of the device. For digital loads (such as ASICs, FPGAs, and DSPs) requiring LILO voltage operation, the exceptional accuracy (0.75% over load and temperature), remote sensing, excellent transient performance, and soft-start capabilities of the TPS7A83A ensure optimal system performance. The versatility of the TPS7A83A makes the device a component of choice for many demanding applications.

2.2.5 LM3881

The LM3881 Simple Power Sequencer offers the easiest method to control the power-up and power-down of multiple power supplies (switching or linear regulators). By staggering the start-up sequence, it is possible to avoid latch conditions or large inrush currents that can affect the reliability of the system. Available in VSSOP-8 package, the Simple Sequencer contains a precision enable pin and three open-drain output flags. When the LM3881 is enabled, the three output flags sequentially release after individual time delays, thus permitting the connected power supplies to start up. The output flags follow a reverse sequence during power down to avoid latch conditions. Time delays are defined using an external capacitor, and the output flag states can be inverted by the user.

2.2.6 TLV70433

The TLV704 series of LDO regulators are ultra-low quiescent current devices designed for extremely power-sensitive applications. Quiescent current is virtually constant over the complete load current and ambient temperature range. These devices are an ideal power-management attachment to low-power microcontrollers, such as the MSP430™ MCU. The TLV704 operates over a wide operating input voltage of 2.5 to 24 V. Thus, the device is an excellent choice for both battery-powered systems as well as industrial applications that undergo large line transients. The TLV704 is available in a 3-mm × 3-mm SOT23-5 package, which is ideal for cost-effective board manufacturing.

2.2.7 TPS25926

The TPS25925x/TPS25926x family of eFuses is a highly integrated circuit protection and power management solution in a tiny package. The devices use few external components and provide multiple protection modes. They are a robust defense against overloads, shorts circuits, voltage surges, excessive inrush current. Current limit level can be set with a single external resistor and current limit set has a typical accuracy of ±15%. Overvoltage events are limited by internal clamping circuits to a safe fixed maximum with no external components required. TPS25926x devices provide overvoltage protection (OVP) for 12-V systems and TPS25925x devices for 5-V systems. In cases with particular voltage ramp requirements, a dV/dT pin is provided that can be programmed with a single capacitor to ensure proper output ramp rates.

2.2.8 CDCLVC1106

The CDCLVC11xx is a modular, high-performance, low-skew, general-purpose clock buffer family from Texas Instruments. The entire family is designed with a modular approach in mind. It is intended to round up TI's series of LVCMOS clock generators. Seven different fan-out variations, 1:2 to 1:12, are available. All of the devices are pin-compatible to each other for easy handling. All family members share the same high performing characteristics such as low additive jitter, low skew, and wide operating temperature range. The CDCLVC11xx supports an asynchronous output enable control (1G) which switches the outputs into a low state when 1G is low. The CDCLVC11xx family operates in a 2.5-V and 3.3-V environment and are characterized for operation from –40°C to 85°C.

2.3 System Design Theory

This reference design is a power supply designed for providing power to eight 16-channel receive AFEs of 12-V ultrasound Imaging systems. This design is based on the specifications of the TI Ultrasound AFE, AFE5818. 表 2 shows the specification summary of eight AFE5818 devices for a 128-channel ultrasound system.

表 2. Specification Summary of 8 AFE5818 for 128-Channel System

AFE RAIL	V _{IN}	V _{OUT}	CURRENT (SINGLE AFE ONLY)	CURRENT (128 CHANNELS, 8 AFEs)	SOLUTION
AVDD_5V	12 V	5 V	0.14 A	1.12 A	Buck + High PSRR LDO
AVDD_3V3	12 V	3.3 V	0.5 A	4 A	Buck + High PSRR LDO
AVDD_1V8	12 V	1.8 V	0.2 A	1.6 A	Buck + DC-DC and LDO
AVDD_1P2	12 V	1.2 V	0.2 A	1.6 A	Buck + DC-DC and LDO

表 2. Specification Summary of 8 AFE5818 for 128-Channel System (continued)

AFE RAIL	V _{IN}	V _{OUT}	CURRENT (SINGLE AFE ONLY)	CURRENT (128 CHANNELS, 8 AFES)	SOLUTION
AVDD_1P8	12 V	1.8 V	0.15 A	1.2 A	Buck + DC-DC and LDO

This reference design has three low-noise DC-DC converter + LDO combos (TPS54122) to provide 1.2 DVDD, 1.8 DVDD, and 1.8 AVDD for the AFEs, a low-dropout voltage regulator (TPS7A83) to provide 5 AVDD, a high-current, high-accuracy, low-noise LDO voltage regulator (TPS7A84) to provide 3.3 AVDD, and two 8-A synchronous swift step-down converters (TPS54824) to generate the input voltages (5.6 V and 3.6 V) for TPS54122, TPS7A83, and TPS7A84. This reference design also uses a power sequencer with adjustable timing (LM3881) for the power sequencing of AFE5818. A low-jitter 1:6 LVCMOS fan out clock buffer (CDCLVC1106) acts as a clock signal fan out buffer for external clock in sync mode for all the DC-DC converters used on board. A 12-V, accurate adjustable current limit eFuse (TPS25926) provides multiple protections. A 24-V, 150-mA, ultra-low I_Q LDO regulator (TLV70433) provides power to the clock buffer.

2.3.1 5.6-V Generation Using DC-DC Converter

图 3 shows the switching circuit to generate 5.6 V using the TPS54824 from a 12-V input. This 5.6 V is used as input for the LDO TPS7A83 for 5-V generation and input to the DC-DC + LDO combo TPS54122 for 1.8 DVDD, 1.8 AVDD, and 1.2 DVDD generation. The TPS54824 DC-DC is a synchronous buck converter designed to provide up to 4.2 A.

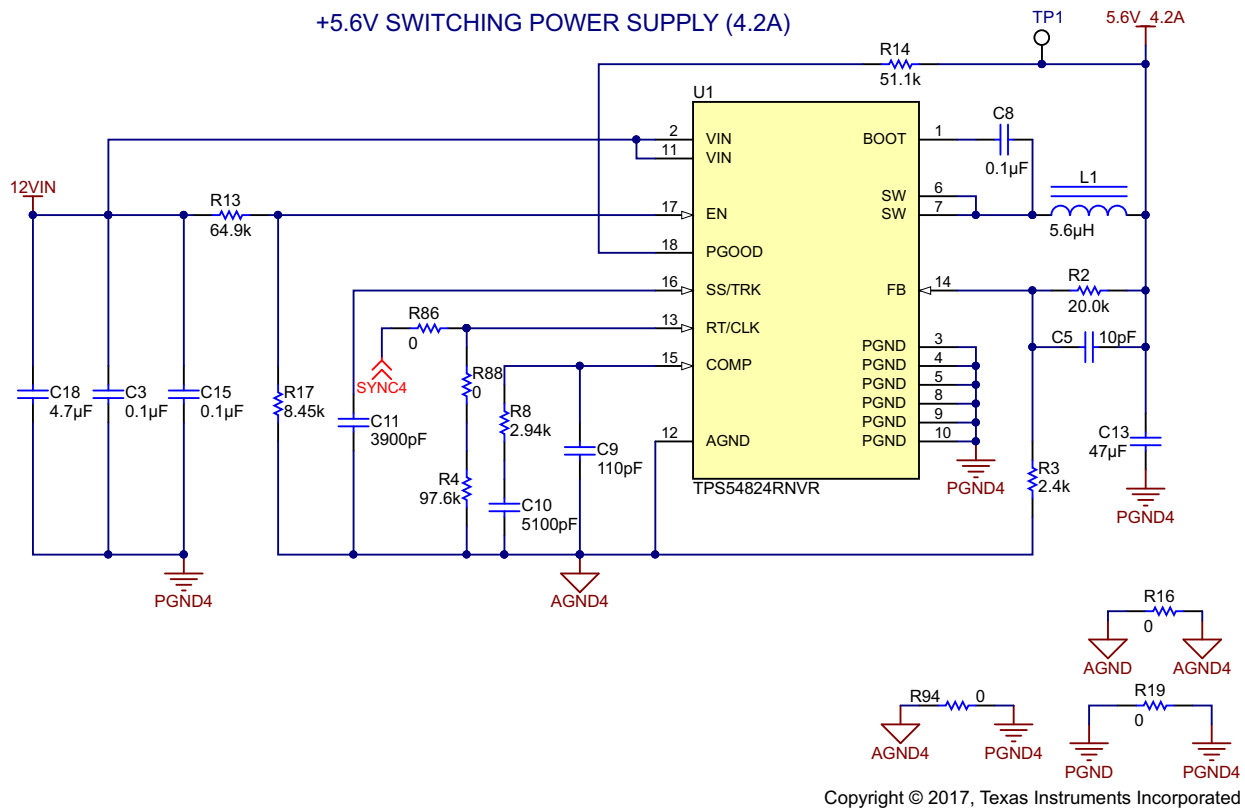


图 3. 5.6-V Generation Using DC-DC Converter

2.3.1.1 Voltage Set Point

The output voltage is set by the resistor divider network of R2 and R3, and the reference voltage V_{REF} is 0.6 V. Output voltage can be calculated using 公式 1.

$$R2 = R3 \times \left(\frac{V_{OUT}}{0.6 \text{ V}} - 1 \right) \quad (1)$$

Where:

- R2 = 20 k Ω
- R3 = 2.4 k Ω

Substituting R2 and R3 in 公式 1 gives:

$$V_{OUT} = \left(\frac{20 \text{ k}\Omega}{2.4 \text{ k}\Omega} + 1 \right) \times 0.6 \text{ V} = 5.6 \text{ V}$$

2.3.1.2 Adjustable Switching Frequency and Synchronization (RT/CLK)

The RT/CLK pin can set the switching frequency of the device in two modes: RT and CLK.

In RT mode, the R4 (R_T) resistor is connected between the RT/CLK pin and GND. The switching frequency of the device can be adjustable by using a resistor R4 (RT) of value, which ranges from 50 to 150 kΩ based on the inductor rating chosen for the DC-DC converter. To determine the value of the RT resistor for a given switching frequency (F_{SW}), use [公式 2](#).

$$F_{SW} \text{ (kHz)} = 43660 \times R_T \text{ (k}\Omega\text{)}^{-0.973} \quad (2)$$

Where:

- R4 = 97.6 kΩ

Substituting R4 in [公式 2](#) gives:

$$F_{SW} \text{ (kHz)} = 43660 \times 97.6^{-0.973} = 506 \text{ kHz}$$

2.3.1.3 CLK Mode

In CLK mode, an external clock is connected through the clock buffer (U11) to the RT/CLK pin. The DC-DC converter is synchronized to the external clock frequency with an internal phase-locked loop (PLL) circuit. The DC-DC converter is able to automatically detect the required mode and switch from RT mode to CLK mode. CLK mode overrides RT mode. An internal PLL is implemented to allow synchronization between 200 and 1600 kHz and to easily switch from RT mode to CLK mode. To implement the synchronization feature, connect a square-wave clock signal to the RT/CLK pin with a minimum on-time of at least 35 ns. The clock signal amplitude must transition from lower than 0.8 V and higher than 2 V. The start of the switching cycle is synchronized to the falling edge of the RT/CLK pin.

In this reference design, 0-Ω resistors R86 and R88 are used on board to select between RT/CLK mode. Placing R86 resistor sets external sync and placing R88 sets CLK mode. See the TPS54824 datasheet ([SLVSDC9](#)) for more details.

2.3.1.4 Adjustable UVLO

The undervoltage lockout (UVLO) can be adjusted externally using R13 and R17. See the TPS54824 datasheet ([SLVSDC9](#)) for detailed instructions for setting the external UVLO. Additionally, the TPS54824 provides adjustable soft start and a power good output.

See the TPS54824 datasheet ([SLVSDC9](#)) and TPS54824 EVM user's guide ([SLVUAX8](#)) for the detailed design instructions and recommendations. See the Texas Instruments [WEBENCH® Design Center](#) for generating solutions using this part.

2.3.2 3.6-V Generation Using DC-DC Converter

图 4 shows the switching circuit to generate 3.6 V using TPS54824 from a 12-V input. This 3.6 V is used as input for the two LDOs (TPS7A84) to generate 3.3 V. The TPS54824 DC-DC is a synchronous buck converter designed to provide up to 5 A.

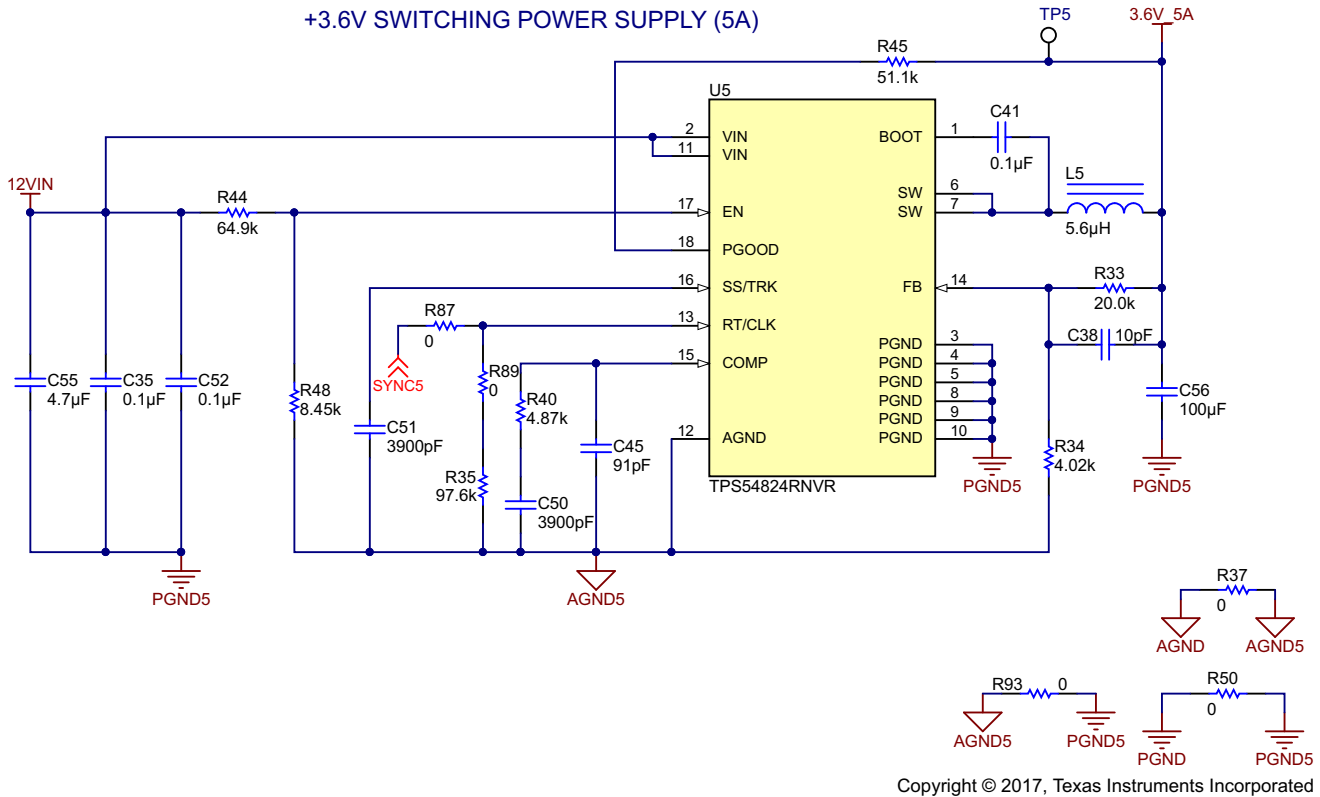


图 4. 3.6-V Generation Using DC-DC Converter

2.3.2.1 Voltage Set Point

The output voltage is set by the resistor divider network of R33 and R34 and the reference voltage (V_{REF}) is 0.6 V. Output voltage can be calculated using 公式 3.

$$R33 = R34 \times \left(\frac{V_{OUT}}{0.6\text{ V}} - 1 \right) \tag{3}$$

Where:

- R33 = 20 kΩ
- R34 = 4.02 kΩ

Substituting R33 and R34 in 公式 3 gives:

$$V_{OUT} = \left(\frac{20\text{ k}\Omega}{4.02\text{ k}\Omega} + 1 \right) \times 0.6\text{ V} = 3.6\text{ V}$$

2.3.2.2 Adjustable Switching Frequency and Synchronization (RT/CLK)

The RT/CLK pin can set the switching frequency of the device in two modes: RT and CLK.

In RT mode, the R35 (RT) resistor is connected between the RT/CLK pin and GND. The switching frequency of the device can be adjustable by using a resistor R35 (RT) of value, which ranges from 50 to 150 kΩ based on the inductor rating chosen for the DC-DC converter. To determine the value of the RT resistor for a given switching frequency (F_{SW}), use [公式 4](#).

$$F_{SW} \text{ (kHz)} = 43660 \times R_T \text{ (k}\Omega\text{)}^{-0.973} \quad (4)$$

Where:

- R35 = 97.6 kΩ

Substituting F_{SW} in [公式 4](#) gives:

$$F_{SW} \text{ (kHz)} = 43660 \times 97.6^{-0.973} = 506 \text{ kHz}$$

2.3.2.3 CLK Mode

See [节 2.3.1](#) for CLK mode operation using the TPS54824.

In this reference design, 0-Ω resistors R87 and R89 are used on board to select between RT/CLK mode. Placing an R87 resistor sets external sync, and placing R89 sets CLK mode. See the TPS54824 datasheet ([SLVSDC9](#)) for more details

2.3.2.4 Adjustable UVLO

The UVLO can be adjusted externally using R44 and R48. See the TPS54824 datasheet ([SLVSDC9](#)) for detailed instructions for setting the external UVLO. Additionally, the TPS54824 provides adjustable soft start and a power good output.

See the TPS54824 datasheet and TPS54824 EVM user's guide ([SLVUAX8](#)) for the detailed design instructions and recommendations. See the Texas Instruments [WEBENCH Design Center](#) for generating solutions using this part.

2.3.3 1.2-V and 1.8-V Generation Using DC-DC Converter + LDO

[图 5](#) shows the TPS54122 DC-DC + LDO combo circuit to generate 1.2 DVDD from a 5.6-V input. The TPS54122 is designed to provide up to 2 A. With the TPS54122's flexibility of having a DC-DC converter and an LDO in a single device, it is possible to obtain maximum LDO efficiency by setting LDO input just above the dropout voltage. This demonstrates the printed circuit board (PCB) space saving compared to standalone switcher and LDO topologies. The TPS54122 device combines the efficiency of a step-down switching (DC-DC) converter with a high power-supply rejection (PSR), low-noise, LDO to provide an ultra-low-noise power supply that delivers quiet supply rails. LDO is kept 0.5 V for good PSRR with a DC-DC converter output of 1.7 V.

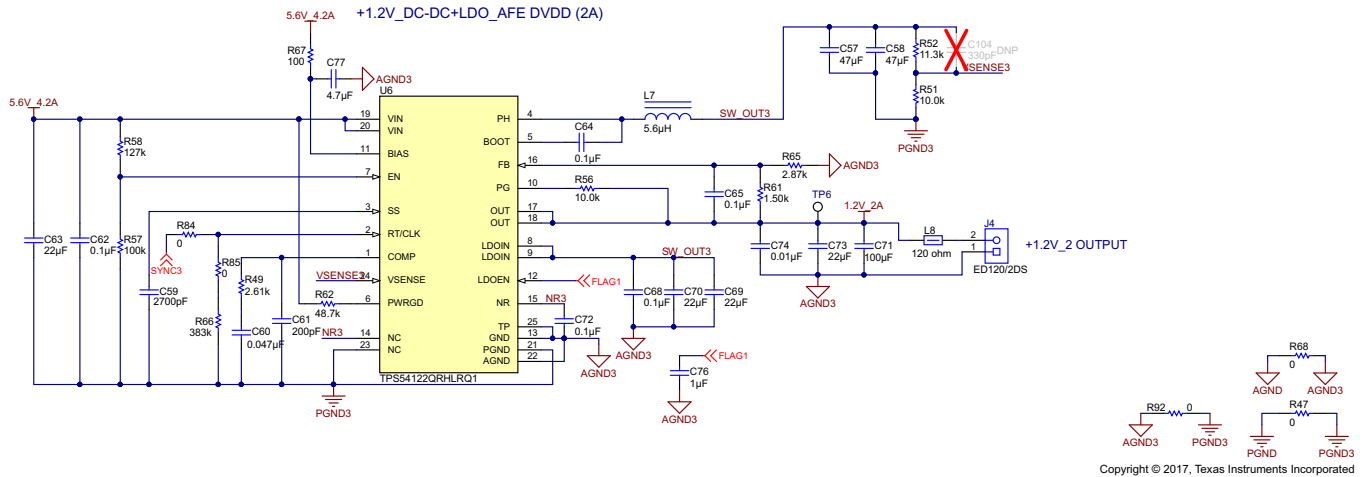


图 5. 1.2-V Generation Using TPS54122

2.3.3.1 DC-DC Converter Output Voltage Set Point

The switcher output voltage can be set using 公式 5.

$$R52 = R51 \times \left(\frac{V_{OUT}}{V_{REF}} - 1 \right) \tag{5}$$

Where:

- R52 = 11.3 kΩ
- R51 = 10 kΩ
- V_{REF} = 0.827 V

Substituting R52, R51, and V_{REF} in 公式 5 gives:

$$V_{OUT} = \left(\frac{11.3 \text{ k}\Omega}{10 \text{ k}\Omega} + 1 \right) \times 0.827 \text{ V} = 1.76 \text{ V}$$

2.3.3.2 LDO Output Voltage Set Point

The LDO output voltage can be set using 公式 6.

$$R61 = R65 \times \left(\frac{V_{OUT}}{V_{REF}} - 1 \right) \tag{6}$$

Where:

- R61 = 1.5 kΩ
- R65 = 2.87 kΩ
- V_{REF} = 0.8 V

Substituting R61, R65, and V_{REF} in 公式 6 gives:

$$V_{OUT} = \left(\frac{1.5 \text{ k}\Omega}{2.87 \text{ k}\Omega} + 1 \right) \times 0.8 \text{ V} = 1.218 \text{ V}$$

2.3.3.3 Adjustable Switching Frequency and Synchronization (RT/CLK)

In RT mode, the R66 (RT) resistor is connected between the RT/CLK pin and GND. The switching frequency of the device can be adjustable by using a resistor R66 (RT) of value, which ranges from 350 to 450 kΩ based on the inductor rating chosen for the DC-DC converter. To determine the value of the RT resistor for a given switching frequency (F_{sw}), use [公式 7](#).

$$R_T \text{ (k}\Omega\text{)} = 311890 \times F_{sw} \text{ (kHz)}^{-1.0793} \quad (7)$$

Where:

- $R_T = R66 = 383 \text{ k}\Omega$

Substituting $R_T = 383 \text{ k}\Omega$ in [公式 7](#) gives $F_{sw} = 500 \text{ kHz}$.

2.3.3.4 CLK Mode

In CLK mode, an external clock is connected through the clock buffer (U11) to the RT/CLK pin. The DC-DC converter is synchronized to the external clock frequency with an internal phase-locked loop (PLL) circuit. The DC-DC converter is able to automatically detect the required mode and switch from RT mode to CLK mode. CLK mode overrides RT mode. An internal PLL is implemented to allow synchronization between 300 kHz and 2 MHz and to easily switch from RT mode to CLK mode. To implement the synchronization feature, connect a square-wave clock signal to the RT/CLK pin with a minimum on-time of at least 75 ns. The clock signal amplitude must transition to less than 0.6 V and to greater than 1.6 V. The PH rising edge is synchronized to the RT/CLK pin falling edge. In applications where the RT mode and CLK mode are required, the device can be configured to have an RT resistor and an external clock connected at the same time to the RT/CLK pin. If no external clock is present, the device functions in RT mode and the switching frequency is set by the R66 (RT) resistor.

The EN pin of the 1.2-V LDO is connected to the output (Flag1) of LM3881 as per the sequencing requirement of AFE5818 mentioned in [节 2.3.6](#).

In this reference design, 0-Ω resistors R84 and R85 are used on board to select between RT/CLK mode. Placing an R84 resistor sets external sync and placing R85 sets CLK mode.

2.3.3.5 Soft-Start of DC-DC Converter

The rate at which the output voltage of the switcher rises up to the full operational level during the start-up phase is controlled through the SS pin. The CSS capacitor is connected between the SS pin and ground. The size of the capacitor determines the soft-start ramp-up time (t_{ss} , 10% to 90%), as shown in [公式 8](#).

$$t_{ss} \text{ (ms)} = \frac{C_{SS} \text{ (nF)} \times V_{REF} \text{ (V)}}{I_{SS} \text{ (}\mu\text{A)}} \quad (8)$$

Where:

- $V_{REF} \text{ (V)} = 0.827 \text{ V}$
- $C_{SS} \text{ (nF)} = 2.7 \text{ nF}$
- $I_{SS} \text{ (}\mu\text{A)} = 2.2 \text{ }\mu\text{A}$

Substituting $V_{REF} \text{ (V)}$, $C_{SS} \text{ (nF)}$, and $I_{SS} \text{ (}\mu\text{A)}$ in [公式 8](#) gives:

$$t_{ss} = \frac{(2.7 \times 0.827)}{2.2} = 1.01 \text{ ms}$$

The device has an internal pullup current source (I_{SS}) of 2.2 μA that charges the external soft-start capacitor, C_{SS} . The voltage reference, V_{REF} , for this device is 0.827 V. By sourcing a constant current onto the capacitor, the device linearly ramps up the voltage on the SS pin that corresponds to the voltage on the FB pin, and thus, the output voltage of the switcher. When the voltage on the SS pin exceeds the value of the internal reference, the device starts regulating to the internal reference value. If the input UVLO is triggered (or the EN pin is pulled below 1.21 V or a thermal shutdown event occurs), then the device stops switching and enters low-current operation. At the subsequent power-up when the shutdown condition is removed, the DC-DC does not start switching until the SS pin is discharged to ground, ensuring proper soft-start behavior.

2.3.3.6 NR Soft-Start Time and LDO Start-Up

The primary purpose of the NR capacitor is to filter the noise from the LDO band gap and thereby reduce the LDO output noise. However, the NR capacitor affects the start-up time of the LDO. The TPS54122 device has a soft-start circuit to charge CNR at a controlled rate for a monotonic soft-start. The controlled voltage ramp of the output reduces peak inrush current during start-up.

The soft-start ramp time depends on the soft-start charging current (I_{NR}), the external noise-reduction capacitor (CNR), and the internal voltage reference of the LDO and can be calculated as shown in [公式 9](#).

$$t_{SS} \text{ (ms)} = 1096 \times \text{CNR} \text{ (}\mu\text{F)} \quad (9)$$

Where:

- CNR (μF) = 0.1 μF

Substituting CNR (μF) in [公式 9](#) gives:

$$t_{SS} \text{ (ms)} = 1096 \times 0.1 \mu\text{F} = 109.6 \text{ ms}$$

In this reference design, the delay between 1.2 V and all other rails (1.8 AVDD, 1.8 DVDD, 5 AVDD, 3.3 AVDD) is set as 50 ms by choosing the Tadj capacitor (C75) as 47 nF. The LM3881 is powered using the 3.6-V TPS7A84 LDO. Keep the delay sufficiently large such that the tolerances of the capacitors do not make the second voltage override the first due to the soft start.

See the TPS54122 datasheet ([SLVSDC9](#)) and TPS54122 EVM user's guide ([SLVUAX8](#)) for the detailed design instructions and recommendations. See the Texas Instruments [WEBENCH Design Center](#) for generating solution using this part. The DC-DC converter equivalent part for the TPS54122 is the TPS54319, which can be used in webench for simulation.

Both the switcher and the LDO have independent protection and control features such as internal current limit, thermal shutdown, power good signal, and enable circuitry.

[图 6](#) shows the TPS54122 DC-DC + LDO combo circuit to generate 1.8 DVDD/1.8 AVDD from a 5.6-V input. The TPS54122 is designed to provide up to 2 A. With the TPS54122's flexibility of having a DC-DC converter and LDO in a single device, it is possible to obtain maximum LDO efficiency by setting LDO input just above dropout voltage. This demonstrates the PCB space saving compared to standalone switcher and LDO topologies. The TPS54122 device combines the efficiency of a step-down switching (DC-DC) converter with a high PSR, low-noise LDO to provide an ultra-low-noise power supply that delivers quiet supply rails. The LDO is kept 0.5 V for good PSRR with a DC-DC converter output of 2.3 V.

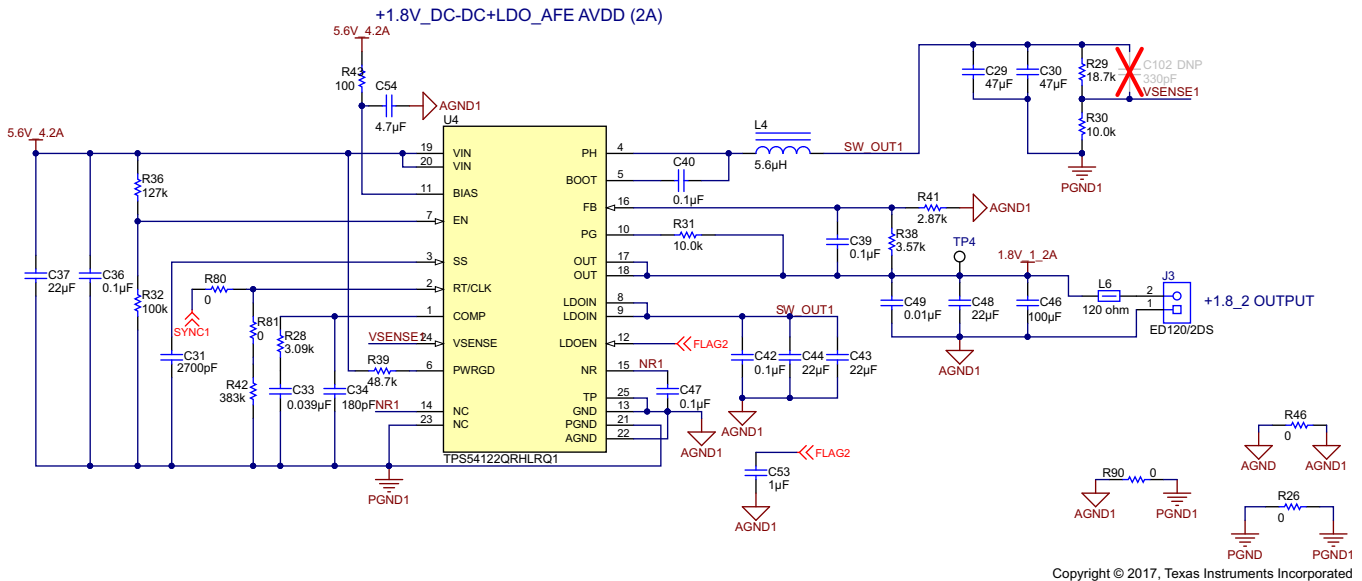


图 6. 1.8-V Generation Using TPS54122

2.3.3.7 DC-DC Converter Output Voltage Set Point

The switcher output voltage can be set using 公式 10:

$$R29 = R30 \times \left(\frac{V_{OUT}}{V_{REF}} - 1 \right) \quad (10)$$

Where:

- R29 = 18.7 kΩ
- R30 = 10 kΩ
- $V_{REF} = 0.827 \text{ V}$

Substituting R29, R30, and V_{REF} in 公式 10 gives:

$$V_{OUT} = (18.7 / 10 + 1) \times 0.827 = 2.37 \text{ V} \quad V_{OUT} = \left(\frac{18.7}{10} + 1 \right) \times 0.827 \text{ V} = 2.37 \text{ V}$$

2.3.3.8 LDO Output Voltage Set Point

The LDO output voltage can be set using 公式 11:

$$R38 = R41 \times \left(\frac{V_{OUT}}{V_{REF}} - 1 \right) \quad (11)$$

Where:

- R38 = 3.57 kΩ
- R41 = 2.87 kΩ
- $V_{REF} = 0.8 \text{ V}$

Substituting R38, R41, and V_{REF} in 公式 11 gives:

$$V_{OUT} = \left(\frac{3.57 \text{ k}\Omega}{2.87 \text{ k}\Omega} + 1 \right) \times 0.8 = 1.79$$

2.3.3.9 Adjustable Switching Frequency and Synchronization (RT/CLK)

In RT mode, the R42 (RT) resistor is connected between the RT/CLK pin and GND. The switching frequency of the device can be adjustable by using a resistor R42 (RT) of value, which ranges from 350 to 450 kΩ based on the inductor rating chosen for the DC-DC converter. To determine the value of the RT resistor for a given switching frequency (F_{sw}), use [公式 12](#).

$$R_T \text{ (k}\Omega\text{)} = 311890 \times F_{sw} \text{ (kHz)}^{-1.0793} \quad (12)$$

Where:

- $R_T = R42 = 383 \text{ k}\Omega$

Substituting $R_T = 383 \text{ k}\Omega$ in [公式 12](#) gives $F_{sw} = 500 \text{ kHz}$.

2.3.3.10 CLK Mode

In CLK mode, an external clock is connected through the clock buffer (U11) to the RT/CLK pin. The DC-DC converter is synchronized to the external clock frequency with an internal phase-locked loop (PLL) circuit. The DC-DC converter is able to automatically detect the required mode and switch from RT mode to CLK mode. CLK mode overrides RT mode. An internal PLL is implemented to allow synchronization between 300 kHz and 2 MHz and to easily switch from RT mode to CLK mode. To implement the synchronization feature, connect a square-wave clock signal to the RT/CLK pin with a minimum on-time of at least 75 ns. The clock signal amplitude must transition to less than 0.6 V and to greater than 1.6 V. The PH rising edge is synchronized to the RT/CLK pin falling edge. In applications where the RT mode and CLK mode are required, the device can be configured to have an RT resistor and an external clock connected at the same time to the RT/CLK pin. If no external clock is present, the device functions in RT mode and the switching frequency is set by the R42 (RT) resistor.

The EN pin of the 1.8-V LDO is connected to the output (Flag2) of LM3881 as per the sequencing requirement of AFE5818 mentioned in 节 2.3.6.


In this reference design, 0-Ω resistors R80 and R81 are used on board to select between RT/CLK mode. Placing R80 resistor sets external sync and placing R81 sets CLK mode

Both the switcher and the LDO have independent protection and control features such as soft start, internal current limit, thermal shutdown, power good signal, and enable circuitry.

See the TPS54122 datasheet (SLVSDC9) and TPS54122 EVM user's guide (SLVUAX8) for the detailed design instructions and recommendations. See the Texas Instruments WEBENCH Design Center for generating solution using this part. The DC-DC converter equivalent part for TPS54122 is TPS54319, which can be used in webench for simulation.

2.3.4 3.3-V Generation Using LDO

图 7 shows the LDO circuit to generate 3.3 V from a 3.6-V input using the TPS7A84. Two such circuits are used to provide the total 5-A requirement of eight AFEs. To have an optimal PSRR, 0.3-V LDO is set for the TPS7A83.

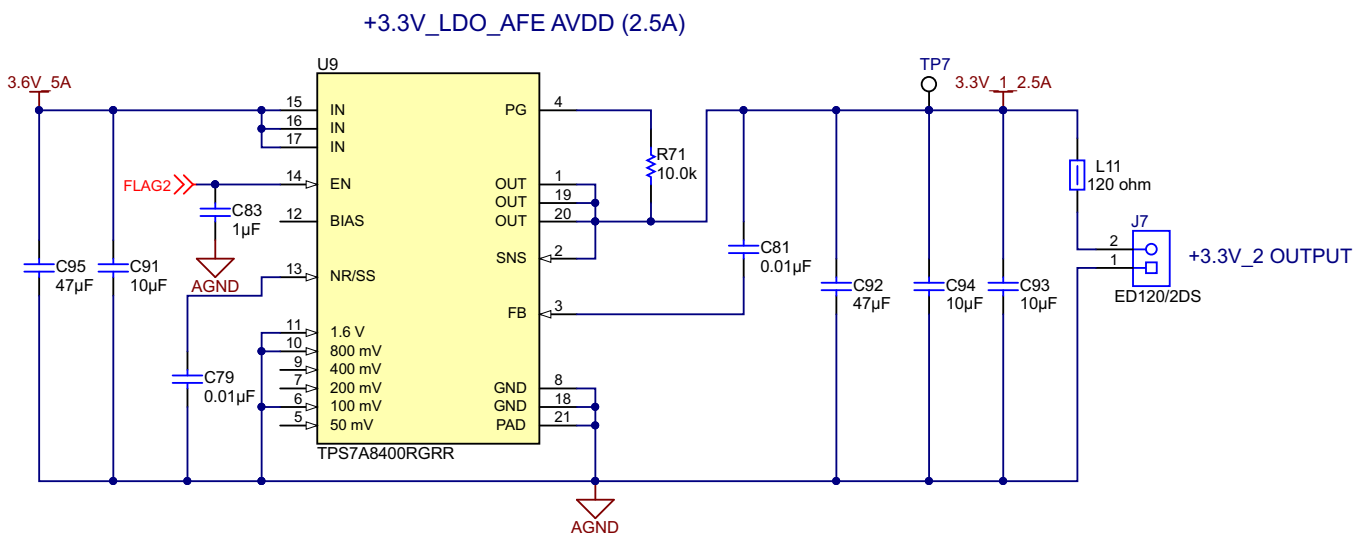

Copyright © 2017, Texas Instruments Incorporated

图 7. 3.3-V Generation Using TPS7A84

2.3.4.1 Output Voltage Set

The TPS7A84 can use either external resistors or the internally-matched ANY-OUT feedback resistor network to set output voltage. The ANY-OUT resistors are accessible through pin 2 and pins 5 to 11 and are used to program the regulated output voltage. Each pin is can be connected to ground (active) or left open (floating), or connected to SNS. ANY-OUT programming is set by 公式 13 as the sum of the internal reference voltage ($V_{NR} / SS = 0.8 \text{ V}$) plus the accumulated sum of the respective voltages assigned to each active pin. In this reference design 1.6 V (pin 11), 800 mV (pin 10), 100 mV (pin 6) plus V_{REF} of 0.8 V gives a 3.3-V output; the voltages at each pin are 50 mV (pin 5), 100 mV (pin 6), 200 mV (pin 7), 400 mV (pin 9), 800 mV (pin 10), or 1.6 V (pin 11). 表 3 summarizes these voltage values associated with each active pin setting for reference. By leaving all program pins open, or floating, the output is thereby programmed to the minimum possible output voltage equal to V_{REF} .

$$V_{OUT} = V_{REF} + (\varepsilon \text{ ANY OUT Pins to Ground}) \quad (13)$$

表 3. ANY OUT Programmable Output Voltage

PIN	VALUE
Pin 5	50 mV
Pin 6	100 mV
Pin 7	200 mV
Pin 9	400 mV
Pin 10	800 mV
Pin 11	1.6 V

There are several alternative ways to set the output voltage. The program pins can be driven using external general-purpose input/output pins (GPIOs), manually connected to ground using 0-Ω resistors (or left open), or hardwired by the given layout of the PCB to set the ANY-OUT voltage. Using the ANY-OUT network allows the TPS7A8300 to be programmed from 0.8 to 3.95 V. The EN pin of the 3.3-V LDO is connected to the output (Flag2) of the LM3881 as per the sequencing requirement of the AFE5818 mentioned in 节 2.3.6.

See the TPS7A84 datasheet ([SBVS233](#)) and TPS7A84 EVM ([SBVU028](#)) for detailed design instructions and recommendations. See the Texas Instruments [WEBENCH Design Center](#) for generating solution using this part.

2.3.5 5-V Generation Using LDO

图 8 shows the LDO circuit to generate 5 V from a 5.6-V input using the TPS7A83. To have an optimal PSRR, 0.6-V LDO is set for the TPS7A83.

2.3.5.1 Output Voltage Set

The TPS7A8300 can be used either with the internal ANY-OUT network or using external resistors. Using the ANY-OUT network allows the TPS7A8300 to be programmed from 0.8 to 3.95 V. To extend this range of output voltage operation to 5.0 V, external resistors must be used. 公式 14 shows how to set the output voltage in adjustable output operation.


$$R73 = R72 \times \left(\frac{V_{OUT}}{V_{REF}} - 1 \right) \quad (14)$$

Where:

- $V_{REF} = 0.8 \text{ V}$

- R73 = 105 kΩ
- R72 = 20 kΩ

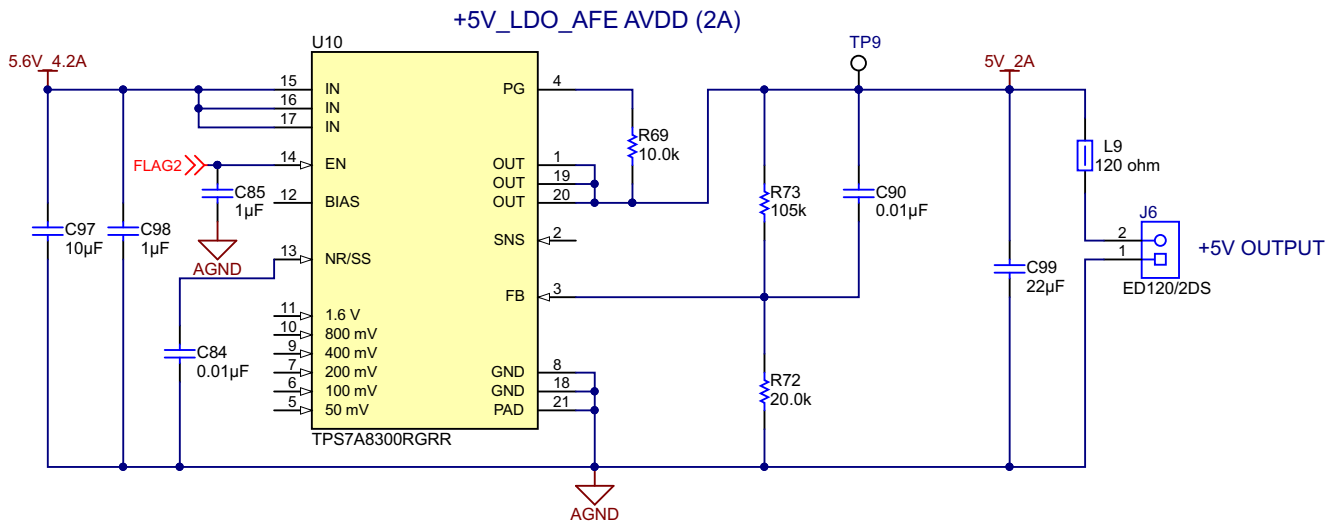Substituting V_{REF} , R73, and R72 in 公式 14 gives $V_{OUT} = 5\text{ V}$. The EN pin of the 5-V LDO is connected to the output (Flag2) of the LM3881 as per the sequencing requirement of the AFE5818 mentioned in 节 2.3.6.




Copyright © 2017, Texas Instruments Incorporated

图 8. 5-V Generation Using TPS7A83

See the TPS7A83 datasheet (SBVS197) and TPS7A83 EVM (SLVU919) for detailed design instructions and recommendations. See the Texas Instruments WEBENCH Design Center for generating solution using this part.

2.3.6 Power Sequencer and 3.3-V Generation for Power Sequencer

图 9 shows the power sequencing circuit for the power supplies of this reference design using the LM3881.

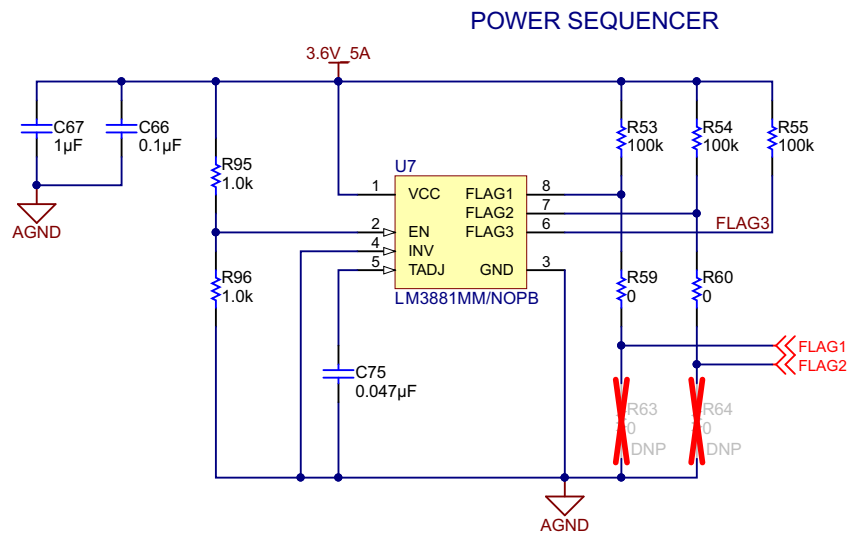


Copyright © 2017, Texas Instruments Incorporated

图 9. Power Sequencing Circuit

The requirements for power sequencing the AFE5818 is as shown in 图 10:

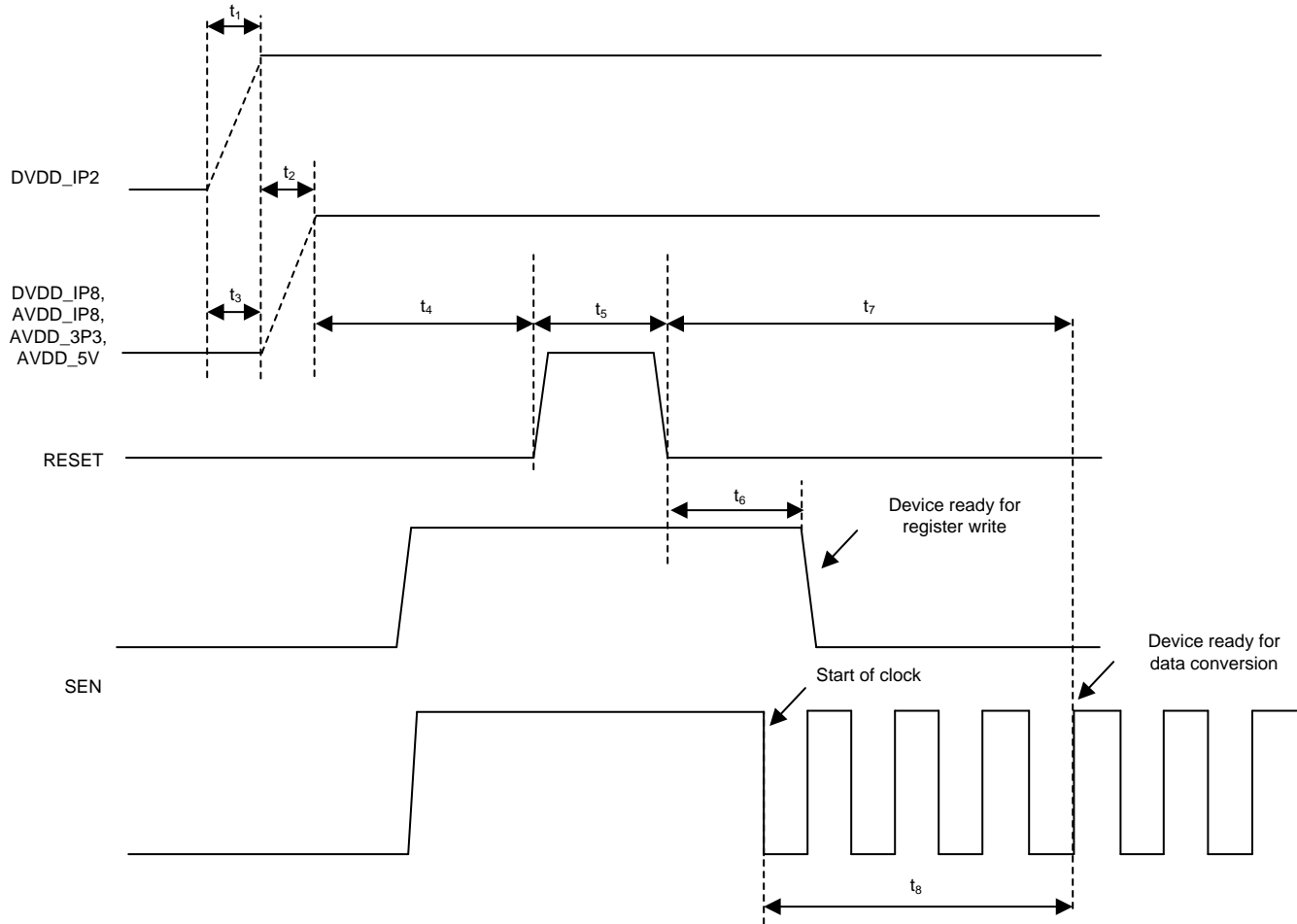- The DVDD_1.2V supply must rise before the AVDD_1.8V supply.
- If the AVDD_1.8V supply rises before the DVDD_1.2V supply, the AVDD_1.8V supply current is 8 to 12 times larger than the normal current until the DVDD_1.2V supply reaches a 1.2-V level.



Note: $10\ \mu\text{s} < t_1 < 50\ \text{ms}$, $10\ \mu\text{s} < t_2 < 50\ \text{ms}$, $t_3 > t_1$, $t_4 > 10\ \text{ms}$, $t_5 > 100\ \text{ns}$, $t_6 > 100\ \text{ns}$, $t_7 > 4$ ADC clock cycles, and $t_8 > 100\ \mu\text{s}$

图 10. Power Sequencing of AFE5818

In this reference design, the delay between 1.2 V and all other rails (1.8 AVDD, 1.8 DVDD, 5 AVDD, 3.3 AVDD) is set as 50 ms by choosing the Tadj capacitor (C75) as 47 nF. The LM3881 is powered using a 3.6-V TPS7A84 LDO. Keep the delay sufficiently large such that the tolerances of the capacitors do not make the second voltage override the first due to the soft start. See the LM3881 datasheet (SNVS555) and LM3881 EVM (SNVA322) for design details. See the Texas Instruments WEBENCH Design Center for generating solution using this part.

2.3.7 Clock Buffer and 3.3-V Generation

图 11 shows the clock signal fan out buffer using the CDCLVC1106, a 1:6, 3.3-V LVCMOS, high-performance, low-skew, general purpose clock buffer that supports frequencies up to 180 MHz. In an ultrasound system, the switching frequencies are in the range of 100 to 500 kHz, hence the CDCLVC1106 is selected for this reference design. It is recommended to place 15-Ω series resistors close to the driver to minimize signal reflection.

See the CDCLVC1106 datasheet (SCAS895) and CDCLVC1106 EVM (SCAU041) for detailed information.

图 12 shows the circuit to generate the 3.3-V supply for the CDCLVC1106 using the LDO TLV70433.

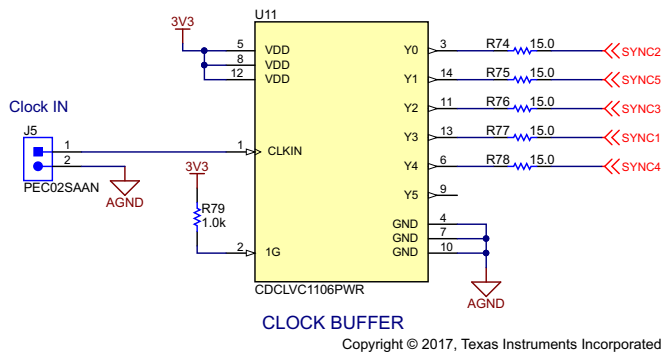


图 11. Clock Signal Fan Out Buffer

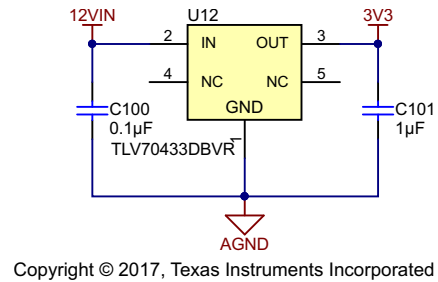


图 12. 3.3-V Generation

See the TLV70433 datasheet (SBVS148) for more details.

2.3.8 eFUSE

图 13 shows the eFuse circuit for this reference design using the TPS259260, a 12-V eFuse protection switch.

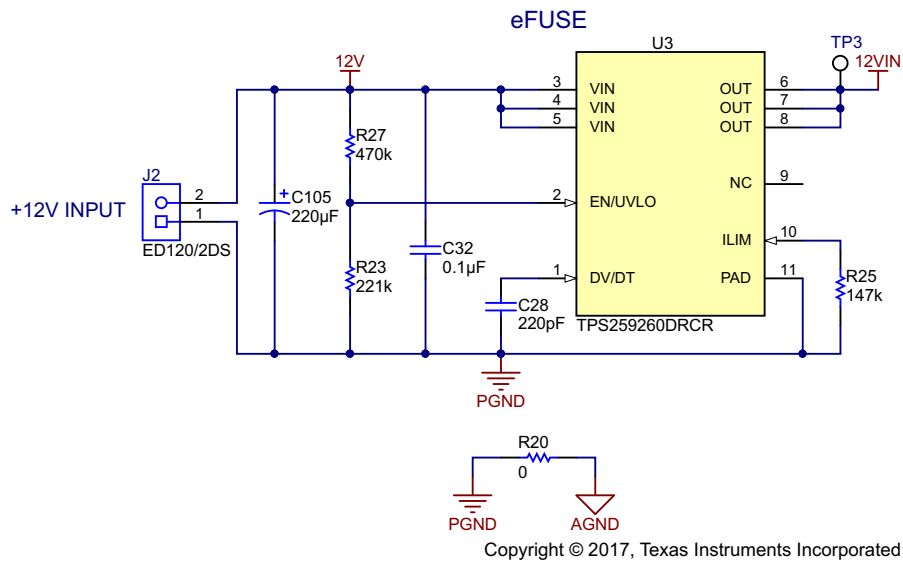


图 13. eFUSE Circuit for TIDA-01466

2.3.8.1 ILIM

The device continuously monitors the load current and keeps it limited to the value programmed by R_{ILIM} . After start-up event and during normal operation, current limit is set to I_{OL} (overload current limit). ILIM can be calculated using 公式 15:

$$I_{OL} = 0.7 + 3 \times 10^{-5} (R_{ILIM}) \quad (15)$$

Where:

- $R_{ILIM} = 147 \text{ k}\Omega$

Substituting R_{ILIM} in 公式 15 gives $I_{OL} = 4.2 \text{ A}$.

2.3.8.2 UVLO Set Point

The UVLO trip point is adjusted using the external voltage divider network of R27 and R23 as connected between IN, EN/UVLO, and GND pins of the device. UVLO can be calculated using 公式 16:

$$V_{UR} = \frac{R27 + R23}{R23} \times V_{ENR} \quad (16)$$

Where:

- $V_{ENR} = 1.4 \text{ V}$
- $R27 = 470 \text{ k}\Omega$
- $R23 = 221 \text{ k}\Omega$

Substituting V_{ENR} , R27, and R23 in 公式 16 gives $V_{UR} = 4.37 \text{ V}$.

2.3.8.3 Setting Output Voltage Ramp Time ($T_{dV/dT}$)

The total ramp time ($T_{dV/dT}$) for 0 to V_{IN} can be calculated using 公式 17:

$$T_{dV/dT} = 10^{16} \times V_{IN} \times (C_{dV/dT} + 70 \text{ pF}) \quad (17)$$

Where:

- $V_{IN} = 12 \text{ V}$
- $C_{dV/dT} = C28 = 220 \text{ pF}$

Substituting V_{IN} , $C_{dV/dT}$ in 公式 17 gives $T_{dV/dT} = 3.26 \text{ ms}$.

2.3.8.4 Inrush Current (I_{INRUSH}) Setting

Inrush current can be set using 公式 18:

$$I_{INRUSH} = \frac{C_{OUT} \times V_{IN}}{T_{dV/dT}} \quad (18)$$

Where:

- $C_{OUT} = 100 \text{ }\mu\text{F}$ (total output capacitance)
- $V_{IN} = 12 \text{ V}$
- $T_{dV/dT} = 3.26 \text{ ms}$

Substituting C_{OUT} , V_{IN} , and $T_{dV/dT}$ in 公式 18 gives $I_{INRUSH} = 0.37 \text{ A}$. See the TPS259260 datasheet (SLVSCQ3) and design calculator for more details.

3 Hardware, Testing Requirements, and Test Results

3.1 Required Hardware

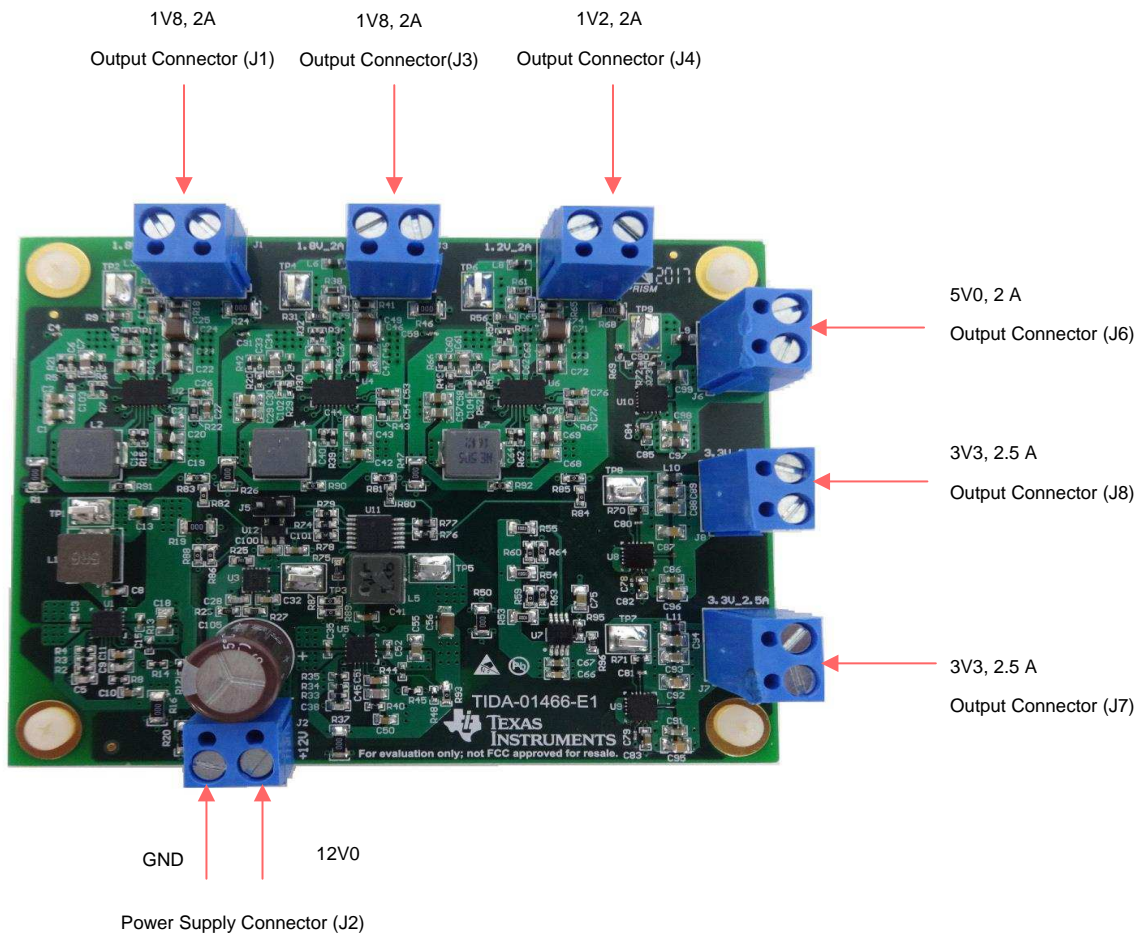


图 14. TIDA-01466 PCB Connectors

表 4. TIDA-01466 Connector Description

SIGNAL	CONNECTOR	FUNCTION
+12V Input	J2	This pin is used to connect the input power supply. Set power supply to 12 V with a 5-A current limit.
Clock IN	J5	Clock IN for sync mode operation
+1.8V_1 Output	J1	1.8-V_1, 2-A output connector
+1.8V_2 Output	J3	1.8-V_2, 2-A output connector
+1.2V_2 Output	J4	1.2-V, 2-A output connector
+3.3V_1 Output	J8	3.3-V_1, 2.5-A output connector
+3.3V_2 Output	J7	3.3-V_2, 2.5-A output connector
+5V Output	J6	5-V, 2-A output connector

3.2 Testing and Results

3.2.1 Test Setup

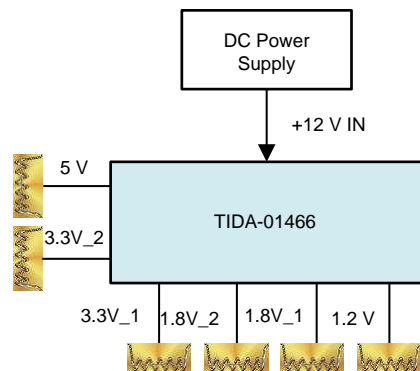


图 15. TIDA-01466 Test Setup

图 15 显示了参考设计的负载测试和纹波测量的测试设置。以下测试是在使用此测试设置的情况下进行的，以评估参考设计。

3.2.1.1 Load Regulation

在此测试中，加热器灯丝用作每个输出的负载电阻器，并观察输出电压。在空载和满载条件下。负载调节率按公式 19 计算，表 5 显示了用于每个电压输出的电阻器的值。请参阅节 3.2.2 以获取测试结果。


$$\text{Load regulation (\%)} = \frac{(V_{NL} - V_{FL})}{V_{FL}} \times 100 \quad (19)$$

表 5. Load Resistors

OUTPUT VOLTAGES	LOADS (Ω)
5 V	2.50
3.3 V_1	1.32
3.3 V_2	1.32
1.8 V_1	0.90
1.8 V_2	0.90
1.2 V	0.60

3.2.1.2 Output Ripple Measurement

图 16 显示了用于测量输出电压纹波的测试设置。测量是使用 PXA Signal Analyzer N9030B 3 Hz 到 44 GHz 在 dBm 下进行的。请参阅节 3.2.2 以获取测试结果。

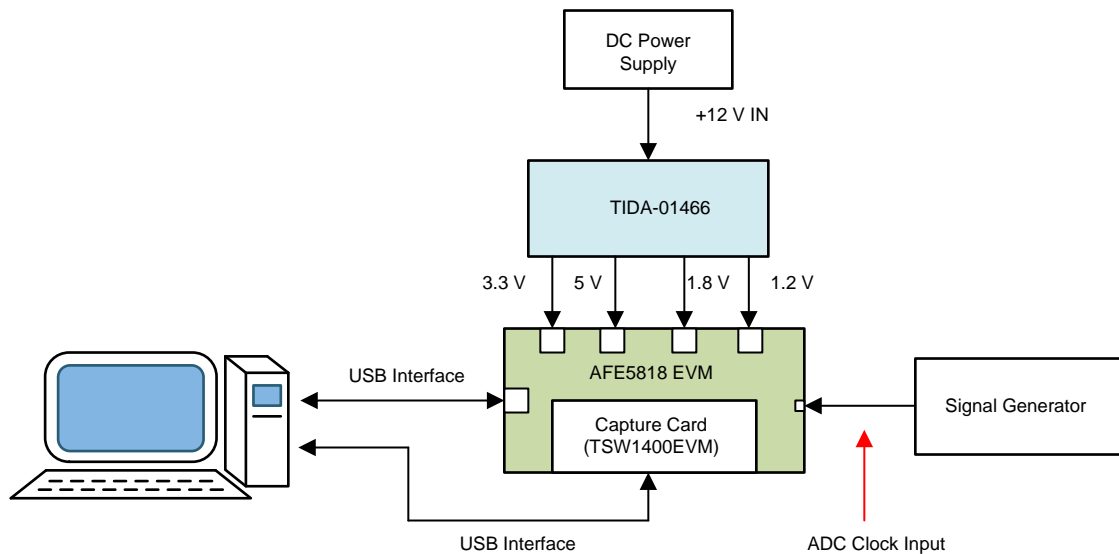

Copyright © 2017, Texas Instruments Incorporated

图 16. TIDA-01466 Test Setup For Test With AFE Integrated

图 16 shows the test setup to evaluate the performance of TI AFE AFE5818 EVM using this reference design. Following test was conducted to evaluate the performance.

3.2.1.3 Test With AFE Integrated

This test evaluates the performance of AFE5818 EVM using this reference design. The test is conducted by disconnecting the onboard EVM power supplies (linear regulators) and by connecting the reference design supplies. Tests are carried out in both TGC and CW mode. In TGC mode, the test is conducted to mimic the beam forming feature of the AFE5818 in the system by coherently summing the outputs of all the 16 channels. These results are averaged and FFT is taken to evaluate the correlated noise. There is no difference observed in the test results between the onboard AFE5818 EVM power supply and the reference design. In this test, 60M clock is used for the AFE ADC provided by the signal generator SG382 and the coherently sampled results are taken. In this test, AFE5818 EVM is controlled using HMC-DAQ GUI. The TSW1400 EVM is also required for capturing data from the AFE5818 EVM and its analysis using the graphical user interface (GUI), called High Speed Data Converter Pro (HSDCPro). The USB connections from the AFE5818 EVM and TSW EVM to the PC are used for communication from the GUIs to the boards. The TSW1400EVM is a complete pattern generator and data capture circuit board used to evaluate most of Texas Instruments' high speed ADCs and DACs. The TSW1400EVM features a high-speed LVDS bus capable of providing 16 bits of data at 1.5 GSPS. The board comes with 1GB of memory, which provides a 16-bit sample depth of 512 MB. This improved memory enables better FFT frequency resolution and larger capture sizes for more realistic tests. HSDC PRO GUI is an easy-to-use GUI that allows users to conduct time domain tests, single- or multiple-tone frequency tests, and even load their own test patterns. See the AFE5818 EVM and TSW1400 EVM for more details.

In CW Mode, summing amplifier output was measured using the signal analyzer PXA Signal Analyzer N9030B 3 Hz to 44 GHz. This test is carried out with an input signal of 15 kHz, 4 dBm. See 节 3.2.2 for test results.

3.2.2 Test Results

3.2.2.1 LDO Output Voltage Spectrum: 1.8 V, 1.2 V, 3.3 V, and 5 V

图 17 shows the output voltage noise spectrum for the TPS54122 with LDO $V_{OUT} = 1.8\text{ V}$, SW OUT = 2.3 V, $V_{IN} = 5.6\text{ V}$. The max peak is -50.23 dBm at 480 kHz with a 2-A load.

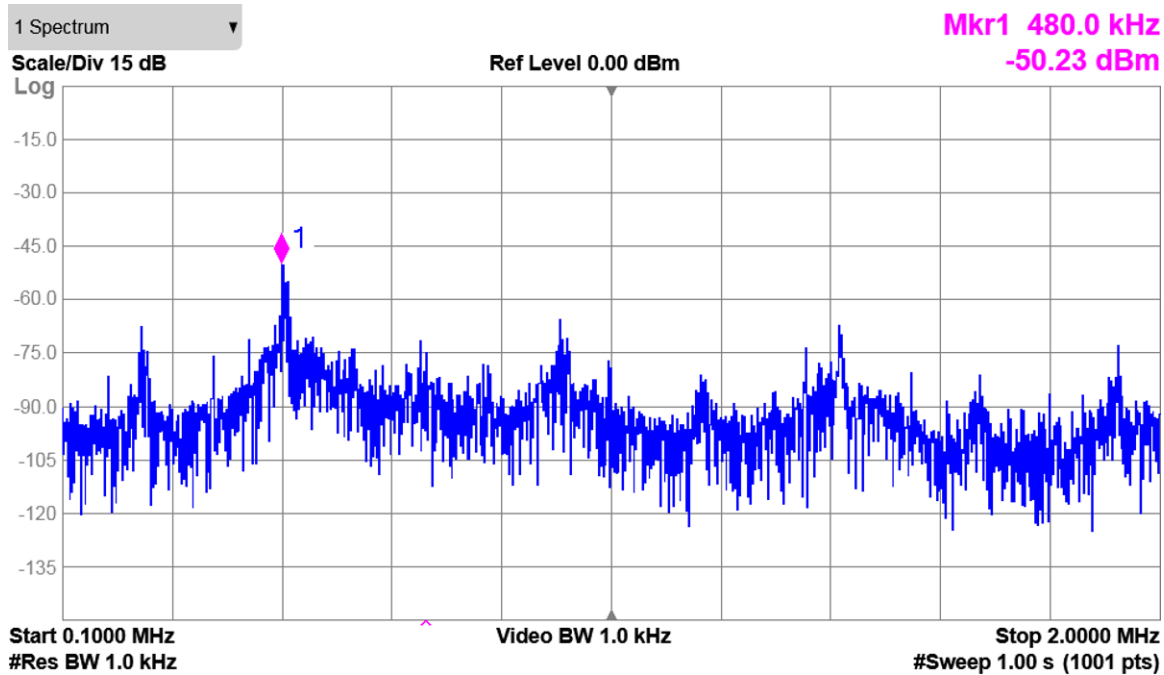


图 17. Output Voltage Spectrum of TPS54122 With LDO $V_{OUT} = 1.8\text{ V}$, 2-A Load, -50.23 dBm Max Peak at 476 kHz

图 18 shows the output voltage noise spectrum for the TPS54122 with LDO $V_{OUT} = 1.2\text{ V}$, SW OUT = 1.7 V, $V_{IN} = 5.6\text{ V}$. The max peak is -60.47 dBm at 476 kHz with a 2-A load.

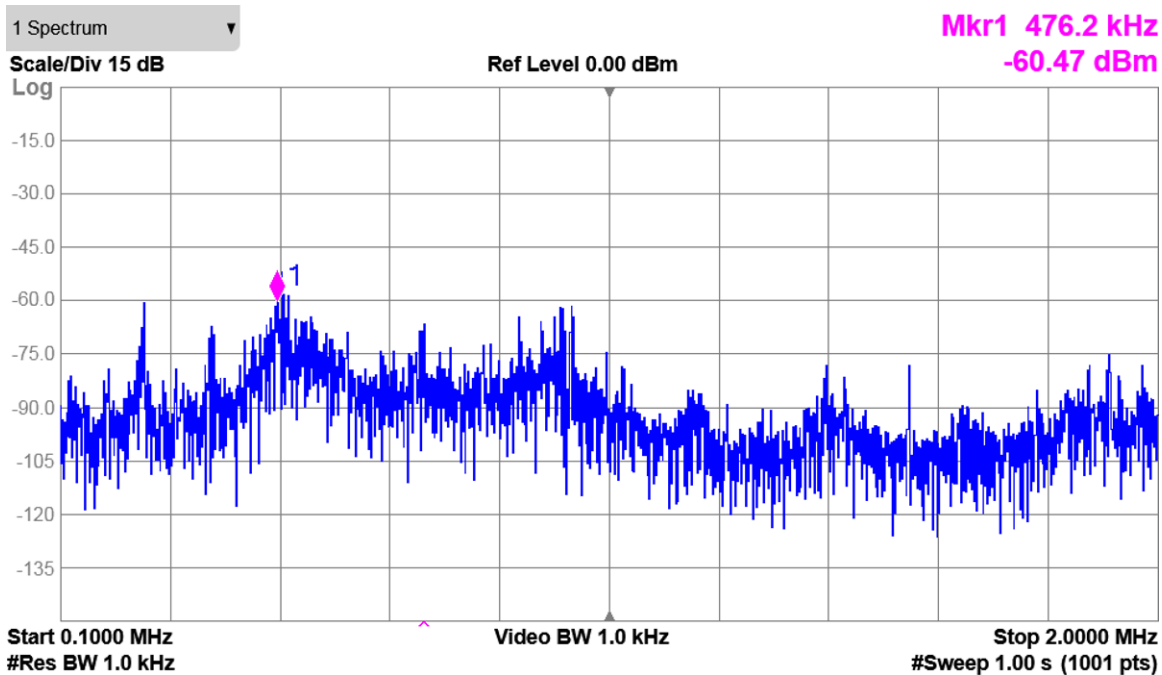


图 18. Output Voltage Spectrum of TPS54122 With LDO $V_{OUT} = 1.2$ V, 2-A Load, -60 dBm Max Peak at 476 kHz

图 19 shows the output voltage noise spectrum for the TPS7A84 with LDO $V_{OUT} = 3.3$ V, $V_{IN} = 3.6$ V. The max peak is -73.23 dBm at 524 kHz with a 2.5-A load.

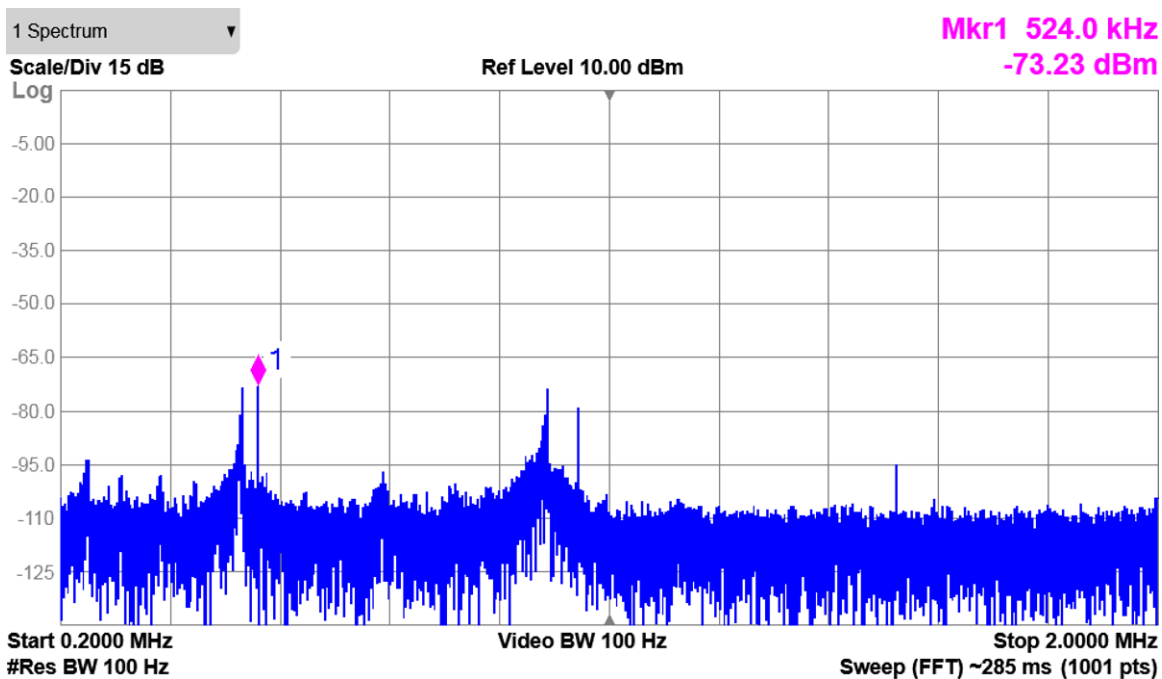


图 19. Output Voltage Spectrum of TPS7A84 With LDO $V_{OUT} = 3.3$ V, 2.5-A Load, -73.23 dBm Max Peak at 524 kHz

图 20 shows the output voltage noise spectrum for the TPS7A83 with LDO $V_{OUT} = 5$ V, $V_{IN} = 5.6$ V. The max peak is -60 dBm at 524 kHz with a 2-A load.

 


图 20. Output Voltage Spectrum of TPS7A83 With LDO $V_{OUT} = 5\text{ V}$, 2-A Load, -60 dBm Max Peak at 524 kHz

3.2.2.2 Load Regulation

表 6 shows the load regulation of this reference design.

表 6. Load Regulation of TIDA-01466 Power Supplies

OUTPUT VOLTAGES	NO LOAD VOLTAGES (V)	FULL LOAD VOLTAGES (V)	LOAD REGULATION
1.8 V_1	1.811	1.797	0.780%
1.8 V_2	1.811	1.798	0.723%
1.2 V	1.228	1.217	0.900%
5 V	4.972	4.970	0.040%
3.3 V_1	3.297	3.294	0.091%
3.3 V_2	3.301	3.299	0.060%

3.2.2.3 Test Results With AFE5818 Integrated (For TGC and CW Mode)

3.2.2.3.1 In TGC Mode

图 21 shows the AFE5818 EVM test result for TGC Mode with total gain of 42, and the calculated SNR is 70.12. With the AFE5818 EVM onboard power supply, SNR is 70.95. Gain settings of the TGC Mode are as shown in 表 7.

表 7. TGC Mode Gain Settings

LNA	ATTN	PGA	TOTAL GAIN
18	0	24	42

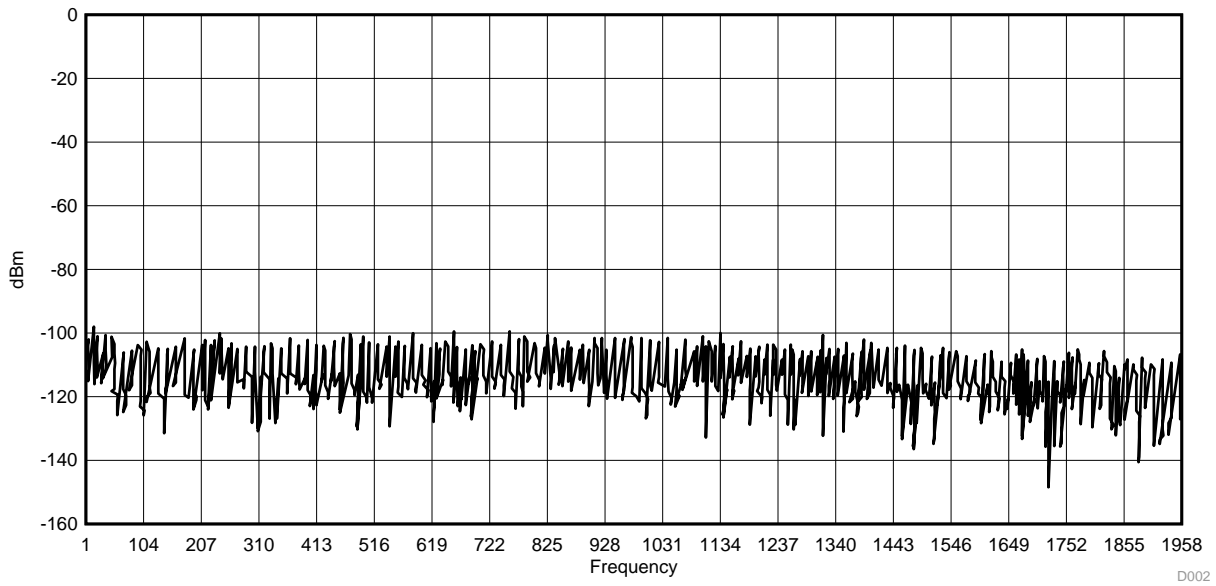


图 21. AFE TGC Path Result With Total Gain of 42, SNR = 70.12

3.2.2.3.2 In CW Mode

图 22 shows the CW summing amplifier output measured using signal analyzer. The input signal used for this test is a 15-kHz, -4-dBm sine wave. First and second harmonic are -96.7 dBm and -77.8 dBm, respectively.

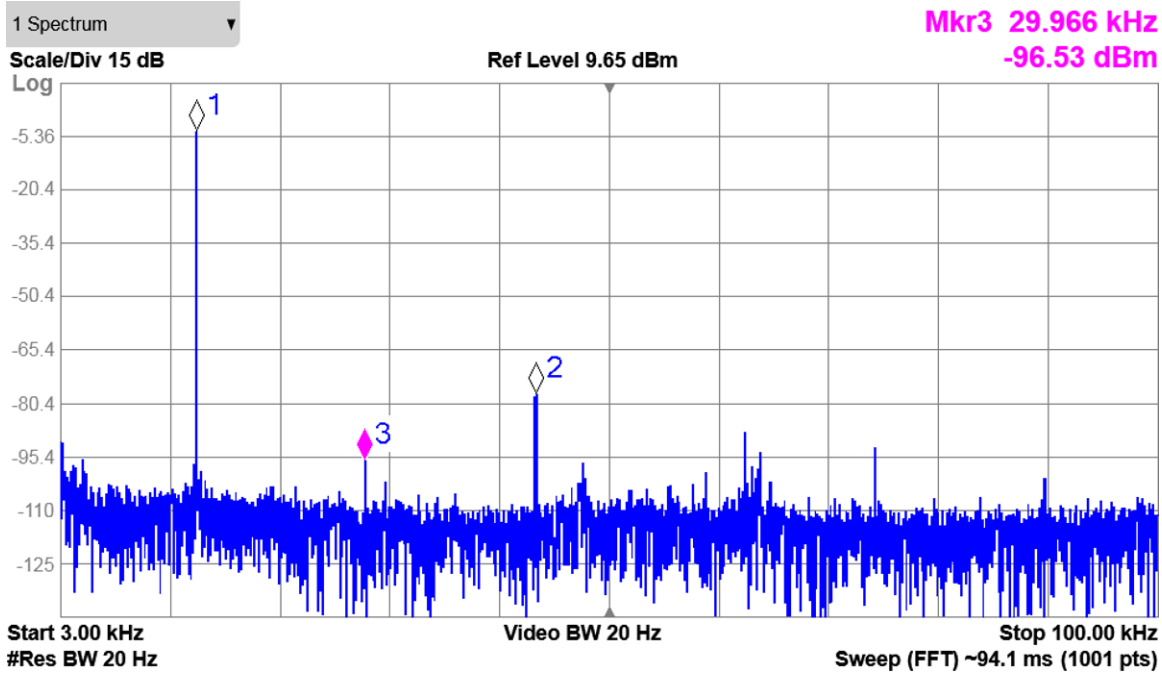


图 22. AFE5818 CW Summer Output With TIDA-01466 Integrated; First Harmonic = -96.7 dBm, Second Harmonic = -77.8 dBm

3.2.2.4 Power Sequencing

图 23 shows the power sequencing of this reference design with regards to 1.2 V and 1.8 V. All other output voltages appear at the same instant as 1.8 V. There is a 50-ms delay between 1.2 V and all other voltage rails.

 


图 23. Delay Between 1.2 V and 1.8 V is 50 ms, Soft Start is 100 ms

3.2.2.5 Thermal Shot

图 24 显示了此参考设计在满载条件下的热成像图。测量的最高温度为 76.5°C。

 


图 24. TIDA-01466 Thermal Shot

4 Design Files

4.1 Schematics

To download the schematics, see the design files at [TIDA-01466](#).

4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01466](#).

4.3 PCB Layout Recommendations

4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01466](#).

4.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01466](#).

4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01466](#).

4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01466](#).

5 Software Files

To download the software files, see the design files at [TIDA-01466](#).

6 Related Documentation

1. Texas Instruments, [AFE5818 16-Channel Analog Front End Evaluation Module \(EVM Rev. C\)](#), User's Guide (SLOU430)
2. Texas Instruments, www.ti.com/tool/TSW1400EVM

6.1 商标

QuietSupply, HotRod, MSP430 are trademarks of Texas Instruments.
WEBENCH is a registered trademark of Texas Instruments.
All other trademarks are the property of their respective owners.

7 About the Author

LENI SKARIAH is a systems engineer at Texas Instruments, where she is responsible for developing subsystem design solutions for the Medical, Healthcare and Fitness sector. Leni brings her experience in precision analog and mixed signal designs to this role. Leni earned her bachelor of technology in electronics and communication engineering from the University of Kannur and her master of technology in digital electronics and communication systems from Visvesvaraya Technological University, Karnataka.

有关 TI 设计信息和资源的重要通知

德州仪器 (TI) 公司提供的技术、应用或其他设计建议、服务或信息，包括但不限于与评估模块有关的参考设计和材料（总称“TI 资源”），旨在帮助设计人员开发整合了 TI 产品的应用；如果您（个人，或如果是代表贵公司，则为贵公司）以任何方式下载、访问或使用了任何特定的 TI 资源，即表示贵方同意仅为该等目标，按照本通知的条款进行使用。

TI 所提供的 TI 资源，并未扩大或以其他方式修改 TI 对 TI 产品的公开适用的质保及质保免责声明；也未导致 TI 承担任何额外的义务或责任。TI 有权对其 TI 资源进行纠正、增强、改进和其他修改。

您理解并同意，在设计应用时应自行实施独立的分析、评价和判断，且应全权负责并确保应用的安全性，以及您的应用（包括应用中使用的 TI 产品）应符合所有适用的法律法规及其他相关要求。您就您的应用声明，您具备制订和实施下列保障措施所需的一切必要专业知识，能够 (1) 预见故障的危险后果，(2) 监视故障及其后果，以及 (3) 降低可能导致危险的故障几率并采取适当措施。您同意，在使用或分发包含 TI 产品的任何应用前，您将彻底测试该等应用和该等应用所用 TI 产品的功能。除特定 TI 资源的公开文档中明确列出的测试外，TI 未进行任何其他测试。

您只有在为开发包含该等 TI 资源所列 TI 产品的应用时，才被授权使用、复制和修改任何相关单项 TI 资源。但并未依据禁止反言原则或其他法律授予您任何 TI 知识产权的任何其他明示或默示的许可，也未授予您 TI 或第三方的任何技术或知识产权的许可，该等产权包括但不限于任何专利权、版权、屏蔽作品权或与使用 TI 产品或服务的任何整合、机器制作、流程相关的其他知识产权。涉及或参考了第三方产品或服务的信息不构成使用此类产品或服务的许可或与其相关的保证或认可。使用 TI 资源可能需要您向第三方获得对该等第三方专利或其他知识产权的许可。

TI 资源系“按原样”提供。TI 兹免除对 TI 资源及其使用作出所有其他明确或默示的保证或陈述，包括但不限于对准确性或完整性、产权保证、无复发故障保证，以及适销性、适合特定用途和不侵犯任何第三方知识产权的任何默认保证。

TI 不负责任何申索，包括但不限于因组合产品所致或与之有关的申索，也不为您辩护或赔偿，即使该等产品组合已列于 TI 资源或其他地方。对因 TI 资源或其使用引起或与之有关的任何实际的、直接的、特殊的、附带的、间接的、惩罚性的、偶发的、从属或惩戒性损害赔偿，不管 TI 是否获悉可能会产生上述损害赔偿，TI 概不负责。

您同意向 TI 及其代表全额赔偿因您不遵守本通知条款和条件而引起的任何损害、费用、损失和/或责任。

本通知适用于 TI 资源。另有其他条款适用于某些类型的材料、TI 产品和服务的使用和采购。这些条款包括但不限于适用于 TI 的半导体产品 (<http://www.ti.com/sc/docs/stdterms.htm>)、[评估模块](http://www.ti.com/sc/docs/sampters.htm)和样品 (<http://www.ti.com/sc/docs/sampters.htm>) 的标准条款。

邮寄地址：上海市浦东新区世纪大道 1568 号中建大厦 32 楼，邮政编码：200122
Copyright © 2017 德州仪器半导体技术（上海）有限公司