


# Patient monitoring 101: Part-3

## Key considerations for designing electrocardiogram (ECG) front-end circuit

Prepared by: Ryan Andrews


# Typical ECG system

## Block diagram – 1 Lead

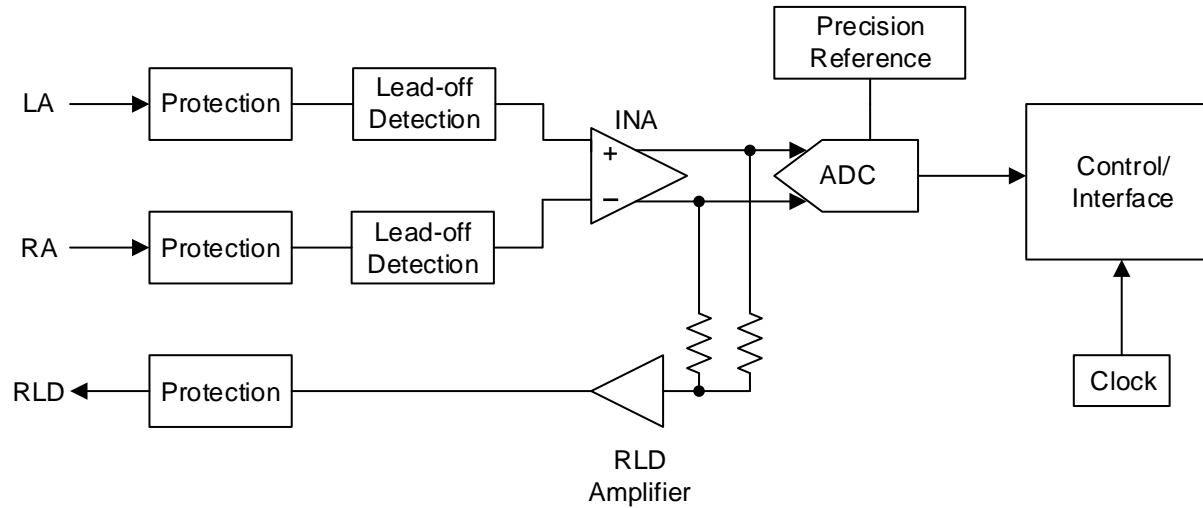


# Typical ECG system

## Block diagram – 3 Leads

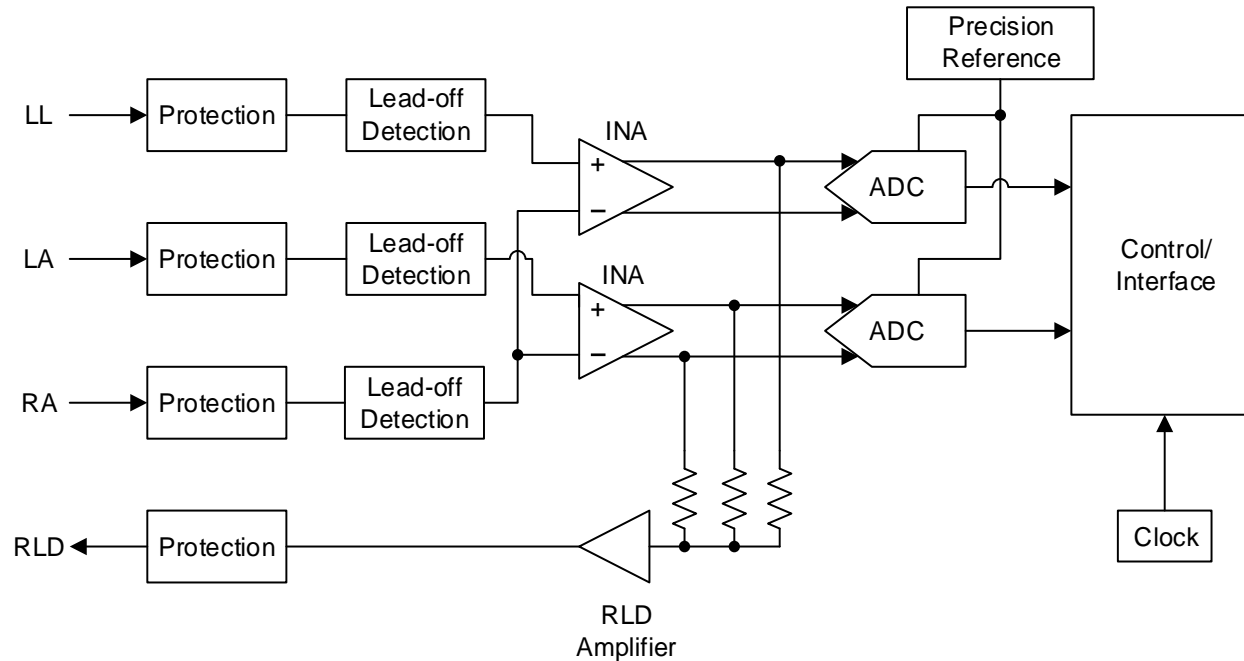


# Typical ECG system

## Block diagram – 12 Leads

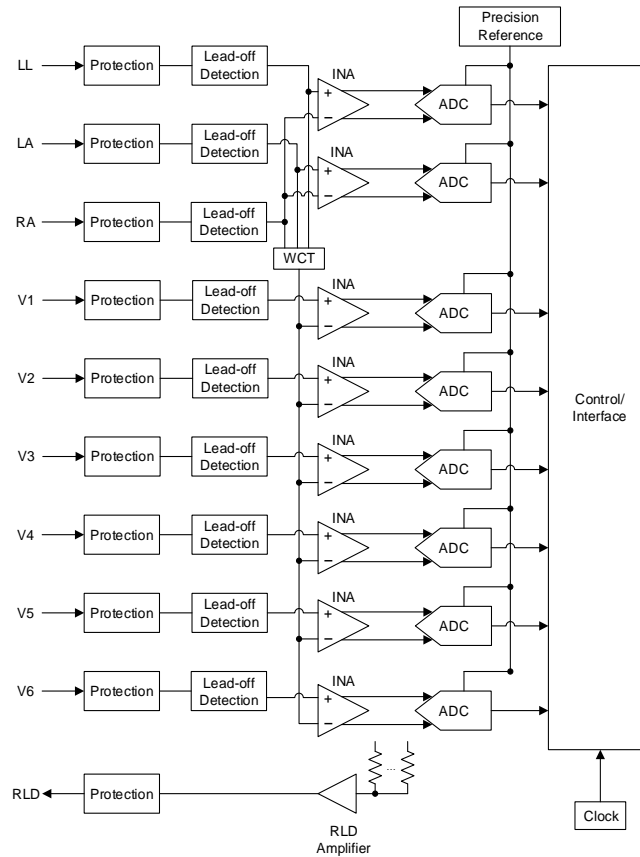


# Input filtering and protection

## Example: Lead I

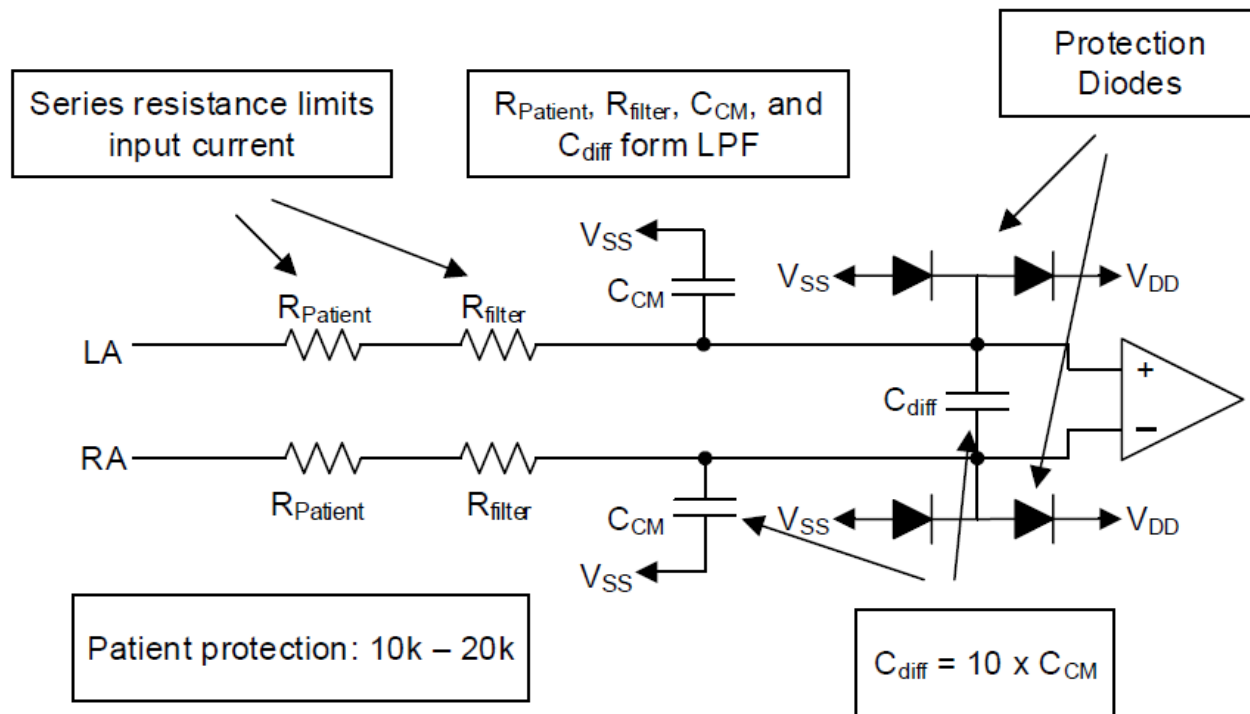


# Input filtering and protection

## Example: Lead I, AC-coupled

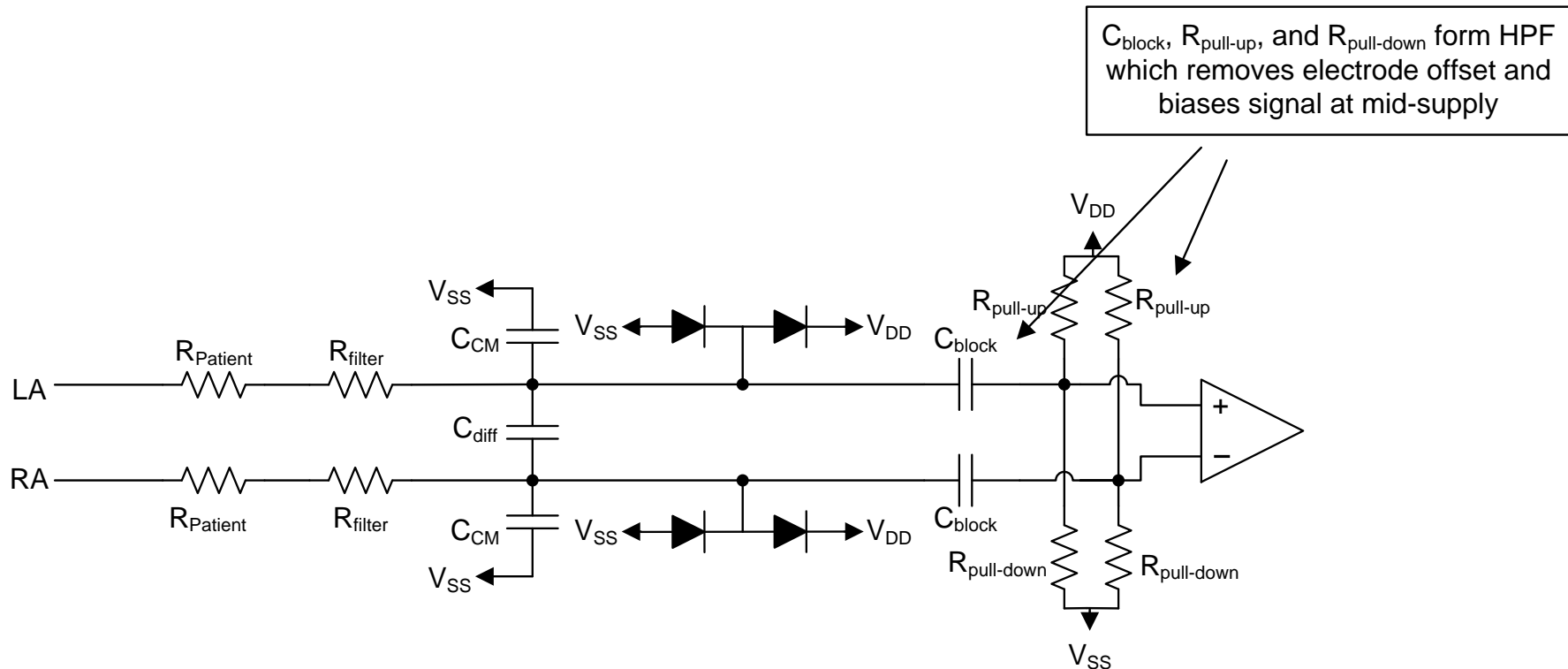

# Input filtering and protection

## Example: Lead I, AC-coupled

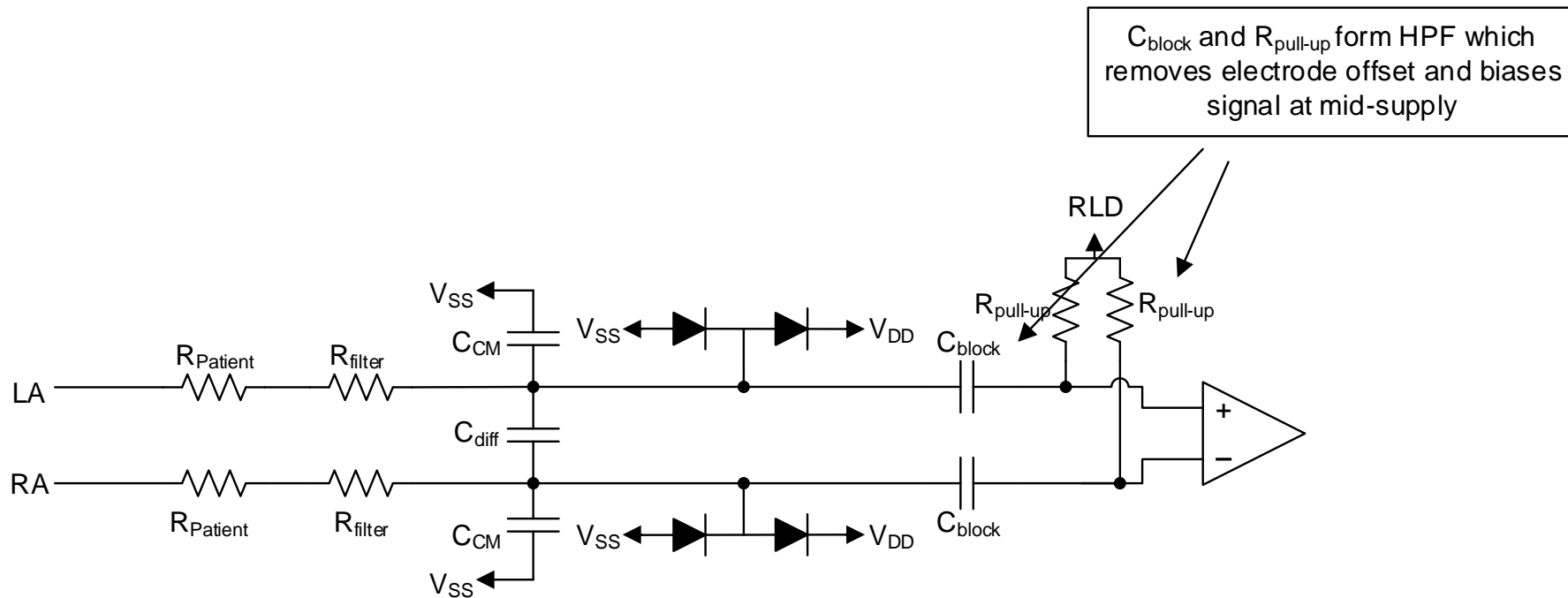


# INA front end

## Key features
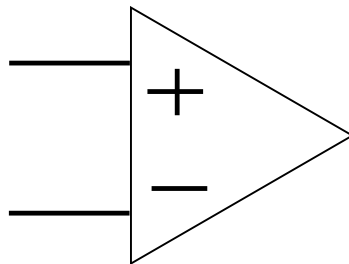
### Important

- Input Bias Current
- Input Impedance
- Input Current Noise
- Input Voltage Noise
- Power Consumption
- DC/AC CMRR




### Less Important

- Input Offset Voltage
- Input Offset Voltage Drift
- Gain Error
- Nonlinearity
- PSRR

DC errors such as offset error are small compared to the offsets introduced by the **skin-electrode** contacts



# Common-mode rejection in ECG front end

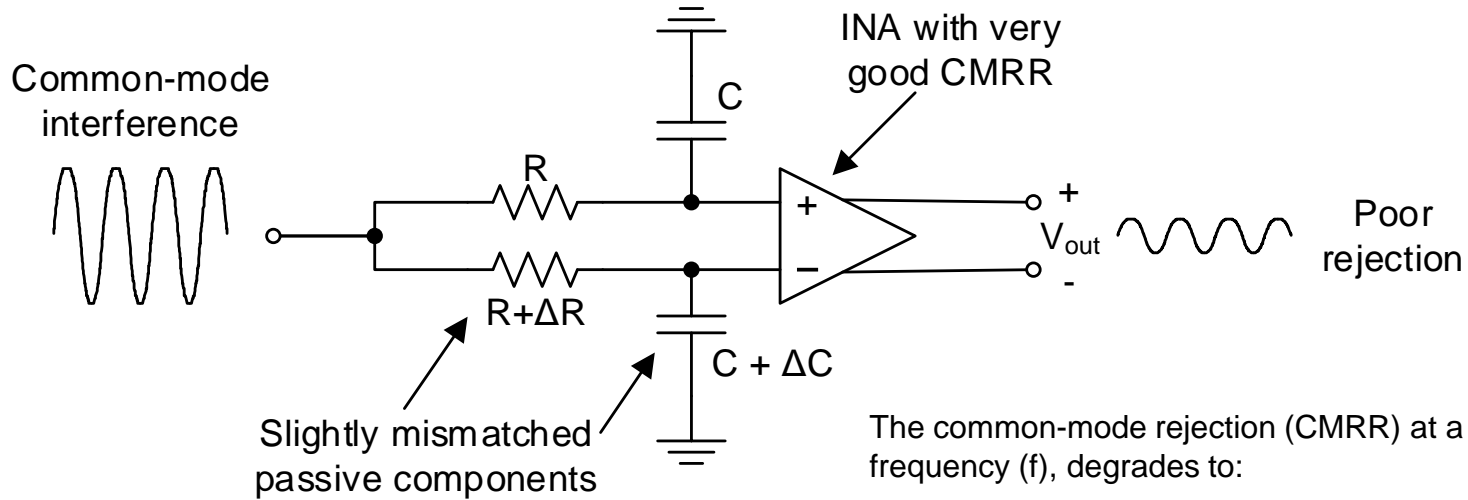

The common-mode rejection (CMRR) at a given frequency ( $f$ ), degrades to:

$$\text{CMRR} = 20 \times \log_{10} \left( \frac{\Delta R}{R} + \frac{\Delta C}{C} \right) + 20 \times \log_{10} \left( \frac{f}{f_c} \right)$$


where  $f_c$  is the designed filter cutoff.

# The RLD amplifier

Purpose of RLD amplifier is to:

- Bias the patient to the proper voltage range
- Cancel common-mode interference


$$\text{RLD Amp Output} = -\frac{Z_f}{R_i} (RA + LA)$$

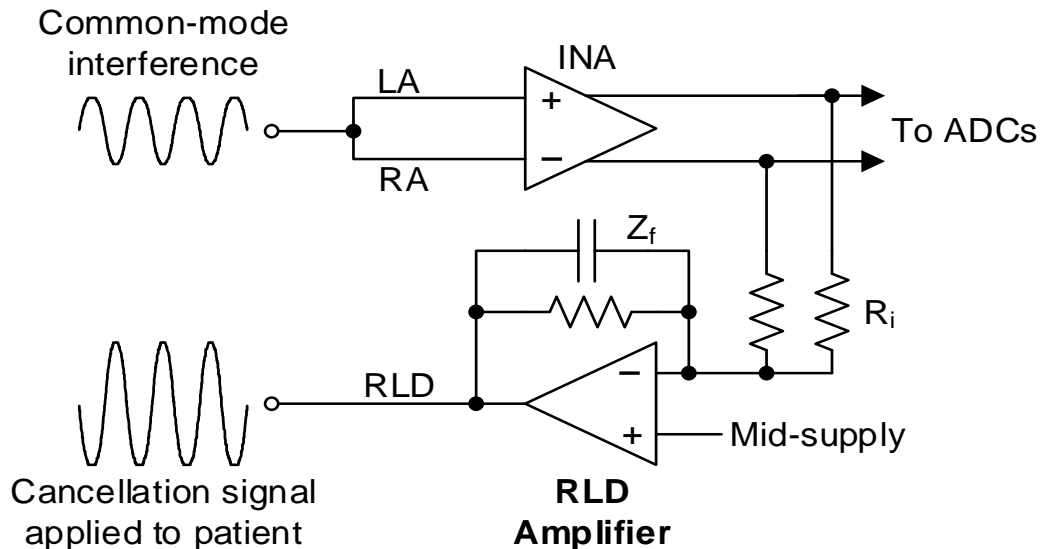

**SBAA188:** [Improving Common-Mode Rejection Using the Right-Leg Drive Amplifier](#)


# DC lead-off detection

Detect if *electrode* is disconnected

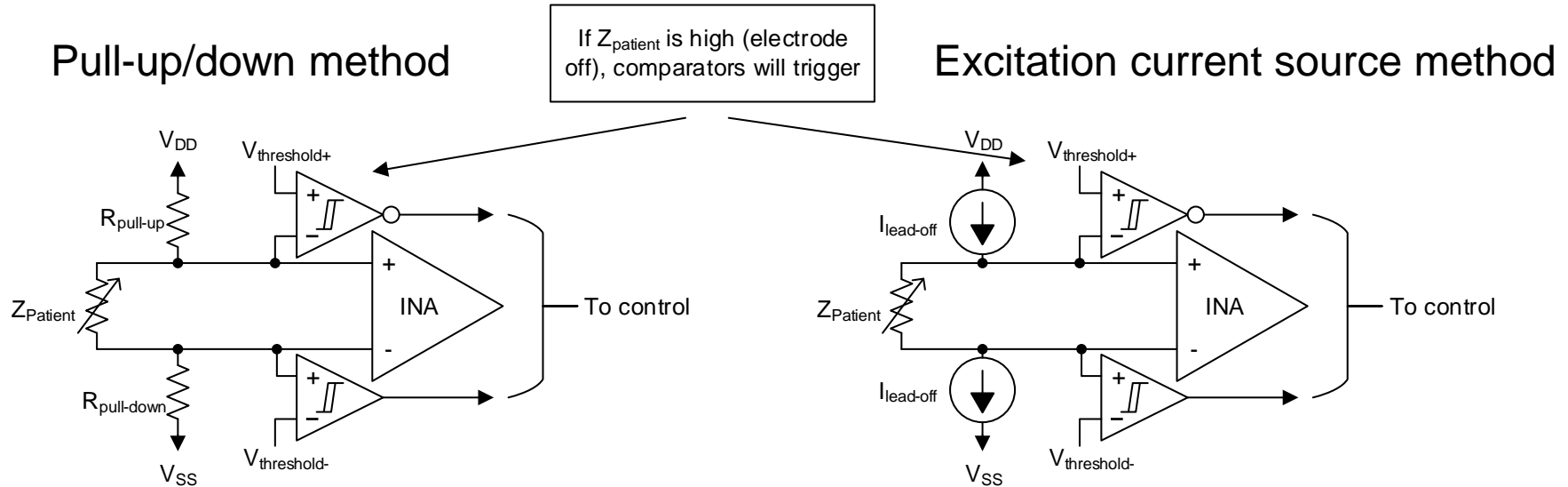
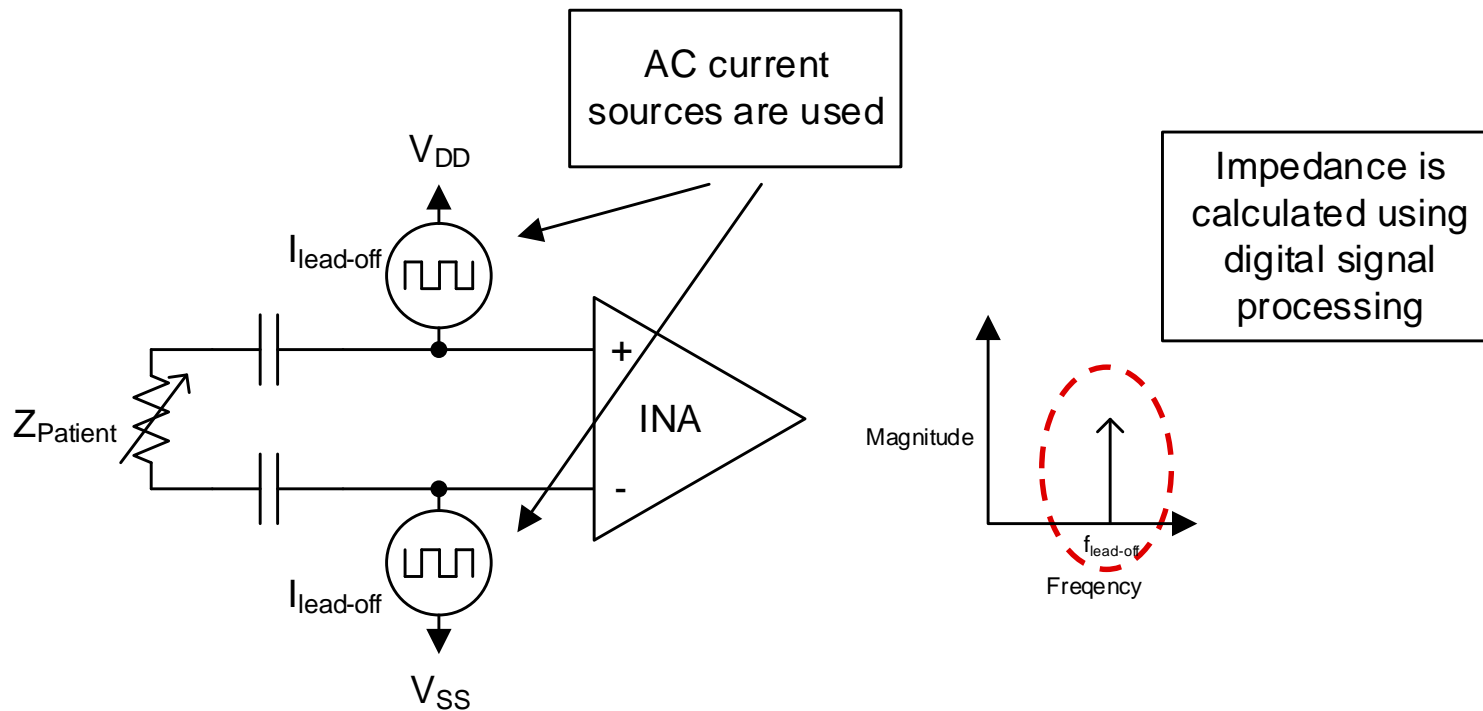
# AC lead-off detection


Detect if *lead* is disconnected: AC coupled front end



# Data converter for ECG

## Resolution requirements


### Legacy ECG systems

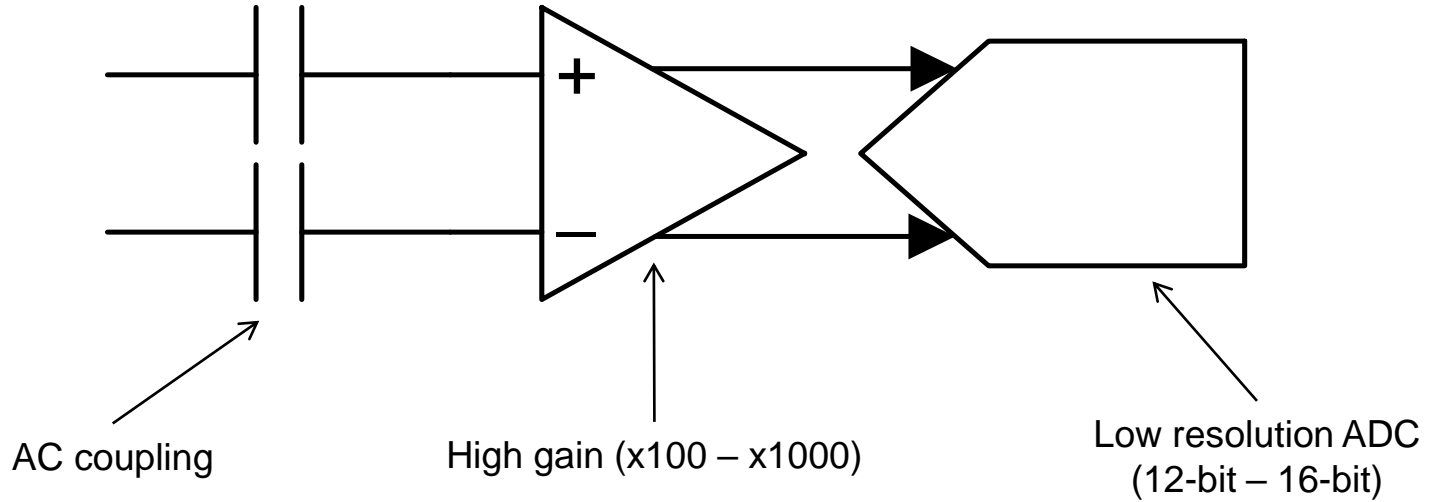

# Data converter for ECG

## Resolution requirements

### New ECG systems

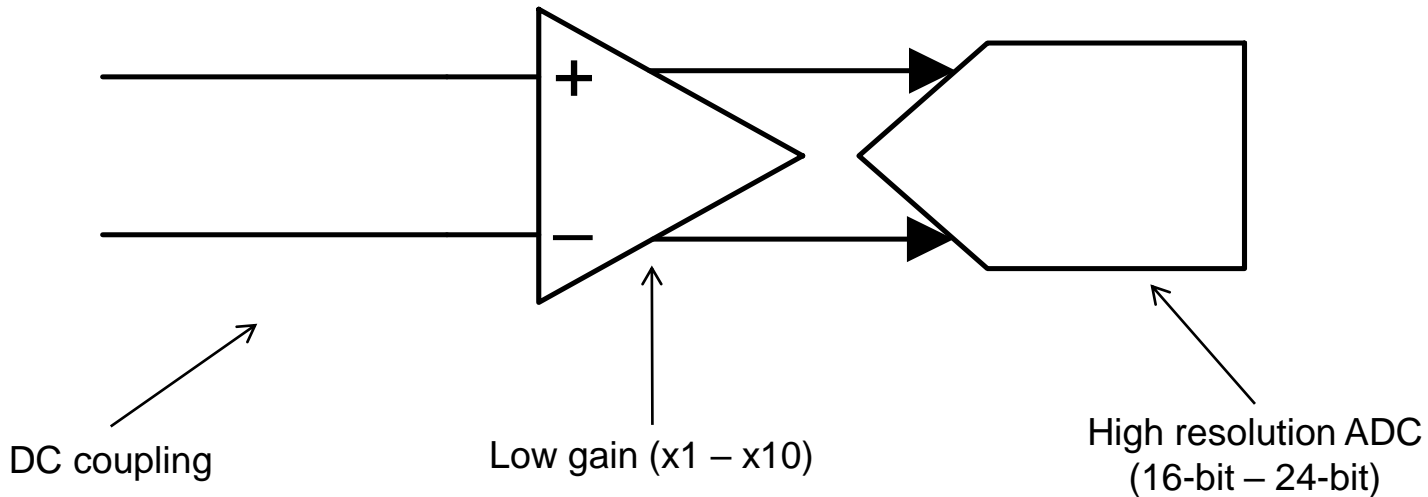



© Copyright 2021 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.  
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)