


# Let's Break It Down: How Buck Converters Make Your Power Supply More Flexible



Kelvin Odom


It's been said that if you only have a hammer, you'll see every problem as a nail. When it comes to powering automotive processors, you'll find hammers, screwdrivers and more in TI's extensive portfolio of highly integrated power-management ICs (PMICs). My colleague Karl Wallinger describes the benefits of these devices in his blog post, "[How an integrated power management IC can simplify your infotainment or ADAS system.](#)" However, your power designer's toolbox is not complete without also considering discrete buck converters. In this post, I'll illustrate a few situations where the flexibility of buck converters makes them a good choice for automotive point-of-load (POL) power.

Regardless of the specific system they're used in, the processor power trees for advanced driver assistance systems (ADAS) and infotainment systems tend to look fairly similar. The car battery supplies its nominal 13.5V output through an overvoltage protection IC to a wide input voltage buck converter. The wide  $V_{IN}$  converter then supplies 5V or 3.3V to several POL converters, which convert down to the voltage levels required by the processor. [Figure 1](#) illustrates this common architecture.

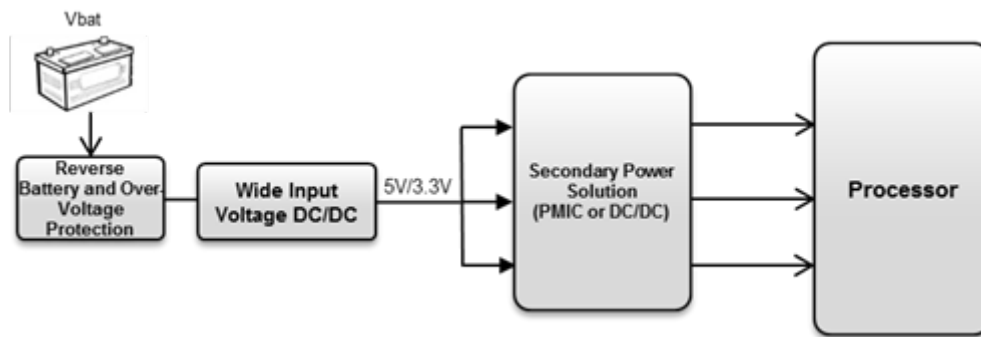


**Figure 1. Common Power Tree for ADAS and Infotainment Systems**

You can easily adapt this basic solution to a variety of system needs, with either one integrated PMIC (one IC with multiple power converters inside) or multiple discrete, single-output converters supplying the processor power. The biggest benefit of using discrete converters is their flexibility in the face of changing system power requirements. [Figure 2](#) shows a typical power tree of a surround-view camera electronic control unit (ECU) using a discrete buck converter solution.

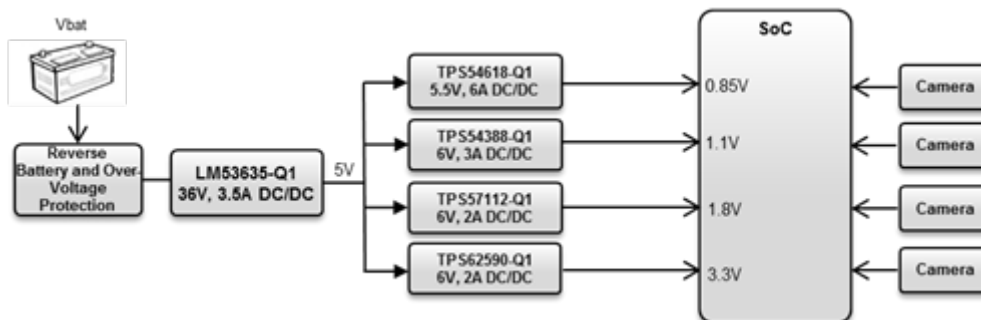

**Figure 2. Typical Power Tree for a Surround-view System ECU**

In this layout, there is one buck converter for each power rail on the system on chip (SoC), which might seem a bit more complex than an integrated solution. One other consideration, however, is the trend of increasing processor power requirements. Just a few years ago, the processor core rail may have required only 4A. All other things being equal, you'd likely be inclined to use the [LP87524B-Q1](#), a PMIC that can supply a 4A rail, a 2.5A rail, and two 1.5A rails, and capture the full power tree in one device. Unfortunately, when you discover later in the design process that your core rail needs more power than you initially thought, your board will need to change radically. This won't happen with discrete converters, where you can quickly remedy the issue by removing the 4A [TPS57114-Q1](#) and replacing it with the footprint-compatible 6A [TPS54618-Q1](#). Sure, there will be some board layout changes, but you won't need to rebuild the power tree from the ground up – and you'll ultimately save design time by leaving the lower-current rails untouched. Figure 3 illustrates this easy scalability.

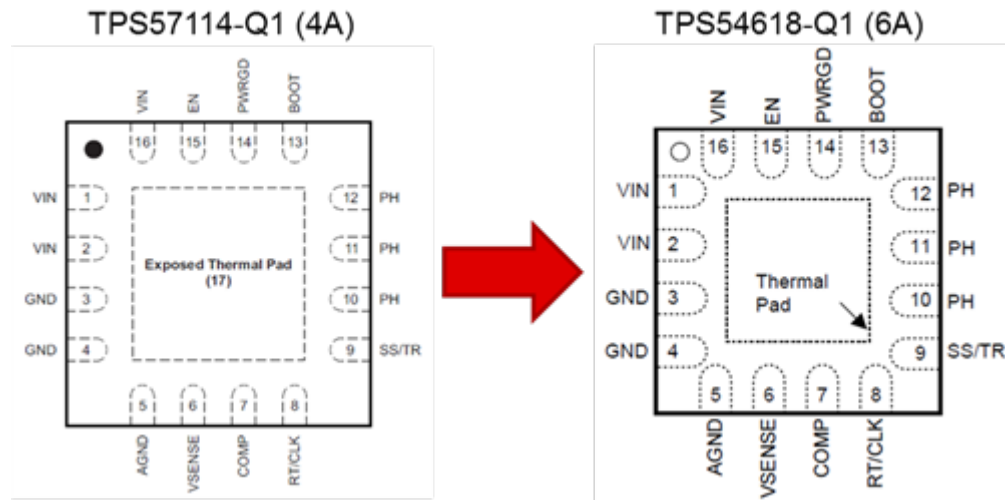

**Figure 3. Pin Compatibility Makes Scaling Core Power Easy**

On the flip side, you might find yourself looking to scale your solution down to a more cost-optimized, less processor-power-hungry version. Using the same PMIC is a quick and easy solution, but it's not possible to simply “remove” an output that you're not using. You'll be paying (in both price and board space) for one or more channels that serve no function in the system. In the case of a discrete solution, removing one or more power rails from an existing design is as simple as not populating the components on the board. There, you're getting (and using) exactly what you pay for.

PMICs are becoming an increasingly common solution for secondary power in ADAS and infotainment systems thanks to their high level of integration and ease of power sequencing. They're great solutions for these applications, but discrete DC/DC converters also provide benefits in terms of flexibility and scalability. Next time you open your toolbox to start a power design, make sure your trusty buck converters are inside. You can find all of TI's automotive secondary DC/DC converters [here](#).

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated