

Technical Article

Evolution of the Brushed DC Driver



Looking back at 20 years of electronics, we've come a long way. The components being released in 2015 have unparalleled refinement and integration. Processors are faster, LEDs are brighter, memory is denser, everything is lower power and integrated circuits (ICs) have more components integrated than ever.

Then look at a final product, such as a modern drone (Figure 1).



Figure 1. Modern Drone

1080p60 camera with active gimbal compensation? Check.

Four speed-controlled brushless DC motors outputting kilowatts of power? Check.

Long-range gigahertz digital transceiver? Not a problem.

[Brushed DC motor control](#) isn't the first thing that comes to mind when you think about advances in electronics, but it too has evolved over the years. The great thing about brushed motors is their clever internal mechanics that switch the direction of current using a constant external voltage. Primitive systems can even get away with just using a battery and power switch, but that leaves out several useful features.

A couple decades ago, building a full-featured brushed motor driver left system designers no choice but to use many discrete components. That included a microcontroller, gate drivers, relays or MOSFETs to form an H-bridge, a sense resistor, an op amp circuit to amplify the sense voltage, an [analog-to-digital converter](#) (ADC) to measure the sense voltage, a fuse for fault protection, and a multitude of passive components for various purposes. This approach grants the following features:

- **Variable speed:** An H-bridge provides switches to pulse-width modulate (PWM) the voltage being applied to the motor, and the duty cycle directly controls motor speed.
- **Bidirectional control:** An H-bridge also lets you bias the motor with either voltage polarity, to spin in both directions.
- **Fault protection:** While a fuse is often a last resort, a sense resistor gives a nondestructive way of measuring overcurrent.
- **Current control:** A sense resistor can also be used to regulate current by disabling the H-bridge momentarily.

Over the years, all of these features (and more) have been merged into monolithic slabs of silicon. Not only is it far more efficient for IC designers to optimize the analog circuits in a closed system, but you can also do things in an IC that you can't do discretely. For example, thousands of gates of digital logic can provide a serial interface, robust shoot-through protection, gate driver current control ("IDRIVE"), fault reporting, and low-power modes. The IC approach also offers FET V_{DS} sensing, supply voltage monitors and local temperature sensors. The end result is a stand-alone chip that takes up little board space, offers high reliability, and makes life simpler for the system designer.

This integration has been complemented with advances in analog process technology. Back in the 1990's, TI designed an early-generation BiCMOS process that used a "state-of-the-art" 1 μ m feature size! Our BiCMOS process nodes have since gone through numerous iterations, and 2015 technology offers dense digital logic, wide voltage support, and FETs with very low $R_{DS(on)}$ per area. The trend only continues with even more advanced nodes on the horizon.

In high-current applications, some designers today still use discrete motor circuits, historically for the sake of cost and design reuse. We addressed that space this year with the [DRV8701](#), our first full-bridge gate driver. It's competitive on cost while offering all the modern advancements of IC technology.

For lower-current brushed motors (up to 3.6-A peak), we've just released the 8-pin DRV8871 family. The [DRV8871](#) uses breakthrough technology that senses and regulates motor current without a sense resistor! That avoids the power loss, heat, board space, and cost associated with sense resistors, and there's no device in the world like it.

So if you're still using outdated solutions that are over five years old, you might want to check out what is latest and greatest.

Additional Resources

- See the [Ultra Small Brushed DC Motor Current Regulation TI Reference Design](#)
- Review the [DRV8871 datasheet](#) to learn more about its integrated features.
- Start your own brushed DC motor design with the [DRV8871EVM](#).
- Learn more about TI's [brushed DC motor drivers](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated