

# High-Side Current Sensing With Comparator Circuit




## Design Goals

Load Current ( $I_L$ )		System Supply ( $V_S$ )	Comparator Output Status	
Overcurrent ( $I_{OC}$ )	Recovery Current ( $I_{RC}$ )	Typical	Overcurrent	Normal Operation
1A	0.5A	10V	$V_{OL} < 0.4V$	$V_{OH} = V_{PU} = 3.3V$
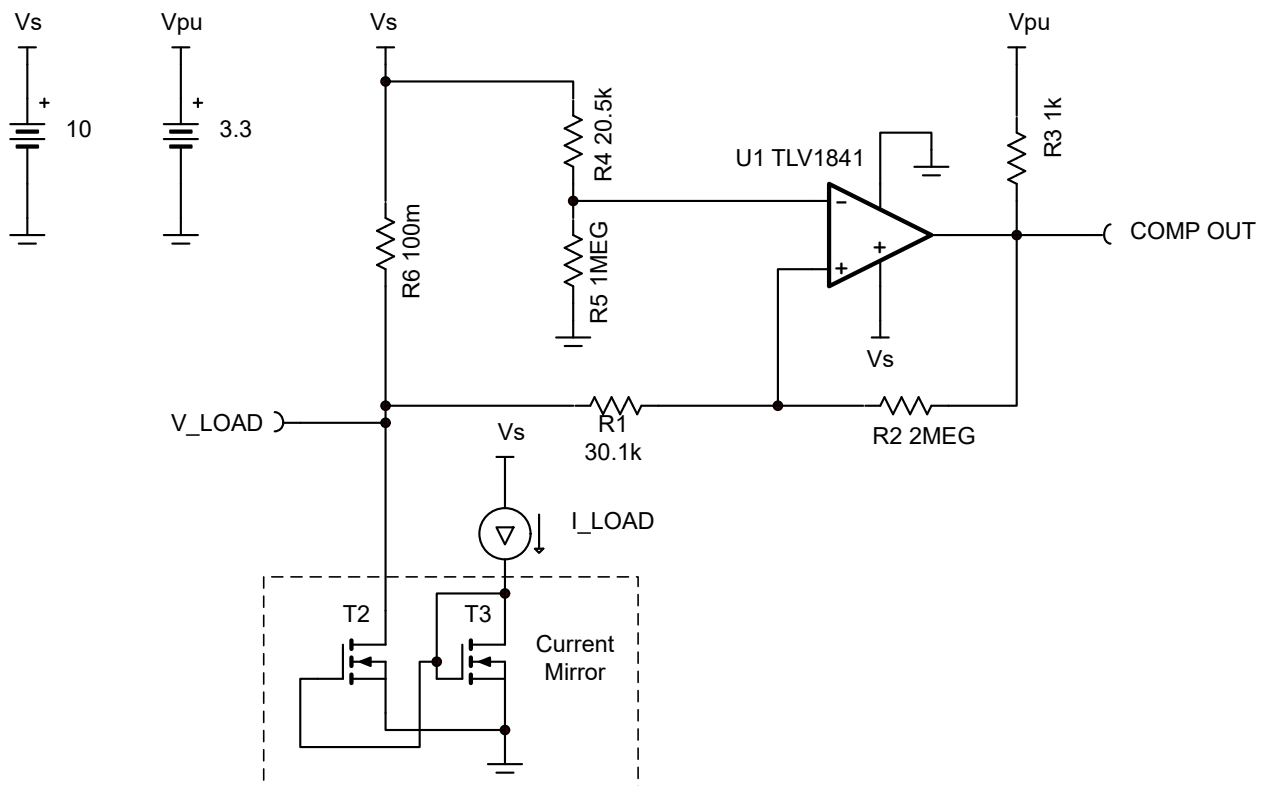
## Design Description

This high-side, current sensing circuit uses one comparator with a rail-to-rail input common-mode range to create an overcurrent alert (OC-Alert) signal at the comparator output (COMP OUT) if the load current rises above 1A. The OC-Alert signal in this implementation is active low. So when the 1A threshold is exceeded, the comparator output goes low. Hysteresis is implemented such that OC-Alert returns to a logic high state when the load current reduces to 0.5A (a 50% reduction). This circuit utilizes an open-drain output comparator to level shift the output high logic level for controlling a digital logic input pin. For applications needing to drive the gate of a MOSFET switch, a comparator with a push-pull output is preferred.



## Design Notes

1. Select a comparator with rail-to-rail input common-mode range to enable high-side current sensing.
2. Select a comparator with an open-drain output stage for level-shifting.
3. Select a comparator with low input offset voltage to optimize accuracy.
4. Calculate the value for the shunt resistor ( $R_6$ ) so the shunt voltage ( $V_{SHUNT}$ ) is at least ten times larger than the comparator offset voltage ( $V_{IO}$ ).

## Design Steps

- Select the value of  $R_6$  so  $V_{SHUNT}$  is at least 10 times greater than the comparator input offset voltage ( $V_{IO}$ ). Making  $R_6$  very large improves OC detection accuracy but reduces supply headroom.


$$V_{SHUNT} = (I_{OC} \times R_6) \geq 10 \times V_{IO} = 55\text{mV}$$

$$\text{set } R_6 = 100\text{m}\Omega \text{ for } I_{OC} = 1\text{A} \text{ and } V_{IO} = 5.5\text{mV}$$


- Determine the desired switching thresholds for when the comparator output transitions from high-to-low ( $V_L$ ) and low-to-high ( $V_H$ ).  $V_L$  represents the threshold when the load current crosses the OC level, while  $V_H$  represents the threshold when the load current recovers to a normal operating level.

$$V_L = V_S - (I_{OC} \times R_6) = 10 - (1 \times 0.1) = 9.9\text{V}$$
 
$$V_H = V_S - (I_{RC} \times R_6) = 10 - (0.5 \times 0.1) = 9.95\text{V}$$




 - With the non-inverting input pin of the comparator labeled as  $V_{TH}$  and the comparator output in a logic low state (ground), derive an equation for  $V_{TH}$  where  $V_H$  represents the load voltage ( $V_{LOAD}$ ) when the comparator output transitions from low to high. Note that the simplified diagram for deriving the equation shows the comparator output as ground (logic low).



$$V_{TH} = V_H \times \left( \frac{R_2}{R_1 + R_2} \right)$$

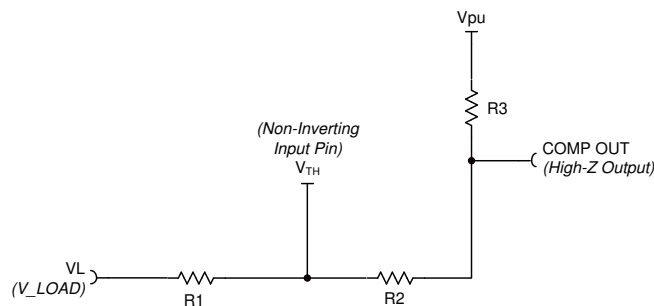- With the non-inverting input pin of the comparator labeled as  $V_{TH}$  and the comparator output in a high-impedance state, derive an equation for  $V_{TH}$  where  $V_L$  represents the load voltage ( $V_{LOAD}$ ) when the comparator output transitions from high to low. Applying *superposition* theory to solve for  $V_{TH}$  is recommended.



$$V_{TH} = V_L \times \left( \frac{R_2 + R_3}{R_1 + R_2 + R_3} \right) + V_{PU} \times \left( \frac{R_1}{R_1 + R_2 + R_3} \right)$$

5. Eliminate variable  $V_{TH}$  by setting the two equations equal to each other and solve for  $R_1$ . The result is the following quadratic equation. Solving for  $R_2$  is less desirable since there are more standard values for small resistor values than the larger ones.

$$0 = (V_{PU}) \times R_1^2 + (V_{PU} \times R_2 + V_L \times (R_3 + R_2) - V_H \times R_2) \times R_1 + (V_L - V_H) \times (R_2^2 + R_2 \times R_3)$$

6. Select values for  $R_3$  and  $R_2$ .  $R_3$  is significantly smaller than  $R_2$  ( $R_3 \ll R_2$ ). Avoid increasing  $R_3$  since an increase in  $R_3$  causes the comparator logic high-output level to increase beyond  $V_{PU}$ . For example, increasing  $R_3$  to a value of  $100\text{k}\Omega$  can cause the logic high output to be  $3.6\text{V}$ . In this case, select  $R_2 = 2\text{M}$  and  $R_3 = 1\text{k}\Omega$ .

$$R_2 = 2\text{M}\Omega$$

$$R_3 = 1\text{k}\Omega$$

7. Calculate  $R_1$  after substituting in numeric values for  $V_{PU}$ ,  $R_2$ ,  $V_L$ ,  $V_H$ , and  $R_3$ . For this design, set  $V_{PU} = 3.3$ ,  $R_2 = 2\text{M}$ ,  $V_L = 9.9$ ,  $V_H = 9.95$ , and  $R_3 = 1\text{k}\Omega$ .

$$0 = (3.3) \times R_1^2 + (6.591\text{M}) \times R_1 - (200.1\text{G})$$

the positive root for  $R_1 = 29.9\text{k}\Omega$

using standard 1% resistor values,  $R_1 = 30.1\text{k}\Omega$

8. Calculate  $V_{TH}$  using the equation derived in [Design Step 3](#); use the calculated value for  $R_1$ . Note that  $V_{TH}$  is less than  $V_L$  since  $V_{PU}$  is less than  $V_L$ .

$$V_{TH} = V_H \times \left( \frac{R_2}{R_1 + R_2} \right) = 9.802\text{V}$$

9. With the inverting terminal labeled as  $V_{TH}$ , derive an equation for  $V_{TH}$  in terms of  $R_4$ ,  $R_5$ , and  $V_S$ .

$$V_{TH} = V_S \times \left( \frac{R_5}{R_4 + R_5} \right)$$


10. Calculate  $R_4$  after substituting in numeric values  $R_5 = 1\text{M}$ ,  $V_S = 10$ , and the calculated value for  $V_{TH}$ .

$$R_4 = \left( \frac{R_5 \times (V_S - V_{TH})}{V_{TH}} \right) = 20.15\text{k}\Omega$$


using standard 1% resistor values,  $R_4 = 20.5\text{k}\Omega$

## Design Simulations

### DC Simulation Results

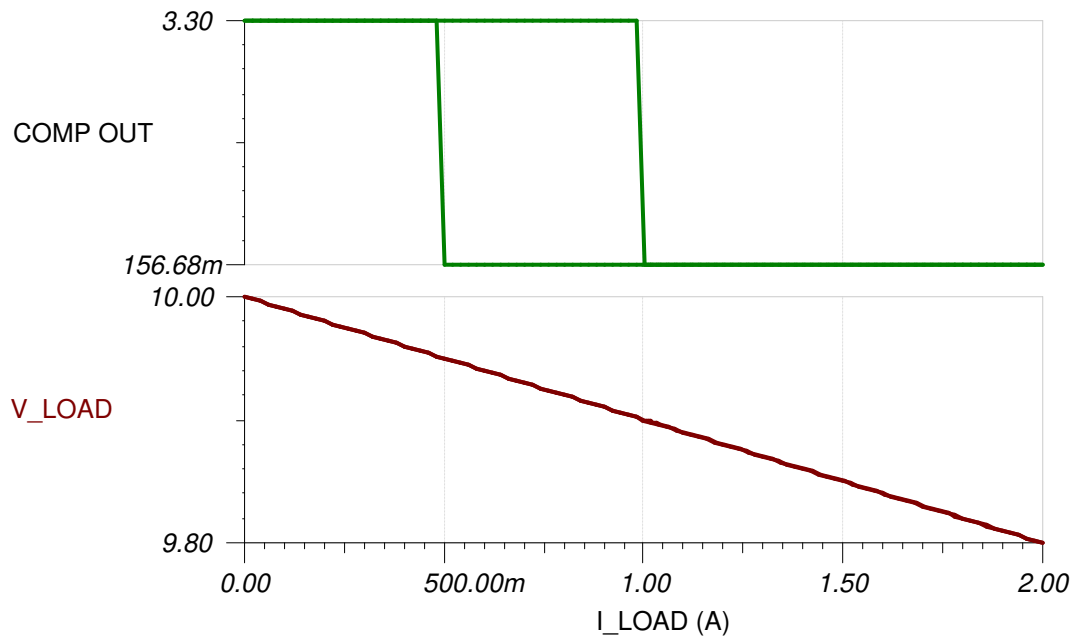

### Transient Simulation Results

 

## Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

See [Circuit SPICE Simulation File SLOM456](#).

## Design Featured Comparator

Parameters	TLV184x	TLV183x
$V_S$	2.7V to 40V	2.7V to 40V
$V_{inCM}$	2.7V to 40V	2.7V to 40V
$V_{OUT}$	Open-Drain	Push-Pull
$V_{OS}$	500 $\mu$ V	500 $\mu$ V
$I_Q$	70 $\mu$ A/Ch	70 $\mu$ A/Ch
$t_{PD(HL)}$	65ns	65ns
#Channels	1, 2, 4	1, 2, 4
	<a href="#">TLV184x</a>	<a href="#">TLV183x</a>

## Design Alternate Comparator

	TLV902x_3x	TLV323x
$V_S$	1.6V to 5.5V	2.7V to 5.5V
$V_{inCM}$	Rail-to-rail	Rail-to-rail
$V_{OUT}$	Open-Drain, Push-Pull	Push-Pull
$V_{OS}$	300 $\mu$ V	500 $\mu$ V
$I_Q$	16 $\mu$ A/Ch	200 $\mu$ A/Ch
$t_{PD(HL)}$	100ns	20ns
#Channels	1, 2, 4	1, 2
	<a href="#">TLV902x_3x</a>	<a href="#">TLV3231</a>

## Trademarks

All trademarks are the property of their respective owners.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated