

# **0.7-V to 3.3-V Input, 3.3-V Output, High-Efficiency DC/DC Converter**

---

*PMP - DC/DC Low-Power Converters*

## **ABSTRACT**

This design was created to help those desiring to design-in a Stellaris® ARM® Cortex™-M3 MCU into a system requiring a very low-input voltage range and is concerned about maintaining high efficiency and long battery life. This particular design allows for an input voltage between 0.7V to 3.3V.

---

## **1 Features**

- 0.7 V to 3.3 V input voltage range
- Fixed 3.3-V output eliminates need for external voltage-setting resistors
- TPS61221 is capable of driving up to 200 mA
- High efficiency (up to 92%)
- Low-quiescent current (less than 5.5  $\mu$ A)
- Tiny SC-70 package

## **2 Introduction**

This reference design is for the Stellaris® ARM® Cortex™-M3 MCU devices and accounts for voltage and current, requirements given below. The Stellaris® devices only require a single 3.3V input, so no sequencing is required. The operating input voltage for this reference design is 0.7V to 3.3V. This design is optimized for very-low input voltage range and small design/low part count.

### 3 Requirements

The power requirements for each Stellaris® ARM® Cortex™-M3 MCU family are listed below.

For more information and other reference designs, please visit [www.ti.com/processorpower](http://www.ti.com/processorpower).

**Table 1. Stellaris® ARM® Cortex™-M3 MCU Family Power Requirements**

DEVICE FAMILY	PIN NAME	VOLTAGE (V)	I <sub>MAX</sub> (mA)	TOLERANCE	SEQUENCING ORDER	TIMING DELAY	COMMENTS
LM3S100 series LM3S300 series LM3S600 series LM3S800 series LM3S1000 series LM3S2000 series LM3S3000 series LM3S5000 series	VDD	3.3	170	±10%	—	—	Internal regulator supplies power to device core
LM3S6000 series LM3S8000 series	VDD	3.3	225	±10%	—	—	Internal regulator supplies power to device core
LM3S9000 series	VDD	3.3	150	±10%	—	—	Internal regulator supplies power to device core
LM3S2B93, LM3S2B2793, LM3S5B91, LM3S5791	VDD	3.3	100	±10%	—	—	Internal regulator supplies power to device core

**Note:** The "Imax" currents listed are worst case expected values.

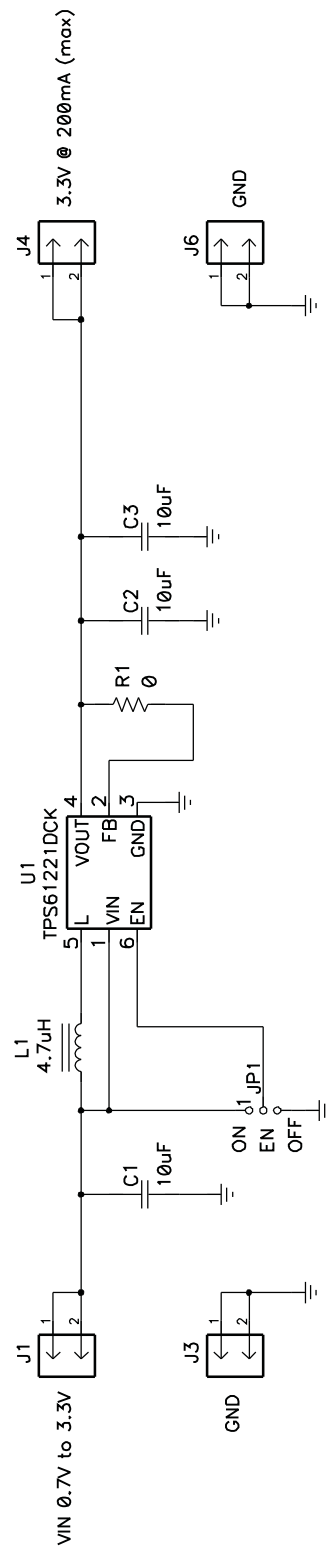


Figure 1. PMP4776 Reference Design Schematic

## 4 List of Materials

**Table 2. PMP4776 List of Materials**

REF DES	QTY	VALUE	DESCRIPTION	SIZE	PART NUMBER	MFR
C1, C2, C3	3	10 $\mu$ F	Capacitor, ceramic, 6.3 V, X5R, 20%	0603	GRM188R60J106ME84	muRata
L1	1	4.7 $\mu$ H	Inductor, SMT, 550 mA, 145 m $\Omega$	0.08" x 0.08"	EPL3015-472ML	Coilcraft
R1	1	0	Resistor, chip, 1/16W, 1%	0603	Std	Std
U1	1		IC, Tiny low-input voltage boost converter	SC-70	TPS61221DCK	TI

## 5 Test Results

### 5.1 Startup

The input and output startup waveforms are shown in the figure below after the application of  $V_{IN}$ . In [Figure 2](#), the input voltage was set to 1.2 V and the 3.3 V output was loaded to 70 mA. In [Figure 3](#) the input voltage was set to 1.2 V and the 3.3-V output was loaded to 0 mA. In [Figure 4](#) The input voltage was set to 2.4 V and the 3.3-V output was loaded to 168 mA. In [Figure 5](#) the input voltage was set to 1.2 V and the 3.3-V output was loaded to 0 mA. ( $V_{IN}$  is 1 V/div,  $V_{OUT}$  is 1 V/div. Timing is 1 ms/div).

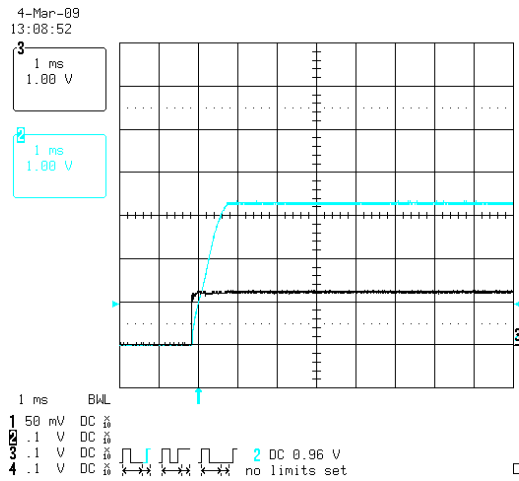


Figure 2. Startup

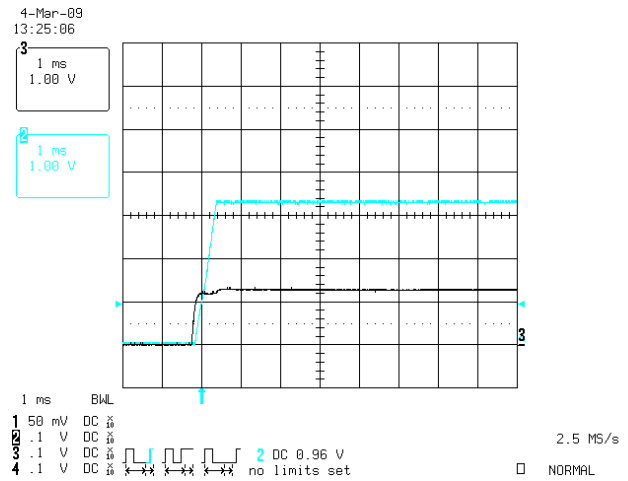


Figure 3. Startup

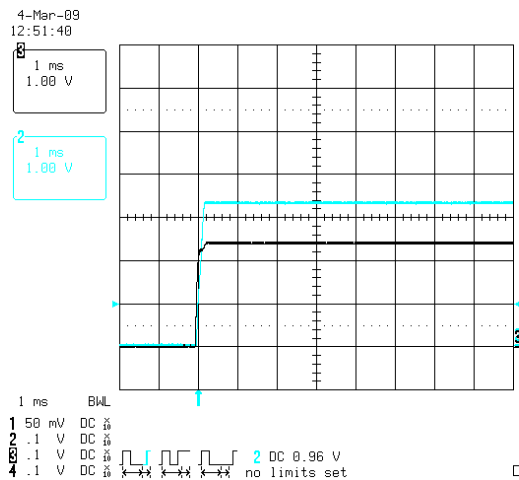


Figure 4. Startup

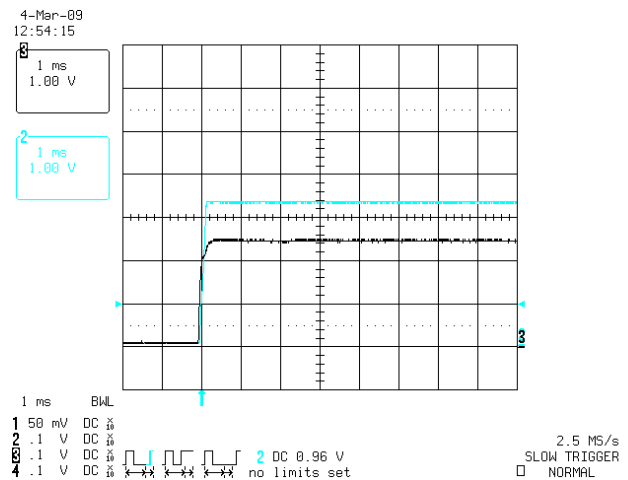


Figure 5. Startup

## 5.2 Ripple

The 3.3-V output ripple voltage is shown in the figures below . In [Figure 6](#), the image was taken with the input voltage set to 1.2 Vdc and the output loaded to 70 mA. In [Figure 7](#), the image was taken with the input voltage set to 2.4 Vdc and the output loaded to 168 mA. (20 m V/div, timing 2  $\mu$ s/div).

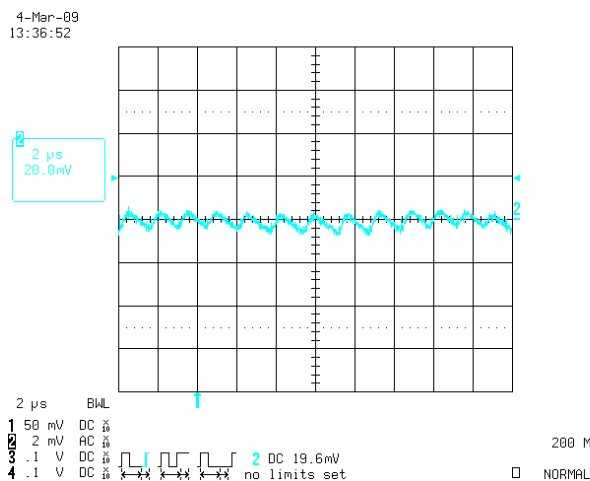


Figure 6. Output Ripple Voltage,  $V_{IN} = 5\text{ V}$

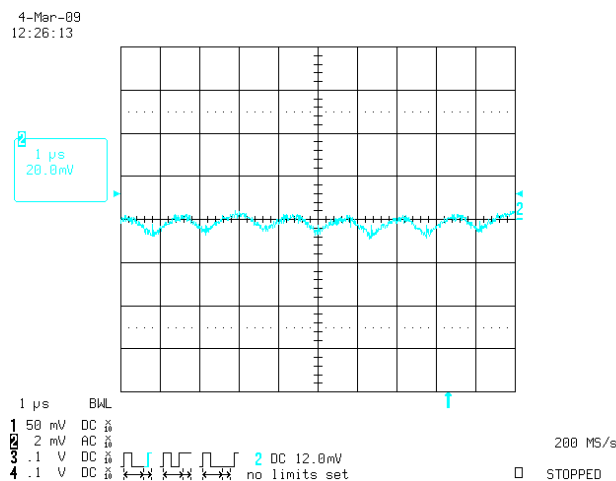


Figure 7. Output Ripple Voltage,  $V_{IN} = 12\text{ V}$

## 5.3 Load Transient

[Figure 8](#) shows the 3.3-V output voltage when the load current is stepped between 35 mA and 65 mA.  $V_{IN} = 1.2\text{ Vdc}$ . (20 mV/div, 50 mA/div, 10 ms/div). [Figure 9](#) shows the 3.3-V output voltage when the load current is stepped between 100 mA and 175 mA.  $V_{IN} = 2.4\text{ Vdc}$ . (20 mV/div, 100 mA/div, 2 ms/div)

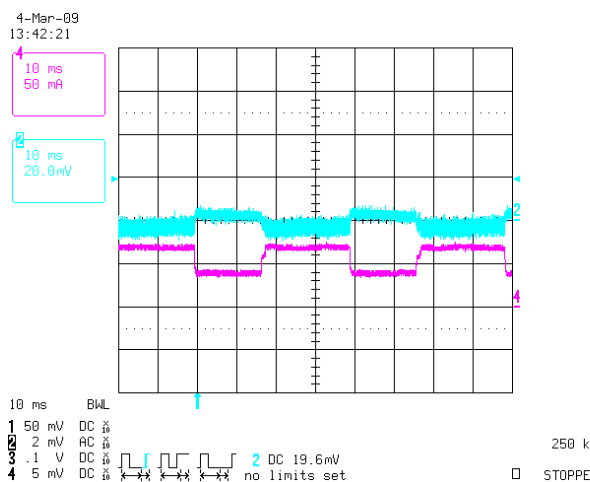


Figure 8. Load Transient

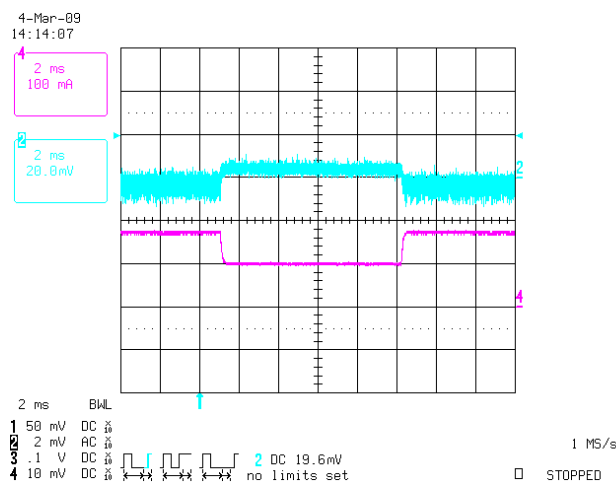



Figure 9. Load Transient

## 5.4 Switching Node

The switching node waveform is shown in [Figure 10](#) with a 2.4-V input voltage and 168-mA load. ( $V_{OUT}$  is 2 V/div, timing is 1  $\mu$ s/div) .

6-Mar-09  
12:54:37

2  
1  $\mu$ s  
2.00 V

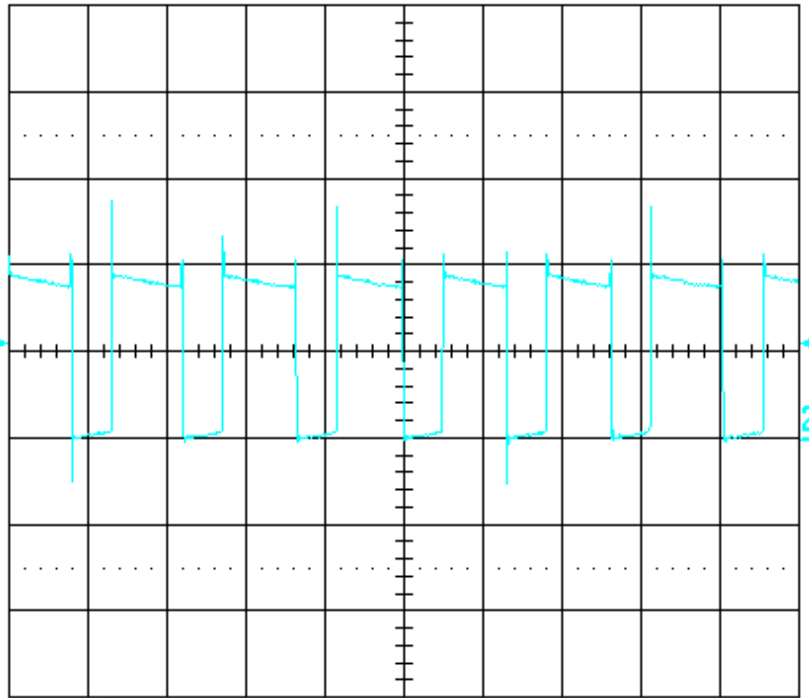

- 1  $\mu$ s
- 1 5 mV 50 $\Omega$
  - 2 .2 V DC  $\times 10$
  - 3 5 mV 50 $\Omega$
  - 4 5 mV 50 $\Omega$



2 DC 2.24 V

200 MS/s

STOPPED

**Figure 10. Switching Node Waveform, 2.4V Input Voltage and 168mA Load**

## 5.5 Efficiency

The TPS61221 converter efficiency is shown in .

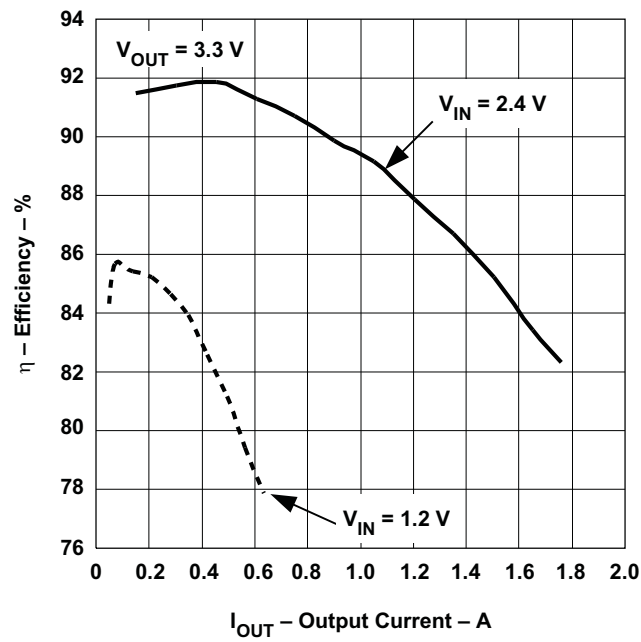


Figure 11. TPS61221 Efficiency



## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2009, Texas Instruments Incorporated