

TI Designs: TIDA-01636

Power Rail Noise Analyzer Reference Design



Description

This reference design is an active pass-band filter connected to the analog-to-digital converter (ADC) in a C2000™ microcontroller (MCU). The system senses ripple and noise on the power rail in the band of interest. The Fast-Fourier Transformation (FFT) algorithm analyzes harmonic content of the signal and allows for switching frequency detection. The analysis enables for adaptive real-time switching frequency dithering in high-power applications and better electromagnetic compatibility interference (EMI) control. Alternatively, ripple counters in feedback-less positioners can benefit the design.

Digital Signal Processing (DSP) features of C2000™ microcontrollers play an important role in the system and enable digital-power (on-board chargers, DC-DC converters) and motor control (traction inverters) applications to become smarter and more efficient.

Resources

TIDA-01636	Design Folder
OPA365-Q1	Product Folder
TMS320F28069M	Product Folder

Features



- Multiple Feedback Filter (MFB) Topology
- Single-Supply Power
- Example Firmware for TMS320F28069M C2000 MCU Including Source Code

Applications

- HEV and EV - Inverter and Motor Control
- HEV and EV - DC/DC Converter
- Various RippleCounters



[ASK Our E2E™ Experts](#)

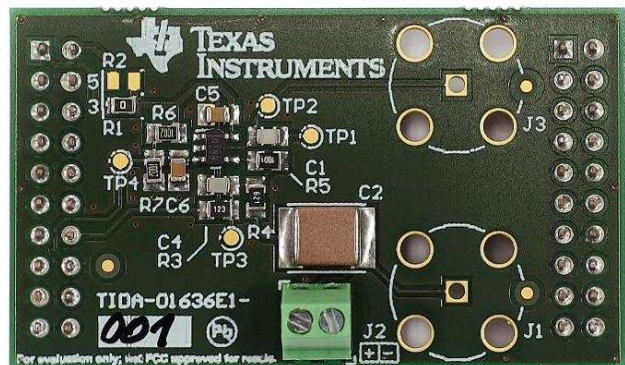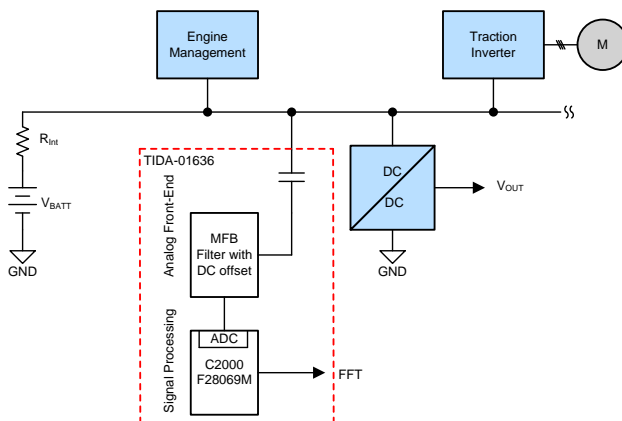

An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 System Description

The TIDA-01636 reference design consists of an active multiple feedback topology (MFB) pass-band filter and a host MCU. Input of the filter connects to the in-vehicle voltage rail. The filter passes and amplifies the signal in the band of interest. The board connects to the LAUNCHXL-F28069M LaunchPad™ Development Kit with the TMS320F28069M host microcontroller from the C2000 family. The microcontroller uses the integrated ADC for signal conversion and performs FFT. This process builds magnitude spectrum of the voltage rail ripple. The host system in an HEV or EV vehicle can use the information for smart control of other in-vehicle systems.

Figure 1 shows the reference design from the top and the bottom side.

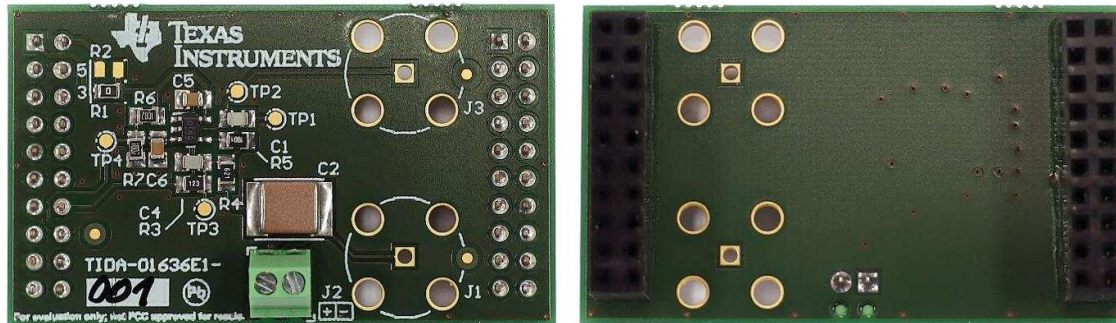


Figure 1. TIDA-01636 Board (Top and Bottom)

1.1 Key System Specifications

Table 1. Key System Specifications

PARAMETER	SPECIFICATIONS
Input Supply Voltage	3.3 V or 5 V from the LaunchPad Development Kit
Input Signal Amplitude	Maximum 170 mV _{p-p}
Filter Bandwidth	77.8 Hz to 1.19 MHz
Filter Gain	25.73 dB (pass-band)
Filter Order	1st order high-pass filter, 2nd order low-pass filter
FFT Stages	10
ADC Sample Rate	1.75 MSPS (up to 3.46 MSPS)
ADC Buffer	2048B
ADC Resolution	12 bit
ADC Reference	Integrated, 3.3 V
Form Factor	2-layer PCB 50 mm x 30 mm
Interface	Code Composer Studio™ (CCS) software

2 System Overview

2.1 Block Diagram

Figure 2 shows a block diagram of the TIDA-01636 reference design and the typical implementation in the system.

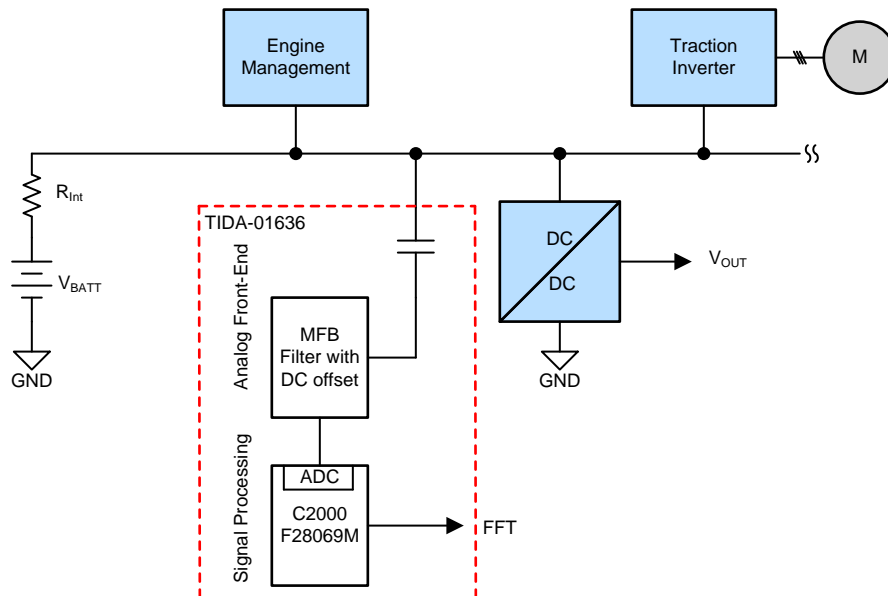


Figure 2. TIDA-01636 Block Diagram

2.2 Highlighted Products

2.2.1 OPA365-Q1

The OPAx365-Q1 zero-crossover family, rail-to-rail, high-performance, CMOS operational amplifiers are optimized for very low voltage, single-supply applications. Rail-to-rail input/output, low noise ($4.5 \text{ nV}/\sqrt{\text{Hz}}$) and high-speed operation (50-MHz gain bandwidth) make these devices ideal for driving sampling data converters (such as the ADS7822-Q1 or the ADS1115-Q1 devices), specifically in short to mid-range radar applications. The OPAx356-Q1 family of operational amplifiers are also well-suited for HEV or EV and powertrain applications in DC-DC converters and as transmission control in engine control units.

Special features include an excellent common-mode rejection ratio (CMRR), no input stage crossover distortion, high input impedance, and rail-to-rail input and output swing. The input common-mode range includes both the negative and positive supplies. The output voltage swing is within 10 mV of the rails.

The OPA365-Q1 device (single version) is available in the 5-pin SOT-23 package. The OPA2365-Q1 device (dual version) is available in the 8-pin SOIC package. All versions are specified for operation from -40°C to 125°C . Single and dual versions have identical specifications for maximum design flexibility.

2.2.2 C2000™ TMS320F28069M MCU

The F2806x Piccolo™ family of microcontrollers (MCUs) provides the power of the C28x core and control law accelerator (CLA) coupled with highly-integrated control peripherals in low pin-count devices. This family is code-compatible with previous C28x-based code, and also provides a high level of analog integration. An internal voltage regulator allows for single-rail operation. Enhancements have been made to the high-resolution pulse-width modulator (HRPWM) module to allow for dual-edge control (frequency modulation). Analog comparators with internal 10-bit references have been added and can be routed directly to control the ePWM outputs. The ADC converts from a 0- to 3.3-V fixed full-scale range and supports ratio-metric VREFHI and VREFLO references. The ADC interface has been optimized for low overhead and latency.

2.3 System Design Theory

2.3.1 Pass Band Filter Design

Figure 3 shows a circuit diagram for the pass-band filter. The filter splits in two parts:

- High-pass filter (1st order, -20 dB/dek)
- Low-pass filter (2nd order, -40 dB/dek)

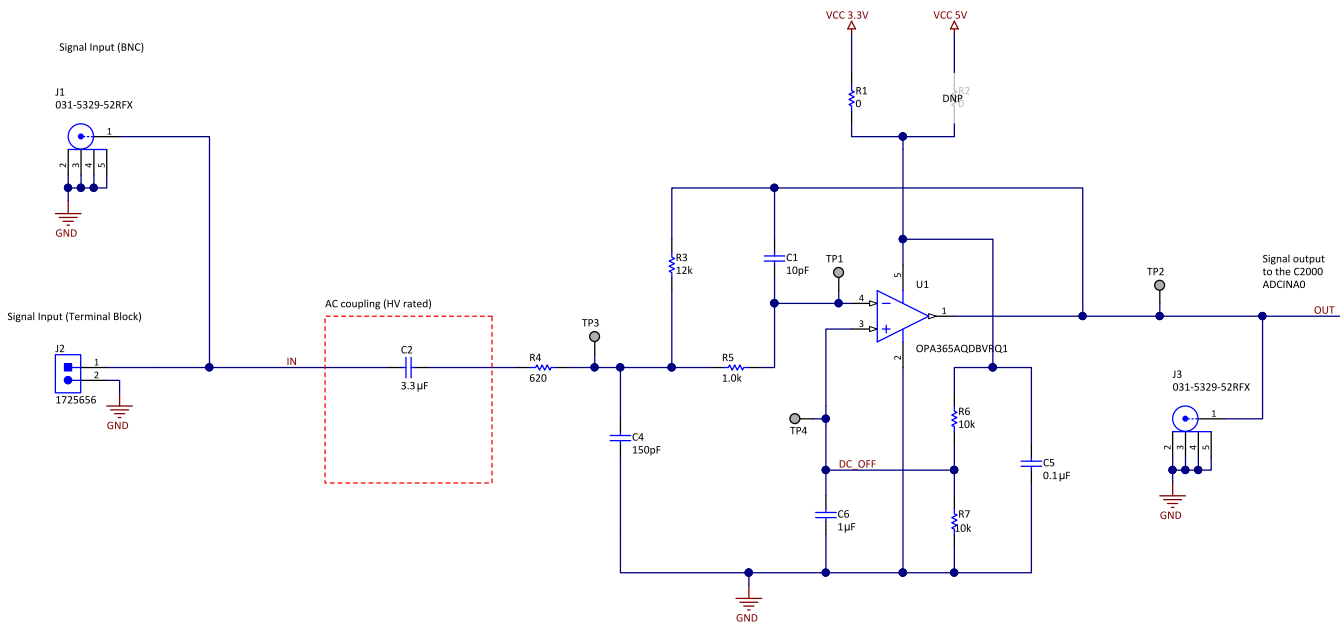


Figure 3. Pass-Band Active Filter in TIDA-01636

The input signal connects to the filter through the terminal block J2. Alternatively, the BNC connector J1 serves this purpose during circuit debugging.

The coupling capacitor C2 and input impedance of the subsequent active filter define the high-pass cutoff frequency. Some assumptions can be made to simplify input impedance calculation. The cutoff frequency for the high-pass filter is significantly lower than the cutoff frequency for the active low-pass filter. For this reason, the analysis can ignore capacitors C1 and C4 and treat them as an open circuit. In this case, resistor R5 is in series only with the inverting input of the operational amplifier U1 and can be ignored as well. Using this simplification turns the circuit into an inverting amplifier where resistors R4 and R3 set gain. Resistor R4 is then the effective input impedance. These assumptions set cutoff frequency of the high-pass filter as per Equation 1. It is important that the voltage rating of the capacitor C2 is higher than maximum DC voltage from the signal source.

$$f_{c(\text{high-pass})} = \frac{1}{2\pi \times C2 \times R4} = \frac{1}{2\pi \times 3.3 \mu\text{F} \times 620 \text{ k}\Omega} = 77.8 \text{ Hz } (-3 \text{ dB}) \quad (1)$$

The cutoff frequency of the low-pass filter is independent of the C2 selection. Resistors R3 and R4 set the gain for the band of interest as per Equation 2.

$$A_{\text{PASS}} = -\frac{R3}{R4} = \frac{12 \text{ k}\Omega}{620 \text{ k}\Omega} = 19.35 \rightarrow 20 \times \log 19.35 = 25.73 \text{ dB} \quad (2)$$

Equation 3 defines the cutoff frequency for the MFB low-pass filter.

$$f_{c(\text{low-pass})} = \frac{1}{2\pi \times \sqrt{R3 \times R5 \times C1 \times C4}} = \frac{1}{2\pi \times \sqrt{12 \text{ k}\Omega \times 1 \text{ k}\Omega \times 10 \text{ pF} \times 150 \text{ pF}}} = 1.19 \text{ MHz} \quad (3)$$

The resistor divider R6, R7 creates a virtual ground for the single-supply filter. Capacitor C6 reduces the noise on the non-inverting input pin of the operational amplifier. Capacitor C5 is a bypassing capacitor for U1. Resistors R1 and R2 are power-supply selectors which enable power either from the 3.3-V or 5-V rail from the C2000 LaunchPad.

NOTE: The cutoff frequency is typically identified as the point where the transfer function of a filter drops by -3 dB. This drop corresponds to approximately half of the power transfer. However, higher-order filters have a steeper rolloff (for example: -40 dB/dec for a second-order filter) and the cutoff frequency is defined as $n(-3$ dB) where n is the filter order. This definition often causes confusion because some technical articles or online calculators use formulas referring to the -3 -dB point; whereas, others use $n(-3$ dB). Check the calculation using a simulation tool.

2.3.2 Firmware

Embedded firmware for the C2000 LaunchPad development board uses the FFT function from the FPU DSP Software Library from Texas Instruments which is a part of controlSUITE™ software package. The typical installation path is "C:\ti\controlSUITE\libs\dsp\FPU\v1_50_00_00\include\". Documentation for the library is typically found at "C:\ti\controlSUITE\libs\dsp\FPU\v1_50_00_00\doc\FPU-SW-LIB-UG.pdf". Refer to the manual for details on how to use and configure FFT routines used in the reference design.

Figure 4 shows a flow diagram of the source code. The MCU uses a Direct Memory Access (DMA) unit for automatic transfer of ADC data into a buffer. The main loop waits until the DMA fills the buffer and calculates FFT based on the configuration. A user has access to FFT data through Code Composer Studio (CCS).

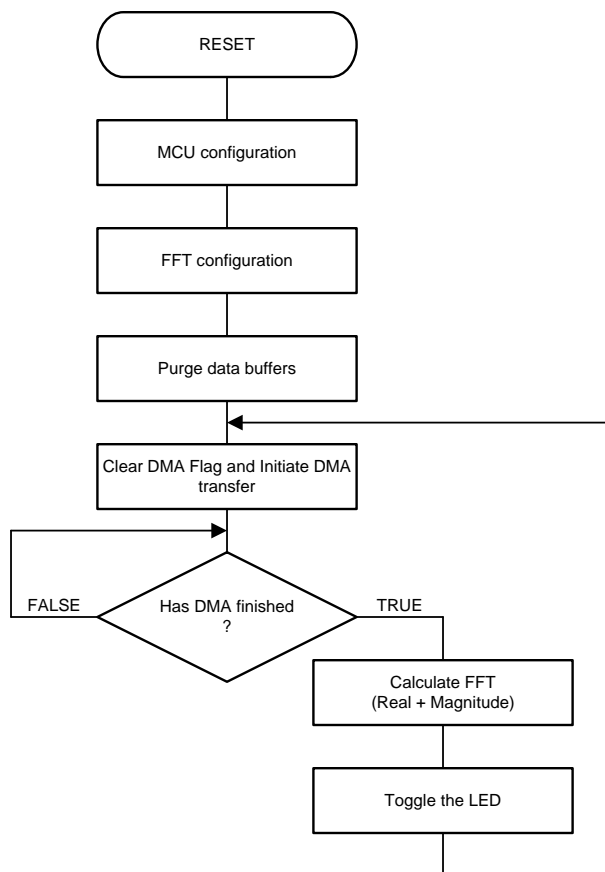


Figure 4. TIDA-01636 Firmware Flow Chart

2.3.3 Aliasing

Every analog-to-digital conversion system must consider the aliasing phenomenon to process data without distortion. This phenomenon causes every spectral content with frequency higher than half of the ADC sampling frequency wrapping around this frequency and starting affecting the band of interest. This corrupts data. The ADC sampling frequency must be at least twice the highest frequency of the input signal spectrum. Refer to for more details on aliasing and anti-aliasing filters.

Figure 5 shows the effect of aliasing.

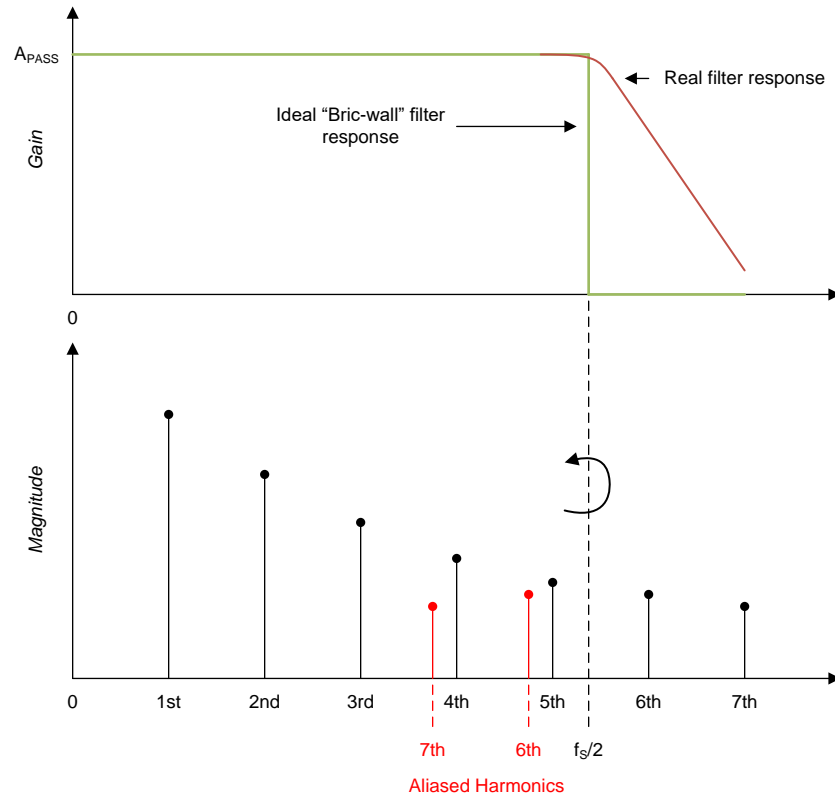


Figure 5. Aliasing Effect and Filter Response

Ideally, the low-pass filter passes every spectral content up to the half of sampling frequency. All spectral content above is suppressed to zero. However, a real filter has limited roll-off slope (for example, -20 dB/dek, -40 dB/dek) which corresponds to the filter order. For this reason, the filter may not sufficiently suppress harmonics above the half of switching frequency and they fold to the band of interest. This causes data corruption. Selecting the proper filter order, bandwidth, and sampling frequency typically requires some trade-offs. The anti-aliasing filter should be set in the way that all aliased spectral content is close to native noise level or below resolution of the system.

There are integrated analog filters which are close to the ideal "brick-wall" response but they are expensive. Note that the digital filter in the MCU does not help to avoid aliasing. The system must implement a low-pass filtering in the analog domain before analog-to-digital conversion.

3 Hardware, Software, Testing Requirements, and Test Results

3.1 Required Hardware and Software

3.1.1 Hardware

To start with the TIDA-01636 reference design:

1. Plug the reference design to the LAUNCHXL-F28069M board. The correct position of the PCB is shown in the circuit diagram.
2. Connect the LaunchPad with the reference design to the personal computer using the provided USB cable. LEDs on the LaunchPad show activity.
3. Use twisted wires for connecting the terminal J2 to the analyzed voltage rail. Alternatively, use the BNC connector J1 as the signal input.

3.1.2 Software

The reference design requires the Code Composer Studio (CCS) development tool for uploading the code example to the MCU and displaying the data. Use the following procedure to upload and run the firmware:

1. Install Code Composer Studio which is available from www.ti.com/ccs. Make sure that you select the C2000 compiler and XDS100 drivers during the installation.
(The CCS 7.4 and TI v16.9.1.LTS compiler were used for the TIDA-01636 development).
2. Import the provided firmware from *File->Import->CCS project* menu.
3. Try to compile the code (*Project->Build All* from the menu). Make sure that compilation passes without any error or warning. If there are missing resources (libraries), download and install C2000 Ware from www.ti.com/tool/C2000WARE.
4. Run the project from the *Run->Debug* menu. This programs the microcontroller.
5. Start code execution from the *Run->Resume* menu.
6. Show a graph plot from the *Tools->Graph-Single Time* menu. Fill in parameters in the dialog as [Figure 6](#) shows.

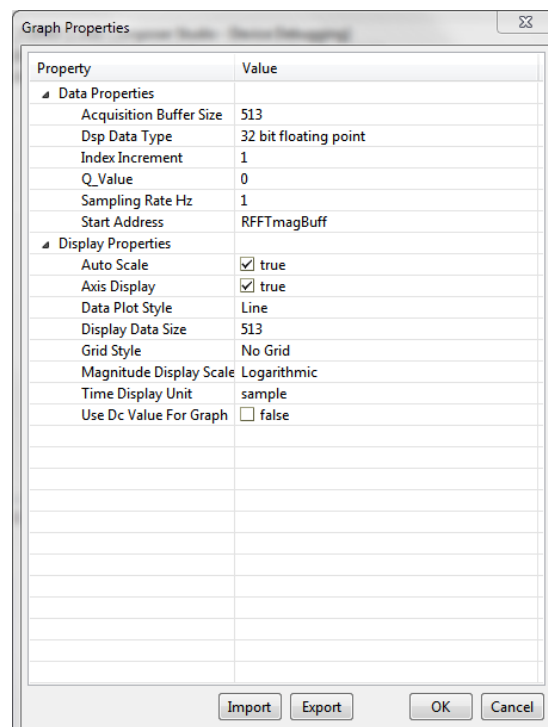


Figure 6. Graph Settings in Code Composer Studio™ for TIDA-01636

7. A graph appears after confirming the previous dialog. Make sure that you enable continuous refresh by clicking on the icon. You can export data to .csv format and import them to programs such as Microsoft® Excel® or MATLAB®. Figure 7 shows an example of the plot in CCS. The example shows an FFT plot of a sinewave with $V_{amp} = 80 \text{ mV}$ and $f = 100 \text{ kHz}$.

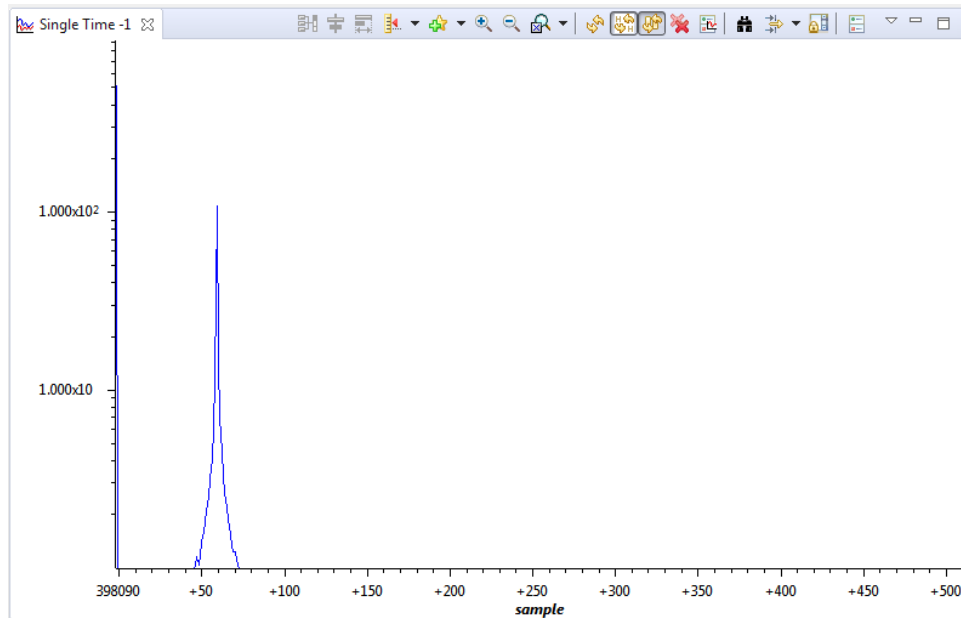


Figure 7. Graph in Code Composer Studio™ Showing 100-kHz Sinewave Magnitude Spectrum

NOTE: For detailed tutorials on how to program, compile, and debug using TI's MCUs, see processors.wiki.ti.com. Alternatively, TI also offers live support within the [E2E™](#) online community.

3.2 Testing and Results

3.2.1 Test Setup

The test setups consists of a personal computer running Code Composer Studio, TIDA-01636 reference design connected to the LaunchPad, and the source of a signal. Measurements in this section use various evaluation modules with DC-DC converters.

Figure 8 shows an example of a typical test setup.


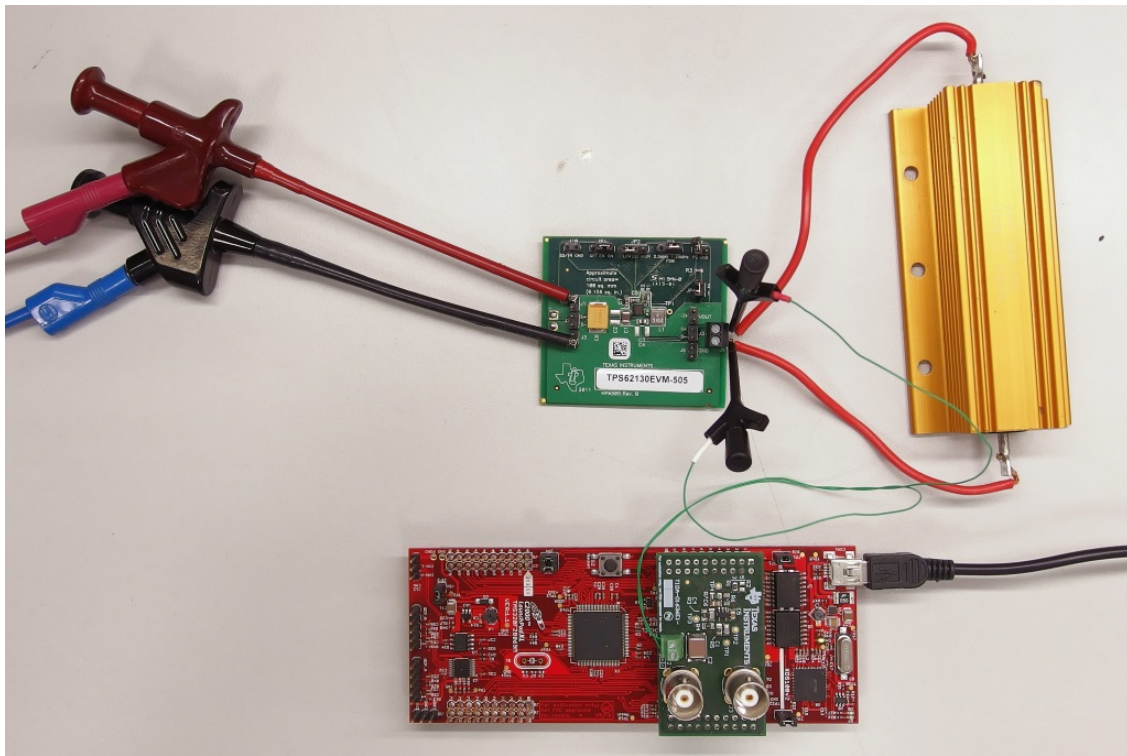


Figure 8. TIDA-01636 Test Setup

3.2.2 Test Results

3.2.2.1 TIDA-01636 Low-Pass MFB Filter Response

Figure 9 shows the TIDA-01636 filter gain and phase measurement data.

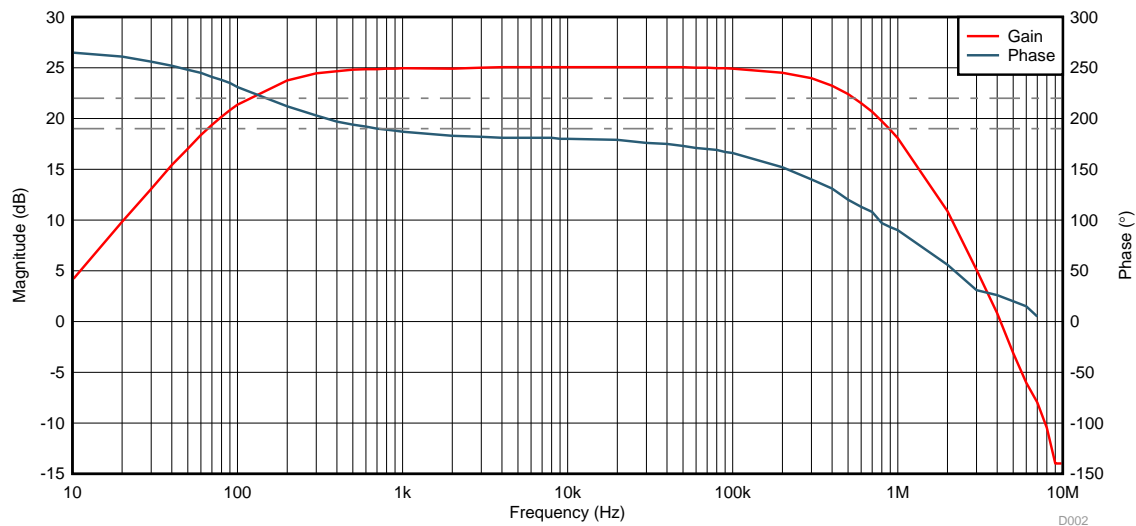

This measurement uses a 2.2- μ F capacitor in place of C2. This increases the cutoff frequency for the high-pass filter to $f_c = 117$ Hz.

Figure 9. TIDA-01636 Filter Gain and Phase Response

3.2.2.2 TIDA-01636 With LM20242EVAL

Figure 10 shows an FFT plot from the TIDA-01636 connected to the LM20242 evaluation board. The evaluation board operates in the following conditions:

- Input voltage: 16 V
- Output voltage: 3.3 V
- Load: 1 A (constant conduction mode - CCM)
- Switching frequency: nominal 300 kHz


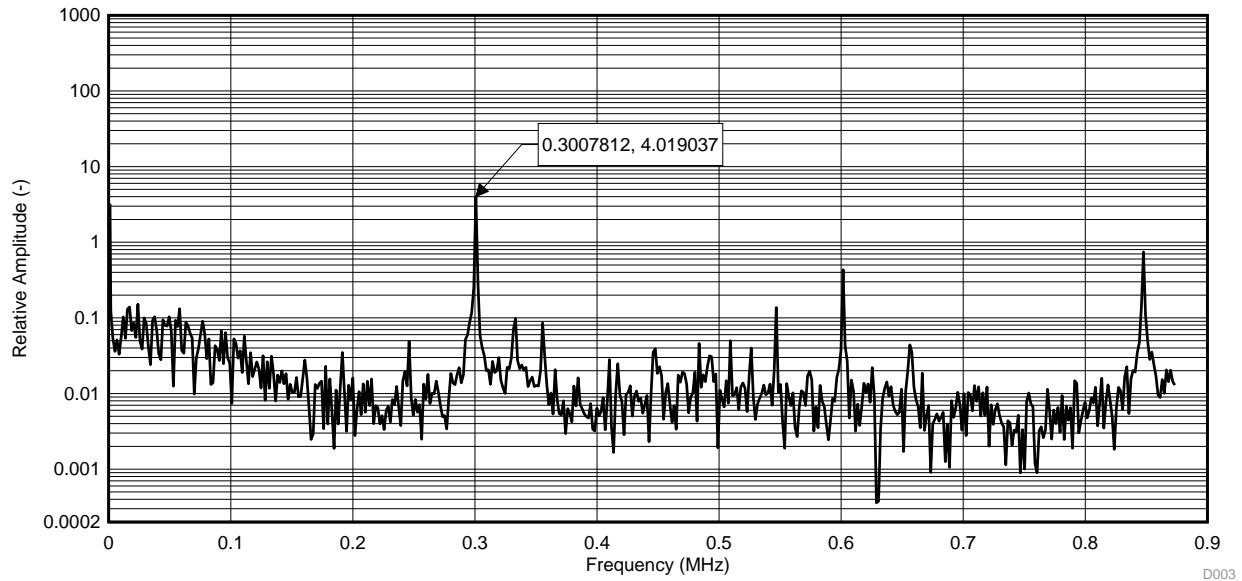


Figure 10. FFT Analysis of LM20242 Evaluation Board Running at 300 kHz in CCM

Figure 11 shows the output ripple of the LM20242 evaluation board in the time domain.

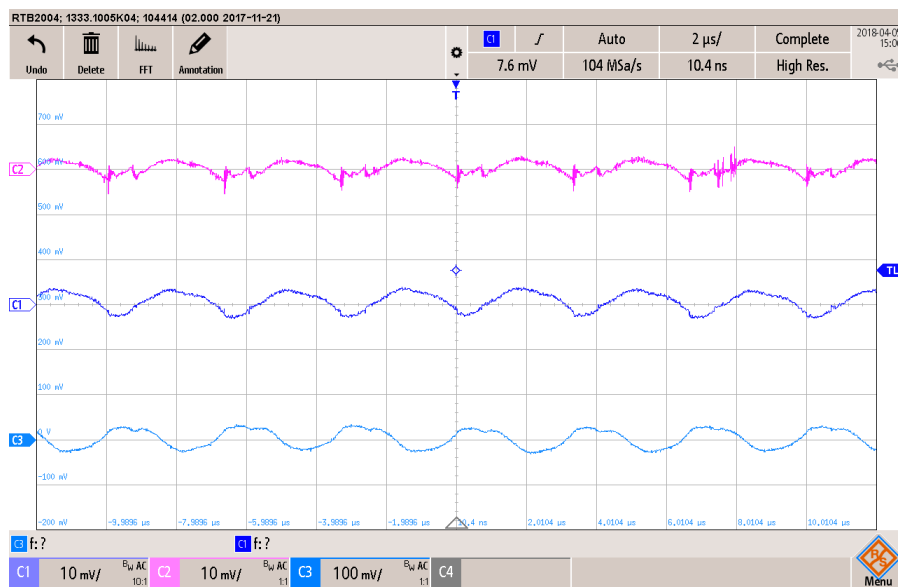

- CH1 - Voltage ripple at the output capacitor measured with 1:10 oscilloscope probe with spring ground terminal.
- CH2 - Signal at the input of the TIDA-01636.
- CH3 - Signal at the output of the TIDA-01636.

Figure 11. TIDA-01636 and LM20242 EVM Waveforms (CCM)

3.2.2.3 TIDA-01636 With LM3100EVAL

Figure 10 shows an FFT plot from the TIDA-01636 connected to the LM3100 evaluation board. The evaluation board operates in the following conditions:

- Input voltage: 16 V
- Output voltage: 3.3 V
- Load: 1 A (constant conduction mode - CCM)
- Switching frequency: nominal 250 kHz

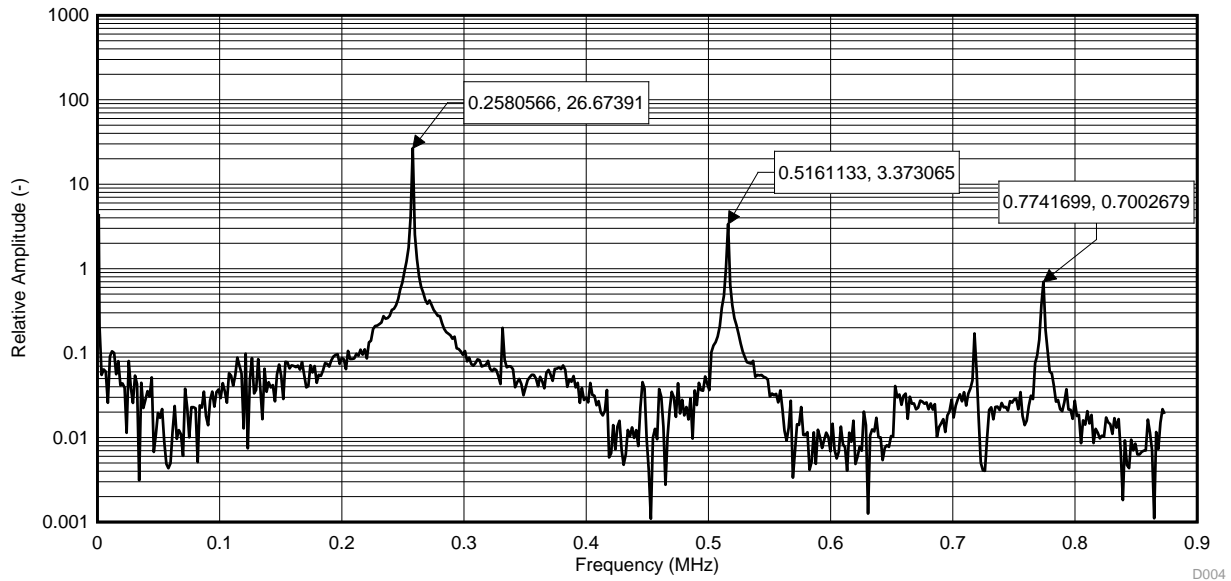


Figure 12. FFT Analysis of LM3100 Evaluation Board Running at 250 kHz in CCM

Alternatively, Figure 13 shows the board operating in discontinuous mode (DCM).

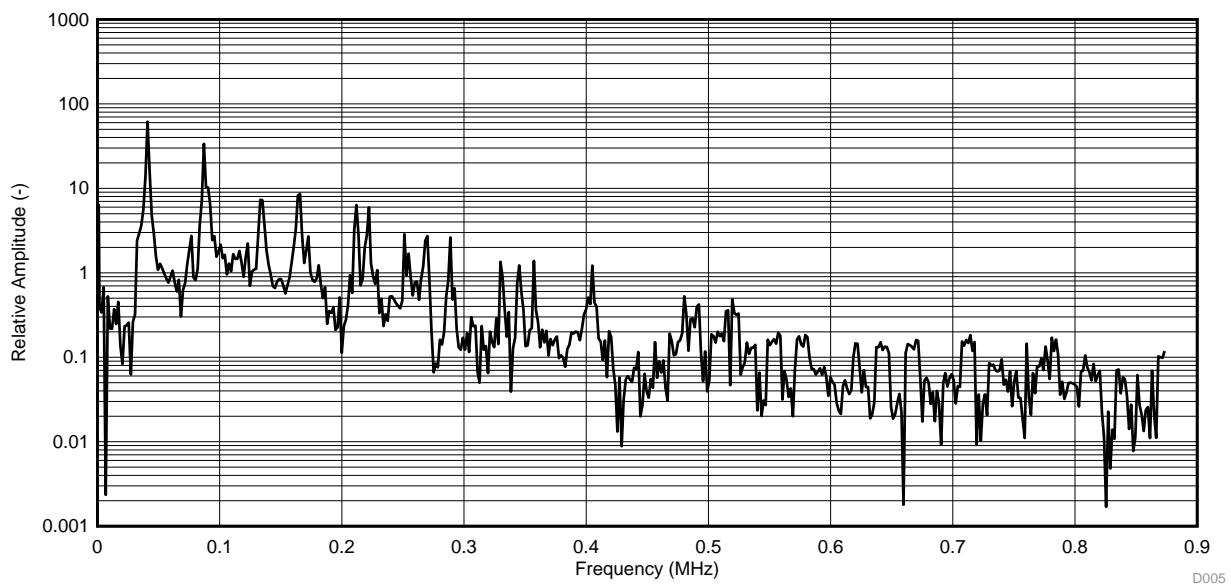


Figure 13. FFT Analysis of LM3100 Evaluation Board Running at 250 kHz in DCM

Figure 14 shows the output ripple of the LM3100 evaluation board in the time domain when operating in CCM.



- CH1 - Voltage ripple at the output capacitor measured with 1:10 oscilloscope probe with spring ground terminal.
- CH2 - Signal at the input of the TIDA-01636.
- CH3 - Signal at the output of the TIDA-01636.

Figure 14. TIDA-01636 and LM3100 EVM Waveforms (CCM)


3.2.2.4 TIDA-01636 With LM3150EVAL

Figure 15 shows an FFT plot from the TIDA-01636 connected to the LM3150 evaluation board. The evaluation board operates in the following conditions:

- Input voltage: 13.2 V
 - Output voltage: 3.3 V
 - Load: 2 A (constant conduction mode - CCM)
 - Switching frequency: nominal 650 kHz
- Note the aliased 2nd and 3rd harmonics.

Figure 15. FFT Analysis of LM3150 Evaluation Board Running at 650 kHz in CCM

Figure 16 shows the output ripple of the LM3150 evaluation board in the time domain when operating in CCM.

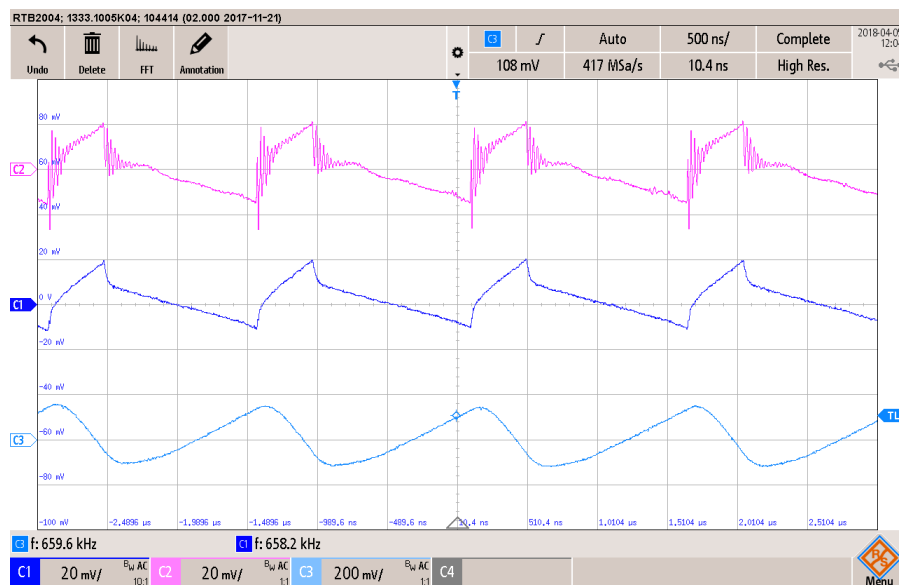

- CH1 - Voltage ripple at the output capacitor measured with 1:10 oscilloscope probe with spring ground terminal.
- CH2 - Signal at the input of the TIDA-01636.
- CH3 - Signal at the output of the TIDA-01636.

Figure 16. TIDA-01636 and LM3150 EVM Waveforms (CCM)

3.2.2.5 TIDA-01636 With LM5001 Flyback

Figure 17 shows an FFT plot from the TIDA-01636 connected to the LM5001 Flyback DC/DC converter. The DC/DC converter operates in following conditions:

- Input voltage: 24 V
- Output voltage: 2 × 5 V (isolated)
- Load: 0.5-A discontinuous mode - DCM
- Switching frequency: nominal 100 kHz


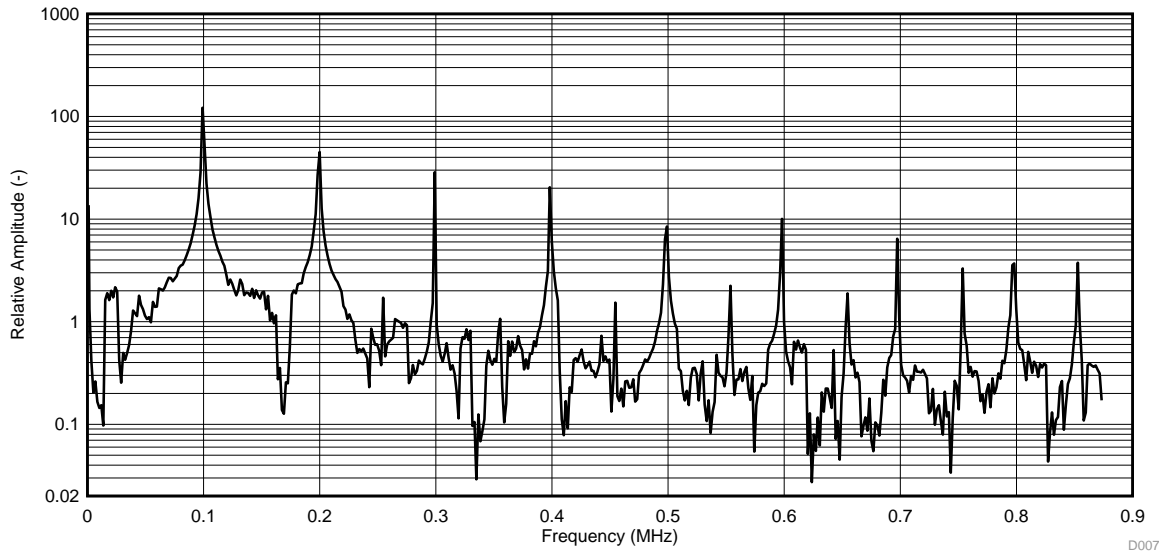


Figure 17. FFT Analysis of LM5001 Flyback DC/DC Converter Running at 100 kHz in DCM

Figure 18 shows the output ripple of the LM5001 Flyback DC/DC converter in the time domain when operating in DCM.

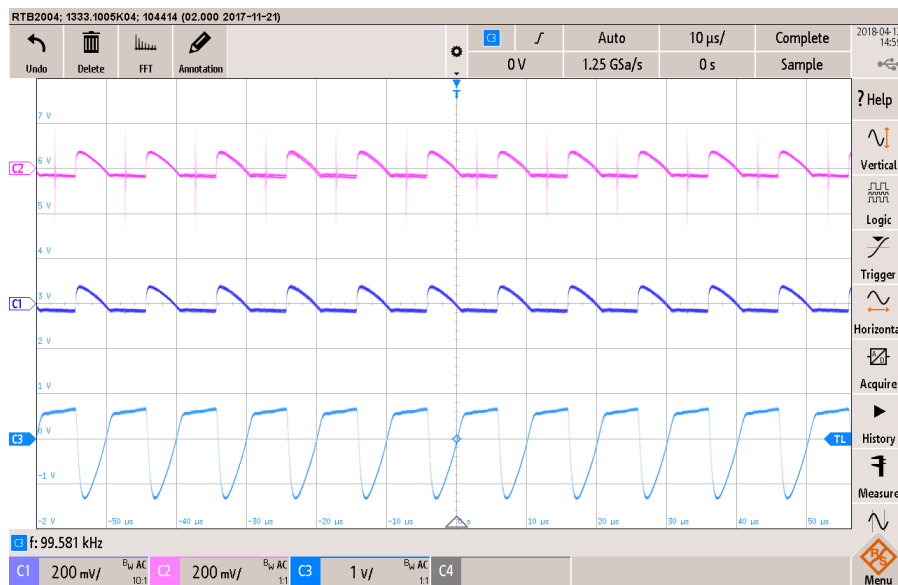

- CH1 - Voltage ripple at the output capacitor measured with a 1:10 oscilloscope probe with spring ground terminal.
- CH2 - Signal at the input of the TIDA-01636.
- CH3 - Signal at the output of the TIDA-01636.

Figure 18. TIDA-01636 and LM5001 Flyback DC/DC Converter Waveforms (DCM)

3.2.2.6 TIDA-01636 With LMZ14203HEVAL

Figure 19 shows an FFT plot from the TIDA-01636 connected to the LMZ14203 evaluation board. The evaluation board is used in following conditions:

- Input voltage: 16.3 V
- Output voltage: 12.0 V
- Load: 2 A
- Switching frequency: nominal 400 kHz

Note the aliased harmonics.


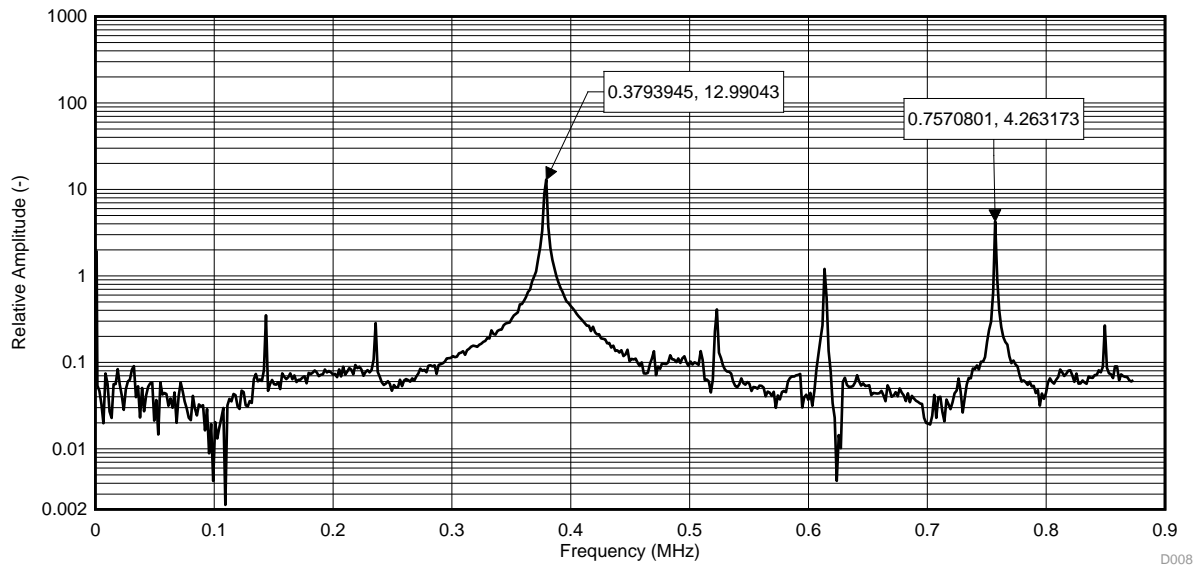


Figure 19. FFT Analysis of LMZ14203H EVM Running at Nominal 400 kHz

Figure 20 shows the output ripple of the LMZ14203H evaluation board in time domain.

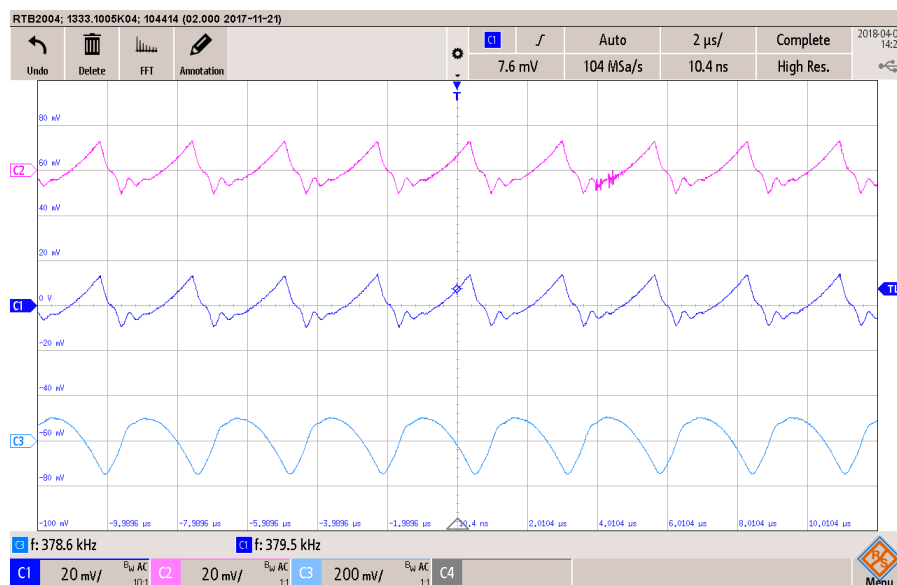

- CH1 - Voltage ripple at the output capacitor measured with a 1:10 oscilloscope probe with spring ground terminal.
- CH2 - Signal at the input of the TIDA-01636.
- CH3 - Signal at the output of the TIDA-01636.

Figure 20. TIDA-01636 and LMZ14203H EVM Waveforms

3.2.2.7 TIDA-01636 With TPS92692EVM-880

Figure 21 shows an FFT plot from the TIDA-01636 connected to the TPS92692 evaluation board. The evaluation board operates in following conditions:

- Input voltage: 12.0 V
- Full brightness
- Switching frequency: nominal 390 kHz
- Boost configuration
- Dither modulation frequency: 600 Hz


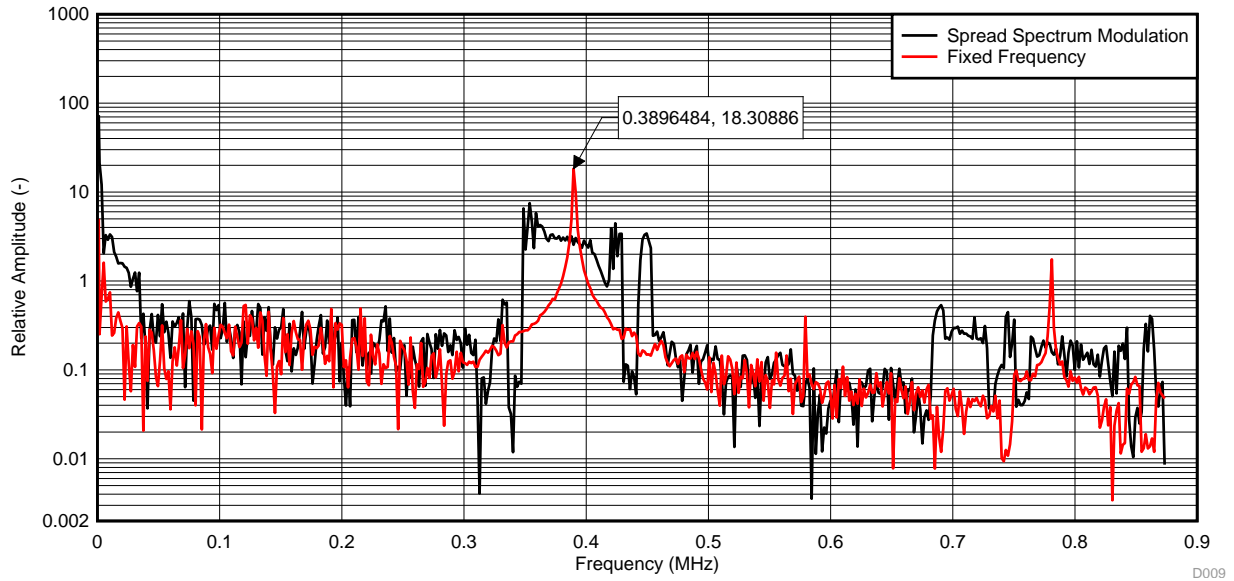


Figure 21. FFT Analysis of TPS92692 EVM Running at Nominal 390 kHz With (Blue Trace) and Without (Red Trace) Spread Spectrum Modulation

Figure 22 shows the output ripple of the TPS92692 evaluation board in the time domain.

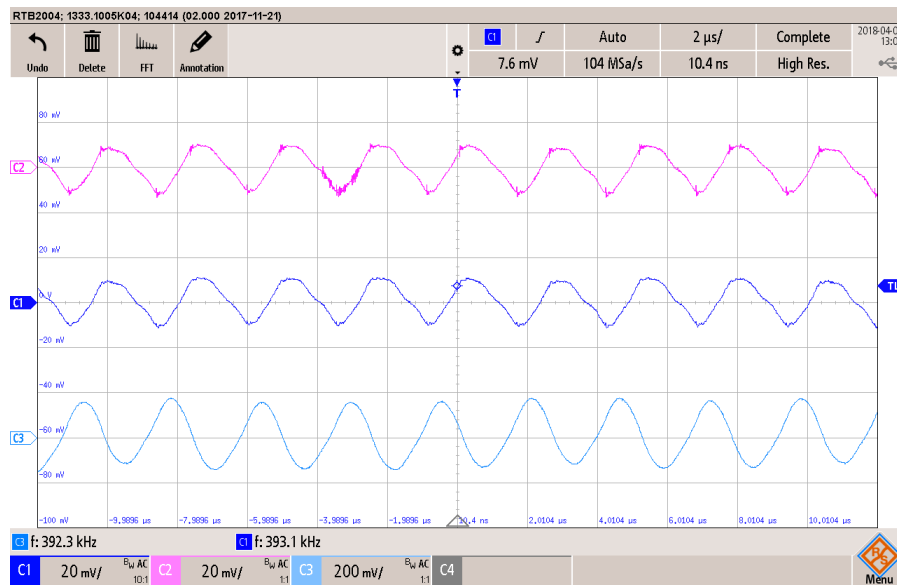

CH1 - Voltage ripple at the output capacitor measured with a 1:10 oscilloscope probe with spring ground terminal.
 CH2 - Signal at the input of the TIDA-01636.
 CH3 - Signal at the output of the TIDA-01636.

Figure 22. TIDA-01636 and TPS92692 EVM Waveforms

3.2.3 Conclusion

The TIDA-01636 reference design proves the concept of using a band-pass filter with FFT analysis for disturbances identification on a power rail. The reference design works well with signal sources operating in the lower range (<100 kHz) of the band of interest. Analysis of DC/DC converters operating with higher frequencies (>100 kHz) suffer from aliasing. TI recommends adding additional low-pass filters in-series with the output of the reference design as well as increasing sampling frequency, if possible.

4 Design Files

4.1 Schematics

To download the schematics, see the design files at [TIDA-01636](#).

4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01636](#).

4.3 PCB Layout Recommendations

The TIDA-01636 reference design does not require any special PCB layout considerations. The PCB has two layers with 35- μm copper plating. The top layer ([Figure 23](#)) is reserved for components and signal traces. The bottom layer ([Figure 24](#)) provides the current return path - signal ground.

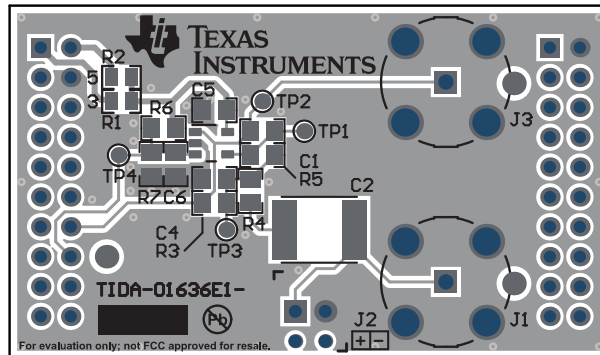


Figure 23. TIDA-01636 PCB Composite Top View

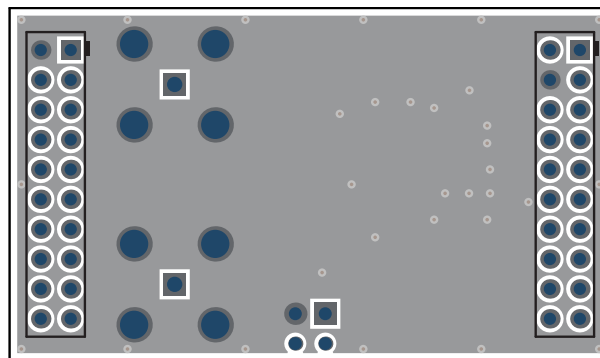


Figure 24. TIDA-01636 PCB Composite Bottom View

4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01636](#).

4.4 Altium Project

To download the Altium Designer® project files, see the design files at [TIDA-01636](#).

4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01636](#).

4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01636](#).

5 Software Files

To download the software files, see the design files at [TIDA-01636](#).

6 Related Documentation

1. Texas Instruments, [Aliasing and Anti-aliasing Filters](#), Peggy Liska

6.1 Trademarks

C2000, E2E, LaunchPad, Code Composer Studio, controlSUITE are trademarks of Texas Instruments.

Altium Designer is a registered trademark of Altium LLC or its affiliated companies.

Microsoft, Excel are registered trademarks of Microsoft Corporation.

MATLAB is a registered trademark of The MathWorks, Inc..

All other trademarks are the property of their respective owners.

7 About the Author

TIM PEISKER is an intern in the Powertrain Automotive Systems team at Texas Instruments from the Wentworth Institute of Technology in Boston, MA. Tim studies applied mathematics and prepares for his bachelor's graduation in summer 2018.

JIRI PANACEK is a systems engineer in the Powertrain Automotive Systems team at Texas Instruments where he develops reference designs. Jiri has five years of field experience in the industrial automation and most recently the HEV and EV automotive segment. Jiri earned his master's degree in microelectronics from the Brno University of Technology in the Czech Republic.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated