

Enabling Smart Solar Inverter Designs with Level Translation



Atul Patel

Green energy has become a critical component of the overall energy strategy for governments, corporations, and individuals. At the heart of green energy is the growing impact of solar power generation. Solar panel or photovoltaic (PV) installations have increased dramatically over the past few years as advancements in technology has significantly reduced the cost of photovoltaic cells that make up solar panels. One technology that has contributed to the increase in solar installations is the availability of low cost and efficient [string](#) (see [Figure 1](#)) and [micro inverter](#) technologies that help address efficiency and scalability concerns often associated with investing in solar power generation. Solar inverter technology is essential for synchronizing a solar installation with the grid so that maximum utility can be realized from the generated power. Solar inverters perform the critical function of converting the Direct Current (DC) generated by solar panels to usable Alternating Current (AC) which can be used on site for home and commercial uses or synchronized back to the grid enabling cost savings through net metering. As solar power generation continues to grow, string and micro inverters have become enabling technologies. Robust and efficient inverter designs have become critical to the PV ecosystem. Inverter systems designers now need to make their designs smarter to improve efficiency and take advantage of power saving algorithms that are being incorporated with other PV system components such as power optimizers. To make inverters smarter, system designers need to use more advanced and capable microcontrollers in their designs. The latest microcontrollers and processors are designed to be low power and extremely efficient. One of the design challenges faced by systems designers as they incorporate these new microcontrollers in their designs is having to align the lower I/O voltage levels of the microcontroller with the higher I/O voltage levels of the peripheral devices of the signal chain such as the wireless communications modules and components of the AC and DC power topologies on the inverter.

The I/O level mismatch between lower power processors and peripheral devices often involve multiple interface types and signaling standards. Interfaces such as I²C, SPI, SMBus, I²S, GPIO and many others often need to be level shifted between processors and peripheral devices. System designers are turning to level shifter integrated circuit devices to help resolve I/O level mismatches between devices in their designs in an easy, efficient, and cost-effective manner without having to sacrifice system performance. One example where level translation devices are often needed within inverter designs is the interface between the microcontroller and the wireless communication module. The MCU to wireless interface is implemented with a UART interface that often needs to be level shifted. The example in figure two shows level translation between an MCU operating at 1.8 V and a wireless module operating at 3.3 V. Level translators like TXU0204 enable design engineers to implement low power level shifting between core components for interfaces such as, UART, GPIO and virtually any other multi-bit interface as well as the low voltage I/O levels associated with low power modes of these devices. Other interfaces that might need level shifting within an inverter signal chain includes interfaces with the AC and DC power topologies as well as various sensors that can be used on a design. For common interface types such as SPI, UART and JTAG push-pull level translation devices from TI's [SN74AXC](#), [SN74LXC](#), and [TXU](#) families can provide solutions that are easy to implement with industry standard footprints. For open drain interfaces like I²C and SMBus, TI's [TXS](#) and [LSF](#) level translation families provide cost effective solutions that are available in a wide variety of channel counts and industry standard packages and pinouts. For a list of recommended level translation devices for common interface types please see table one. For More information on all of TI's level translation solutions please visit [TI's Level Translation Landing Page](#).

Table 1. Solutions for Common Level Translation Use Cases

Interface	TI Recommended Device	
	3.6 V maximum	5.5 V maximum
FET Replacement	2N7001T-Q1	SN74LXC1T45-Q1
1 Bit GPIO/Clock Signal	SN74AXC1T45-Q1	SN74LXC1T45-Q1
2 Bit GPIO	SN74AXC2T245-Q1	SN74LXC2T45-Q1 / TXU0102-Q1/TXU0202-Q1
2-Pin JTAG/UART	SN74AXC2T45-Q1	SN74LXC2T45-Q1 / TXU0102-Q1/TXU0202-Q1
I2C/MDIO/SMBus	TXS0102-Q1 / LSF0102-Q1	TXS0102-Q1 / LSF0102-Q1
4 Bit GPIO	SN74AXC4T245-Q1	TXB0104-Q1 / TXU0104-Q1
UART	SN74AXC4T245-Q1	TXB0104-Q1 / TXU0204-Q1
SPI	SN74AXC4T774-Q1 / TXB0104-Q1	TXB0104-Q1 / TXU0304-Q1
JTAG	SN74AXC4T774-Q1 / TXB0104-Q1	TXB0104-Q1 / TXU0204-Q1
I2S/PCM	SN74AXC4T774-Q1 / TXB0104-Q1	TXB0104-Q1 / TXU0204-Q1
Quad-SPI	TXB0106-Q1	TXB0106-Q1
SDIO/SD/MMC	TXS0206 or TWL1200	N/A
8 Bit GPIO/RGMII	SN74AXC8T245-Q1	SN74LXC8T245-Q1

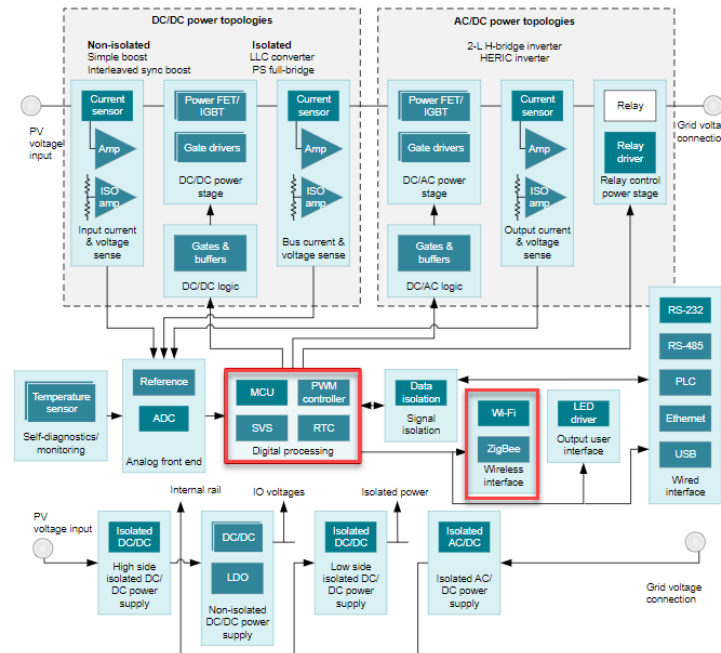


Figure 1. Solar Inverter System Reference Diagram

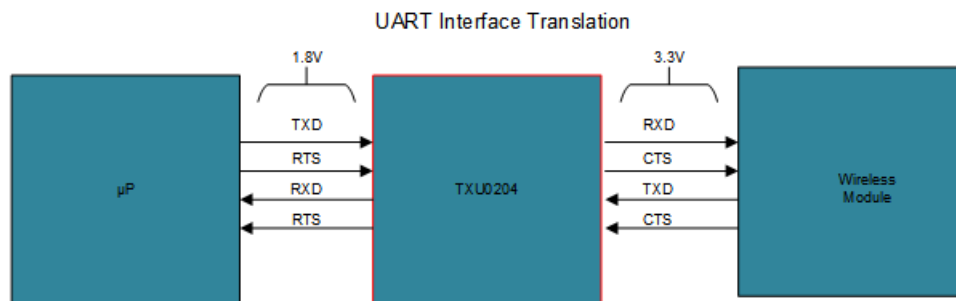


Figure 2. Level Translation Use Case for UART Interface

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated